

Mech. Dept.

LIBRARY

UNIVERSITY OF CALIFORNIA. Received Oct. , 1895

Accessions No. 60850 . Class No.









ARMATURE WINDINGS

OF

ELECTRIC MACHINES

BY

H. F. PARSHALL

MEMBER AMERICAN INSTITUTE ELECTRICAL ENGINEERS, MEMBER INSTITUTION ELECTRICAL ENGINEERS GREAT BRITAIN, MEMBER AMERICAN SOCIETY OF MECHANICAL ENGINEERS, ETC.

H. M. HOBART, S.B.

AND



NEW YORK D. VAN NOSTRAND COMPANY

LONDON ROBERT W. BLACKWELL 39 VICTORIA STREET, WESTMINSTER

1895



TK247 P3

Engineering Library

COPYRIGHT, 1895, BY D. VAN NOSTRAND COMPANY.

TYPOGRAPHY BY J. S. CUSHING & Co., NORWOOD, MASS., U.S.A.



TABLE OF CONTENTS.

00:00

Multipolar commutating dynamos — Limits of bipolar dynamos — Considerations governing choice of windings — Cases in which two-circuit windings may be employed — Importance of symmetry — Extent to which symmetry may be departed from in certain cases — Gramme windings — Lack of symmetry introduced by spider arms — Utility of twocircuit, multiple windings — Conditions affecting voltage between adjacent commutator segments — Slotted armatures — Interdependence of re-entrancy, conductors per slot, number of slots, and number of poles — Interpretation of formulæ in case of coils consisting of several conductors bound together — Alternate-current armature windings.

PART I.

CONTINUOUS-CURRENT ARMATURE WINDINGS.

CHAPTER I. - SINGLE-WOUND GRAMME RINGS

Characteristics — Methods of cross-connecting — Use of only two sets of brushes with multipolar dynamos — Methods of reducing the number of commutator segments relatively to the number of winding sections — Windings suitable for poorly balanced magnetic circuits — Diminution of sparking by use of resistances.

CHAPTER II. - DOUBLE-WOUND GRAMME RINGS .

Multiple windings — Their advantages — Limiting conditions — Importance of symmetry with small numbers of conductors — Singly and multiply re-entrant windings — Importance of avoiding the use of interpolations and cross-connections.

CHAPTER III. - TWO-CIRCUIT, SINGLE-WOUND, MULTIPOLAR RINGS .

Cases permitting the employment of two-circuit windings — Characteristics — Lack of symmetry of the armature coils — Short-connection and long-connection types — Effect of unequal air gaps — Use of long-connection type advisable for high potential armatures — Formulæ and tables for use with the long-connection gramme winding — Definition of "pitch," y — Table for use in determining permissible angular distance between brushes with different numbers of poles — Examples of two-circuit gramme windings — Chief objection to the short-connection type is the great difference of potential existing between adjacent sections of the winding — Modified types.

TABLE OF CONTENTS.

CHAPTER IV Two-Circuit, Multiple-Wound, Multipolar Rings	раде 40
Formula — Meaning of symbols — Rule for re-entrancy — Examples.	
CHAPTER V DRUM ARMATURE WINDINGS	51
General observations — Bipolar drum windings — The von Hefner-Alteneck winding — Short-chord windings; their properties and limitations — Windings in which the two active sides of a coil are diametrically opposite — Term "conduc- tors" often used for convenience, when "groups of conductors" would be more exact — "One-layer" and "two-layer" windings — Windings in which the two short-circuited coils are situated on the same diameter.	
CHAPTER VI MULTIPLE-CIRCUIT, SINGLE-WOUND, MULTIPOLAR DRUMS	71
Discussion — Explanation of diagrammatical methods for representing multipolar drum windings — Effect of different pitches with same number of face conductors — Connection at ends always made between odd and even numbered conductors — Other rules and limitations — Magnitude of differences of potential between adjacent conductors.	
CHAPTER VII MULTIPLE-CIRCUIT, MULTIPLE-WOUND, MULTIPOLAR DRUMS	77
Rules controlling conductors, pitches, and re-entrancy — Irregularities of windings much exaggerated by the small number of conductors necessarily chosen for the illustrative diagrams — Examples of various cases.	
CHAPTER VIII. — Two-Circuit, Single-Wound, Drum Armatures	87
Description of characteristics — Comparison of the merits and faults of the two-circuit and multiple-circuit windings — Formulæ and rules for applying two-circuit single windings to drum armatures — Choice of even integers for " y " involv- ing the use of different pitches at the two ends, but increasing the range of choice — Comparison of the conditions with one pair and with several pairs of brushes upon the commutator — Description of some two-circuit windings with cross-con- nected commutators possessing distinctive features with regard to the possible numbers of coils — Description of a two-cir- cuit drum winding devised by Wenström.	
CHAPTER IX INTERPOLATED COMMUTATOR SEGMENTS	107
A study of the distribution of potential in winding and commutator in the case of some two-circuit drum windings with interpolated commutator segments — Discussion of results.	
CHAPTER X. — Two-Circuit, Multiple-Wound, Drum Armatures	114
General formula — Meaning of symbols — Rules — Conditions of re-entrancy — Scheme of symbolical representation of two-circuit multiple windings — Numerous examples.	
CHAPTER XI.— THE SAYERS WINDING	158
PART II.	

WINDINGS FOR ALTERNATE-CURRENT DYNAMOS AND MOTORS.

Comparison of alternating-current with continuous-current windings — Special considerations involved in design of alternating-current windings — Multi-coil and uni-coil windings — Slotted (or ironclad) and smooth-core construction — High and low voltage windings — Alternating continuous-current commutating machines — Explanation of diagrams — Advantages of multi-coil construction in certain cases.

TABLE OF CONTENTS.

 \mathbf{v}

CHAPTER XIII SINGLE-PHASE WINDINGS	PAGE 166									
Examples of uni- and multi-coil windings — Bar windings — Windings that may be used interchangeably for single and multiphase work — Advantages of symmetry and simplicity — Windings that permit the armature to be built and shipped in segments — Unevenly distributed windings.										
CHAPTER XIV. — QUARTER-PHASE WINDINGS	213									
APTER XIV. — QUARTER-PHASE WINDINGS										
CHAPTER XV. — THREE-PHASE WINDINGS	245									
Typical diagram — Discussion of three-phase windings — Rules regarding voltage — "Y" connection — Delta (Δ) connection — Directions for making these connections — Examples of three-phase windings — Induction motors — Three-phase, continuous-current, commutating machines — Relation of voltage between collector rings to continuous-current voltage at commutator in case of three-phase, continuous-current, commutating machines.	and multi-coil — Windings for quarter-phase, continuous-current, commutating machines — Use of two-circuit and multiple- circuit windings for such machines — Ratio of collector ring to commutator voltage in this class of commutating machines. HAPTER XV. — THREE-PHASE WINDINGS									
PART III.										
APTER XIII SINGLE-PRASE WINDINGS 106 Examples of uni- and multi-coil windings - Bar windings - Windings that may be used interchangeably for single and multiphase work - Advantages of symmetry and simplicity - Windings that permit the armature to be built and shipped in segments - Unevenly distributed windings. 213 AFTER XIV QUARTER-PHASE WINDINGS 213 Meaning of the term "uni-coil" when applied to multiphase windings - Examples of quarter-phase windings, uni-coil and multi-coil - Windings for quarter-phase, continuous-current, commutating machines - Use of two-circuit and multiple-circuit windings for such machines - Ratio of collector ring to commutator voltage in this class of commutating machines. AFTER XV THREE-PHASE WINDINGS 245 Typical diagram - Discussion of three-phase windings - Rules regarding voltage - "Y" connection - Delta (Δ) 245 Ouncetion - Directions for making these connections - Examples of three-phase windings - Induction motors - Three-phase, continuous-current, commutating machines. 245 PART III. WINDING FORMULÆ AND TABLES.										

CHAPTER XVI FORMULÆ FOR ELECTROMOTIVE FORCE					•	•	•		275
Alternating-current windings — Continuous-current windings — Windings for a tating machines, quarter-phase and three-phase.	alterna	ting,	conti	nuou	s-curi	cent, d	comn	ıu-	
CHAPTER XVII METHOD OF APPLYING THE ARMATURE-WINDING TABLES	•								277
Illustrative examples.									
CHAPTER XVIII. — ARMATURE-WINDING TABLES									279
Drum-Winding Constants									280
SUMMARIZED CONDITIONS FOR TWO-CIRCUIT SINGLE WINDINGS				•					281
SUMMARIZED CONDITIONS FOR TWO-CIRCUIT DOUBLE WINDINGS									282
SUMMARIZED CONDITIONS FOR TWO-CIRCUIT TRIPLE WINDINGS									283
WINDING TABLES FOR TWO-CIRCUIT SINGLE WINDINGS									285
WINDING TABLES FOR TWO-CIRCUIT DOUBLE WINDINGS		•							295
WINDING TABLES FOR TWO-CIRCUIT TRIPLE WINDINGS									305
WINDING TABLES FOR MULTIPLE-CIRCUIT SINGLE WINDINGS .						•			315
WINDING TABLES FOR MULTIPLE-CIRCUIT DOURLE WINDINGS .									331
WINDING TABLES FOR MULTIPLE-CIRCUIT TRIPLE WINDINGS .									347





PART I.

CHAPTER I. - SINGLE-WOUND GRAMME RINGS.

It's G KK				PAGE
1. — Gramme ring — Four-circuit, single winding — Four poles				. 3
2 Gramme ring - Two-circuit, single winding - Two poles				. 3
3. — Gramme ring — Four-circuit, single winding — Four poles — Cross-connected				. 5
4. — Gramme ring — Four-circuit, single winding — Four poles — Cross-connected				. 6
5. — Gramme ring — Four-circuit, single winding — Four poles				. 9
6 Gramme ring - Four-circuit, single winding - Four poles - One-half normal number of com	mutator seg	gments		. 10
7 Gramme ring - Four-circuit, single winding - Four poles - One-fourth normal number of co	mmutator a	segments	š.	. 13
8 Gramme ring - Fonr-circuit, single winding - Coils of one circuit from brush to brush, not in	n adjacent	fields		. 14

CHAPTER II. - DOUBLE-WOUND GRAMME RINGS.

9. — Gramme ring — Two-circuit, doubly re-entrant, double winding — Two poles					17
10. — Gramme ring — Four-circuit, doubly re-entrant, double winding — Four poles					18
11 Gramme ring - Four-circuit, singly re-entrant, double winding - Four poles					21

CHAPTER III. - TWO-CIRCUIT, SINGLE-WOUND, MULTIPOLAR RINGS.

	N	o. of poles $= n$.	No. of coils $=s$.	Pitch $= y$.	No. of commu- tator segments.	
12. — Gramme ring — Two-circuit, single winding — Long-connection type		4	15	7	15	25
13. — Gramme ring — Two-circuit, single winding — Long-connection type		10	51	10	51	26
14. — Gramme ring — Two-circuit, single winding — Long-connection type		10	46	9	46	29
15. — Gramme ring — Two-circuit, single winding — Long-connection type (modifie	ed).	4	19	9	28	30
16. — Gramme ring — Two-circuit, single winding — Long-connection type (modifie	ed).	6	19	6	57	33
17. — Gramme ring — Two-circuit, single winding — Short-connection type		4	34	7 & 9	17	34
18. — Gramme ring — Two-circuit, single winding — Short-connection type		4	22	5	11	37
19 Gramme ring - Two-circuit, single winding - Long-connection type (modifie	ed) -	- Four pe	oles — One	-half a	s many com-	
mutator segments as coils						38

CHAPTER IV. - TWO-CIRCUIT, MULTIPLE-WOUND, MULTIPOLAR RINGS.

	No.	of poles $= n$.	No. of coils $= s$.	No. of wind- ings = m .	Re- entrancy.	Pitch $= y$.	•
20. — Gramme ring — Two-circuit, doubly re-entrant, double winding		4	26	2	00	12	PAOE 41
21. — Gramme ring — Two-circuit, singly re-entrant, double winding		4	24	2	0	11	42
22. — Gramme ring — Two-circuit, singly re-entrant, double winding		6	23	2	@* 1+	7	45
23. — Gramme ring — Two-circuit, singly re-entrant, triple winding		4	23	3	0	10	46
24. — Gramme ring — Two-circuit, singly re-entrant, triple winding -	_						
Twice normal number of commutator segments		4	23	3	0	10	49

CHAPTER V.-DRUM ARMATURE WINDINGS.

25. — Bipolar drum — Two-circuit, single winding — One layer — Sixteen conductors	53
26. — Bipolar drum — Two-circuit, single winding — One layer — Short chord — Thirty-two conductors	54
27 Bipolar drum - Two-circuit, single winding - One layer - Thirty conductors - Two sides of coil diametrically opposite	57
28. — Bipolar drum — Two-circuit, single winding — One layer — Short chord — Thirty conductors	58
29. — Bipolar drum — Two-circuit, single winding — One layer — Short chord — Thirty conductors	61
30 (a, b, c, and d). — Bipolar drums — Two-circuit, single windings — One and two layers — Fourteen and sixteen conductors	62
31 Bipolar drum - Two-circnit, single winding - Two layers - Thirty-two conductors - Two sides of coil diametrically	
opposite	65
32. — Bipolar drum — Two-circuit, single winding — Two layers — Short chord — Thirty-two conductors	66
33 Bipolar drum - Two-circuit, single winding - Two layers - Twenty-eight conductors - Coils of outer and inner layers	
alternately connected	69

CHAPTER VI. -- MULTIPLE-CIRCUIT, SINGLE-WOUND, MULTIPOLAR DRUMS.

				N	$ \begin{array}{l} \text{Ko. of poles} \\ = n, \end{array} $	No. of conductors $=C$,	Pitch $= y$.	
34. — Multipolar drum — Six-circuit, single winding					6	50	7 & 9	70
35. — Multipolar drum — Six-circuit, single winding					6	50	5 & 7	73
36. — Multipolar drnm — Six-circuit, single winding					6	80	11 & 13	74

CHAPTER VII. -- MULTIPLE-CIRCUIT, MULTIPLE-WOUND, MULTIPOLAR DRUMS.

	No. of poles $= n$.	No. of con- ductors $= C$.	No. of wind- ings = m .	Re- entrancy.	Pitch $= y$.	
37. — Multipolar drum — Six-circuit, singly re-entrant, triple winding .	. 6	50	3	0	5 & 11	79
38 Multipolar drum - Four-circuit, doubly re-entrant, quadruple winding	4	44	4	00	5 & 13	80
39. — Multipolar drum — Four-circuit, doubly re-entrant, quadruple winding	4	44	4	\odot	7 & 15	83
40. — Multipolar drum — Six-circuit, singly re-entrant, double winding .	. 6	50	2	0	5 & 9	84

CHAPTER VIII. - TWO-CIRCUIT, SINGLE-WOUND, DRUM ARMATURES.

	No. of poles $= n$.	No. of conductors $= C$.	Pltch = y .				
41. — Multipolar drum — Two-circuit, single winding .	. 4	34	9.				89
42. — Multipolar drum — Two-circuit, single winding .	. 4	34	7 & 9 .				90
43. — Multipolar drnm — Two-circuit, single winding .	. 6	68	11 .			 Ξ.	93
44 Multipolar drum - Two-circuit, single winding .	. 6	50	7 & 9 .	t			94

viii

FIGURE	N	o. of poles $= n$.	No. of conductors $= C$.	Pitch $= v_{1}$		PAGE
45. — Multipolar drum — Two-circuit, single winding .		8	56	7	Cross-connected commutator	97
46. — Multipolar drum — Two-circuit, single winding .		8	48	5 & 7	Cross-connected commutator	98
47. — Multipolar drum — Two-circuit, single winding .		8	56	7 & 21	Cross-connected commutator	101
48. — Multipolar drum — Two-circuit, single winding .		8	52	7 & 19	Cross-connected commutator	102
49. — Multipolar drum — Two-circuit, single winding — F	our-	pole wire-	wound armatu	re (Wens	tröm)	105

CHAPTER IX. - INTERPOLATED COMMUTATOR SEGMENTS.

			N	to, of poles $= n$.	Pitch $= y$.	No. of conductors $=C$.	No. of commu- tator segments.	
50. — Multipolar drum — Two-circuit, single winding				6	13	80	80	106
51. — Multipolar drum — Two-circuit, single winding				6	7	44	66	109
52. — Multipolar drum — Two-circuit, single winding				8	5	42	42 '	110
53. — Multipolar drum — Two-circuit, single winding				8	5	42	84	113

CHAPTER X. - TWO-CIRCUIT, MULTIPLE-WOUND, DRUM ARMATURES.

	No. of poles $= n$.	No. of conductors =C.	No. of winding $= m$.	8 Re-entrancy.	Pitch=y.	
54. — Multipolar drum — Two-circuit, singly re-entrant, double winding,	4	32	2	0	7	115
55 Multipolar drum - Two-circuit, singly re-entrant, double winding,	4	32	2	0	7	116
56 Multipolar drum - Two-circuit, singly re-entrant, triple winding .	4	70	3	0	15 & 17	119
57. — Multipolar drum — Two-circuit, triply re-entrant, triple winding .	4	66	3	000	15	120
58 Multipolar drum - Two-circuit, singly re-entrant, double winding,	6	58	2	0	9	123
59 Multipolar drum - Two-circuit, doubly re-entrant, double winding,	6	52	2	00	7 & 9	124
60. — Multipolar drum — Two-circuit, triply re-entrant, triple winding .	6	60	3	000	9	127
61 Multipolar drum - Two-circuit, singly re-entrant, triple winding .	6	54	3	0	7 & 9	128
62. — Multipolar drum — Two-circuit, triply re-entrant, triple winding .	6	78	3	000	11 & 13	131
63 Multipolar drum - Two-circuit, singly re-entrant, quadruple						
winding	6	50	4	000	7	132
64 Multipolar drum - Two-circuit, quadruply re-entrant, quadruple						
winding	6	56	4	0000	7 & 9	135
65 Multipolar drum - Two-circuit, doubly re-entrant, quadruple						
winding	6	68	4	00	9 & 11	136
66. — Multipolar drum — Two-circuit, quadruply re-entrant, quadruple						
winding	6	80	4	0000	11 & 13	139
67 Multipolar drum - Two-circuit, quadruply re-entrant, quadruple						
winding	6	104	4	0000	15 & 17	140
68 Multipolar drum - Two-circuit, quadruply re-entrant, quadruple						
winding	6	88	4	0000	15 & 17	143
69 Multipolar drum - Two-circuit, triply re-entrant, sextuple winding,	6	66	6	000	9	144
70. — Multipolar drum — Two-circuit, doubly re-entrant, sextuple						
winding	6	72	6	60 60	9 & 11	147
71 Multipolar drum - Two-circuit, singly re-entrant, sextuple winding,	6	78	6	(00000)	11	148
72. — Multipolar drum — Two-circuit, sextuply re-entrant. sextuple						
winding	6	84	6	000000	11 & 13	151

.

ix

71GURE 73. — Multipolar drum — Two-circuit, doubly re-entrant, double winding	No. of poles = n . . 8	No. of con- ductors=C. 84	No. of wind- ings=m. 2	Re- entrancy.	Pitch = y. 9 & 11	PAOR 152
74 Multipolar drum - Two-circuit, singly re-entrant, double winding	. 8	84	2	0	11	155
75. — Multipolar drum — Two-circuit, singly re-entrant, double winding	. 8	92	2	0	11	156

CHAPTER XI. - THE SAYERS WINDING.

. 159

76. — Diagram of the Savers winding .		
---------------------------------------	--	--

PART II.

CHAPTER XII. - ALTERNATING-CURRENT WINDINGS.

CHAPTER XIII. - SINGLE-PHASE WINDINGS.

77. — Uni-coil winding — Two coils per group — Sixteen poles — Sixteen coils	167
78. — Uni-coil winding — One coil per group — Twenty-four poles — Twelve coils	168
79. — Bar winding — Twenty-four poles — Twenty-four conductors	171
80. — Overlapping, uni-coil winding — Twenty-four poles — Twelve coils	172
81. — Two-coil winding — One coil per group — Sixteen poles — Sixteen coils	175
82 Bar winding - Sixteen poles - Thirty-two conductors	176
83. — Two-coil winding — One coil per group — Sixteen poles — Sixteen coils	179
84. — Overlapping, two-coil winding — One coil per group — Sixteen poles — Sixteen coils	180
85. — Bar winding — Sixteen poles — Thirty-two conductors	183
86. — Overlapping, two-coil winding — One coil per group — Sixteen poles — Sixteen coils	184
87. — Overlapping, two-coil winding — Two coils per group — Sixteen poles — Thirty-two coils	187
88. — Overlapping, three-coil winding — Oue coil per group — Sixteen poles — Twenty-four coils	188
89. — Bar winding — Sixteen poles — Forty-eight conductors	191
90. — Overlapping, three-coil winding — One coil per group — Sixteen poles — Twenty-four coils	192
91. — Bar winding — Sixteen poles — Forty-eight conductors	195
92 Partially overlapping, three-coil winding - One coil per group - Sixteen poles - Twenty-four coils	196
93. – Bar winding – Sixteen poles – Forty-eight conductors	199
94. — Partially overlapping, three-coil winding — One coil per group — Sixteen poles — Twenty-four coils	200
95. — Three-coil winding — One coil per group — Sixteen poles — Twenty-four coils	203
96. — Non-overlapping winding with one and one-half coils per pole piece — Two coils per group — Twenty poles — Thirty coils .	204
97. — Unevenly distributed, two-coil winding — Twelve poles — Twelve coils	207
98. — Unevenly distributed bar winding — Eight poles — Twenty-four conductors	208
99. — Unevenly distributed two-coil winding — Sixteen poles — Sixteen coils	211
	and the sta

CHAPTER XIV. - QUARTER-PHASE WINDINGS.

100. — Overlapping, uni-coil winding — Oue coil per group — Sixteen poles — Sixteen coils					212
101 Bar winding - Sixteen poles - Thirty-two conductors			••		215
102 Non-overlapping, uni-coil winding - Two coils per group - Eight poles - Sixteen coils					216
103. — Overlapping, uni-coil winding — Two coils per group — Sixteen poles — Thirty-two coil	s .				219
104. — Two-coil winding — Twelve poles — Twenty-four coils					220

.

x

PAGE
223
224
227
228
231
232
235
236
239
240
243

CHAPTER XV. - THREE-PHASE WINDINGS.

116	- Uni-coil winding - Twenty poles - Thirty coils .	•										•				244
117. –	-Diagrams showing "delta" (Δ) and "Y" connections	5	•				•							•		247
118. –	- Bar winding — Twenty poles — Sixty conductors															248
119. –	- Non-overlapping winding - Two coils per group - Tw	went	y pol	es —	Thirt	y coil	s — (One a	and c	ne-ha	lf coi	ls pe	r pol	e piec	e	
	per phase						•	•	•							251
120. –	- Bar winding — Twenty poles — Sixty conductors						•		•							252
121	- Two-coil winding - Eight poles - Twenty-four coils						•									255
122. –	- Bar winding - Eight poles - Forty-eight conductors						•									256
123. –	- Two-coil winding - Eight poles - Twenty-four coils															259
124. –	- Bar winding - Eight poles - Forty-eight conductors							•								260
125. –	- Bar winding - Six poles - Fifty-four conductors.											•				263
126	- Bar winding - Four poles - Fifty-one conductors	•	•			•	•				•					264
127	- Bar winding — Six poles — Fifty-one conductors .	•	•				•					•				267
128. –	- Two-circuit winding for a three-phase, continuous-cur	rent,	com	muta	ting 1	nachi	ne —	-Six	pole	s - Si	ixty-e	ight	cond	uctor	s	268
129	- Six-circuit winding for a three-phase, continuous-curre	ent, o	comn	nutati	iug m	achin	.e —	Six]	poles	-108	8 con	ducto	ors			271

xi





-00:0:00-

THE present treatise is the outcome of an investigation made a number of years ago, before the principles of the armature winding of multipolar commutating dynamos were generally understood by electricians. At that time it appeared that the demand for dynamos of greater current output could only be met satisfactorily by dynamos of the multipolar type, since with bipolars beyond a certain output the number of commutator segments compatible with freedom from sparking was found to be incompatible with the maximum armature reaction which experience has shown to be permissible. After some study it was concluded the only feature of the multipolar dynamo requiring special study was that of the armature windings.

A considerable number of diagrams were prepared and classified; the advantages and disadvantages of each, and the comparative fitness of these windings for different purposes, noted. Inasmuch as it was found convenient to refer to this data frequently, and on account of the comparative inaccessibility of such information when in the form of notes, we decided that it would be a great convenience to electricians generally if our notes were published in book form. We therefore proceeded to do this; but owing to the intervention of certain circumstances contingent to our position in an industrial concern, it became necessary to lay aside this work until those competent to judge of its nature should feel able to permit us to proceed as we had wished. The delay has not been disadvantageous, since in the meantime we have not laid the work aside; on the contrary, we have made a study of the properties of a number of the more important windings, so that the original manuscript has been largely added to.

In the section on continuous-current armature windings our endeavor has been to include only those windings that possess some practical merit, and we have frequently pointed out the advantages and disadvantages peculiar to certain classes of windings. The thought will probably occur to the reader, which one of these windings should be selected for a given voltage after the number of poles and the magnitude of the magnetic flux at the poles have been assigned a proper value. We cannot point out the fitness of each winding for a given purpose, since this is more or less dependent upon the magnetic characteristics peculiar to any particular design. Thus in some machines of particularly good characteristics two-circuit windings have been used in the generation of comparatively large currents with some success, when had the magnetic characteristics of the dynamos been ordinarily good, the use of the two-circuit winding would have been attended with results entirely unsatisfactory.

INTRODUCTORY.

In general, we may state, the type of winding should be determined with reference to the magnitude of the current to be generated. Any deviation from a perfectly symmetrical arrangement of the armature conductors should be inversely proportional to the magnitude of the currents to be generated. When the currents to be generated are large, the coils should be similarly situated with respect to each other, and should all have the same resistance and inductance. It has been frequently found that when the conductors are dissimilarly situated with respect to each other or to any other body that can affect the armature conductors inductively, the wearing away of the commutator is uneven, the trouble increasing more and more as the currents in the conductors are increased, or the resistance of the collecting brushes diminished. Especially in armatures in which there are more than two coils in a slot this uneven wearing away of the commutator has been noticed. In this case the coils are of slightly unequal area, due to the progression of the winding from slot to slot.

In gramme windings the lack of symmetry may be due to some of the coils being longer than the others, or carried near the spider arms.

It may, therefore, be stated generally that when a given result has to be obtained without experimenting, such windings as these are to be avoided when the currents in the conductors have to be of any considerable magnitude.

The utility of the double, triple, and quadruple windings shown and described depends very largely upon the maximum arc upon the commutator over which uniform contact resistance can be obtained. With the thickness of segments now common in practice, only double and triple windings appear to be of practical value, since, in general, brushes cannot be relied upon to maintain a uniform contact over an arc of much more than three-quarters of an inch in width. When the width of the brush has to exceed this amount, it is found that it bridges imperfectly from commutator bar to commutator bar in the same winding, thereby causing sparking.

A feature peculiar to these windings, as well as to some of the two-circuit single windings, is that the voltage between adjacent commutator sections is affected by the angular distance between the different sets of collecting brushes. With some of these windings the voltage between adjacent commutator sections varies simply according to the field strength when the angle between the different sets of brushes corresponds to the angle between the centers of the poles. In other windings the voltage between adjacent commutator sections varies by jumps, but may be made to vary according to the field strength by slightly varying the position of some one set of brushes with respect to the other sets. This feature of the different windings is a subject for special investigation, and is of more or less importance, according to the nature of the winding and the average voltage between commutator bars.

We have frequently made mention of the number of slots. With respect to slotted armatures in general, it is to be remembered that an additional condition to that for smooth-core armatures has to be fulfilled; *i.e.* the total number of the conductors to suit the equations for re-entrancy has to be divisible by the number of conductors possible to place in a slot, this number being dependent upon the number of poles. The number of conductors permissible per slot for two-circuit windings for different numbers of poles is shown in a table.

We have omitted any reference to mechanical details of construction of armature windings, since these permit of great variety, without in any way modifying the results. Further, they are a part of the stock in trade of the electrical manufacturer.

The drum windings considered are principally those in which the end connections are interchangeable, and

XIV

INTRODUCTORY.

are in the form of evolutes, as in the Eickemeyer and Hopkinson windings, description of which will be found in Weymouth's "Drum Armatures and Commutators" ("The Electrician" Printing and Publishing Company, London, 1893). In general, such windings possess the advantages that all coils are of equal inductance and resistance, are equally accessible, have equal radiating surfaces, and are most easily repaired. When a coil consists of a number of conductors, bound together so as to be considered a single unit mechanically, it is so considered in the text, and in the formulæ for the arrangement of conductors.

These windings appear to have been invented by Bollmann, Desroziers, Fritsche, Pischon, Eickemeyer, and others; but inasmuch as it is a disputed question as to which of these inventors has the right to claim priority, and as there may be more or less litigation before the question is settled, we have considered it best to omit all discussion as to who may have invented any of the windings. Where with a winding is given the name of a supposed inventor, it is simply because that winding has been known under that name, and not because the writers possess any special evidence to show by whom the winding was invented. After the possibility of litigation has ceased we hope to do justice to all inventors concerned, giving to each his proper proportion of credit for the work he has done.

We believe that the tables on drum windings are a feature that should meet with especial favor, since after the number of conductors required for a given type of winding has been determined, the proper pitches for any style of winding can be found in the tables. Further, by referring opposite to this number of conductors in the different tables it may be ascertained at a glance whether, by slightly changing the end connections, the winding may be adapted to some other voltage. Such features, peculiar to certain numbers of conductors, are frequently in practice of the greatest importance. As a practical example take the following ease: In a six-pole machine with 104 armature conductors, the winding may be connected for a two-circuit single winding by making the pitch 17 on each end, or for a two-circuit, doubly re-entrant double winding, by making the pitch 17 on one end and 19 on the other; this second arrangement being suitable for the same watt output as the first, at one-half the voltage.

In the section on alternate-current armature windings are included a number of windings that have now only a limited application in practice, as it is thought that, on account of the very limited literature on this subject, a description of all windings of any practical use will be appreciated.

With respect to the work in general, we should be glad to receive the suggestions and criticisms of all who are interested in this subject.

The following articles on armature windings have been consulted in the preparation of this book, and are mentioned here for reference : ---

ARNOLD — Die Ankerwicklungen der Gleichstrom-Dynamomaschinen. Berlin, 1891. FRITSCHE — Die Gleichstrom-Dynamomaschine. Berlin, 1889. KAPP — Practical Electrical Engineering, Vol. II., p. 43. Loudon, 1893. KITTLER — Handbuch der Elektrotechnik, Vol. I. Stuttgart, 1892. RECHNIEWSKI — L'Electricien, Vol. V. Jan. 14, 1893 et seq. THOMPSON — Dynamo-Electric Machinery. London, 1892. WEYMOUTH — The Electrician, Vol. XXV. Nov. 7 to Dec. 19, 1890.

The





PART I.

and the second s

CONTINUOUS-CURRENT ARMATURE WINDINGS.





CHAPTER I.

SINGLE-WOUND GRAMME RINGS.

THESE are the simplest windings in use, and will require only a very few diagrams and explanations. Many complex connections have been proposed, but only such forms will be discussed as are of general practical use.

The plain gramme ring, with a single winding, is shown in Figs. 1 and 2, from which it may be seen that the construction, as far as concerns location of coils, connectors, and commutator segments, is independent of the number of poles. The number of coils should be a multiple of the number of poles in order to maintain S



Fig. I FOUR-CIRCUIT, SINGLE-WINDING.



Fig.2 TWO-CIRCUIT, SINGLE-WINDING.

symmetry among all the branches from brush to brush. The number of commutator segments is equal to the number of coils. It is desirable to minimize the turns per coil, and consequently the inductance of the shortcircuited elements, by as large a number of segments as practicable.

A further discussion of these two diagrams would be superfluous, beyond calling attention to the progressive nature of the rise of potential around the ring, whereby the contiguous wires have only the small difference of potential of one turn, making the question of insulation very simple.

CHAF. 1

In cases where it is desirable to use but two brushes in multipolar rings with more than two circuits, the method of cross-connecting, shown in Fig. 3, may be used. The number of commutator segments remains equal to the number of coils. An inspection of the diagram will show that it really consists in connecting in parallel those coils occupying corresponding positions in the various fields.

It would seldom be desirable to utilize this method of connection, except in very small machines, as the use of only one pair of sets of brushes would necessitate lengthening the commutator in order to retain the proper extent of brush contact surfaces.



Fig. 3 FOUR CIRCUIT, SINGLE WINDING.



Fig. 4 FOUR CIRCUIT SINGLE WINDING

Figure 4 differs from Fig. 3 only in the use of two crossconnecting leads instead of one. This diagram would sometimes be of advantage, inasmuch as it utilizes the available space more completely and symmetrically. Each crossconnecting conductor could be of smaller cross-section than if only one were used.

Both this and the preceding method have the disadvantage that the two parallel sections have unequal resistance, due to one section having the long cross-connecting leads in series with it, and the other merely the regular short leads to the commutator.

Failure to give due attention to this point often causes serious trouble.

\$.

Figure 5 gives a winding which is *wrong*, but which has been given in the treatises of many of the specialists on windings, none of whom, except Herr Arnold, criticise it.

The fault is that the positions of the coils bear such a relation to the positions of their respective commutator segments, that during each revolution of the armature the position given in the figure is the only one in which the brushes are properly placed with regard to the diameter of commutation. In order that the brushes should always be in a position to properly perform their commutative function, they would have to be revolved in a direction opposite to that of the armature, and with a velocity equal to it.

The characteristic of the winding is that it brings together into one segment each pair of cross-connected segments of the previous diagram. As above stated, however, this diagram is worthless, except to call attention to its character, so that the text-books in which it is described shall not be misleading.

See ARNOLD — Die Ankerwicklungen der Gleichstrom-Dynamomaschinen, Fig. 42.

KITTLER — Handbuch der Elektrotechnik, 1892, Fig. 401 C. FRITSCHE — Die Gleichstrom-Dynamomaschinen, Fig 64. CHAP. I.





Fig. 6 FOUR CIRCUIT SINGLE WINDING.

In Fig. 6 the number of commutator segments is made equal to half the number of coils by connecting two coils in series between each pair of adjacent segments. The coils so connected in series are situated in adjoining fields of opposite polarity. This winding has the disadvantage that coils at quite different potentials are adjacent, as may be seen by following through the various armature circuits from brush to brush. This increases the difficulty of insulating. The volts per bar also, for the same number of conductors per coil, are twice as high as in the simple gramme ring. If it is necessary, for any reason, to halve the number of bars, it would be preferable to combine two *adjacent* coils into one, and retain the advantages of the simple gramme ring connection.

But in cases where the shape of the frame necessitates somewhat unequal magnetic circuits, this connection averages up the unequal induction in the various coils, and therefore tends to diminish the sparking which might, with a simple gramme ring in such an unbalanced magnetic system, be considerable.

If s = number of coils, and n = number of poles, then any coil is connected across to one $\left(\frac{s}{n} \pm 1\right)$ in advance of it, and the two free ends of this pair of coils are connected to adjacent commutator segments.

CHAP. I.

Figure 7 is merely a step in advance of Fig. 6, and the advantages and disadvantages pointed out in the discussion of Fig. 6 apply in still greater degree to Fig. 7.

It will be seen that the number of commutator segments is reduced to one-fourth of the number of coils by the connecting in series of four coils, one in each field, between two adjacent segments of the commutator.

As in the previous figure, the rule for connecting the coils is to connect each coil to one $\left(\frac{s}{n} \pm 1\right)$ in advance.



FOUR CIRCUIT SINGLE WINDING.


Figure 8 represents a winding in which the coils of one circuit, from brush to brush, instead of being adjacent to each other, are situated in different fields. For instance, the circuits through the armature in the position shown are, —

 $\longrightarrow \begin{array}{c} -\left\{ \begin{array}{ccc} 3 & 10 & 5 \\ 8 & 1 & 6 \end{array} \right\} + \\ -\left\{ \begin{array}{ccc} 2 & 7 & 12 \\ 9 & 4 & 11 \end{array} \right\} + \end{array} \longrightarrow$

It is important to note that when the armature has entered the position in which four coils are short-circuited, the short-circuiting of any coil occurs, not at any one brush, but through the pair of brushes of like polarity. This would enable sparking to be diminished by connecting the two positive brushes together through a suitable resistance (ohmic or inductive), and leading off to the load from the middle point of this resistance. The magnitude of the resistance, if ohmic, would be limited only by the permissible loss therein. High resistance leads to the commutator, and high-resistance brushes have been used with considerable success; but in both of these cases heat has to be developed in undesirable localities. But in the above method of connection, the insertion of this resistance externally to the brushes will not increase the heating of the machine. This resistance is also so located that it could be adjusted in experimental work, and the difference in sparking noted by having a short-circuiting switch shunted around the resistance.

Another advantage of this winding is that pointed out in the remarks on Fig. 6, that in cases where the shape of the frame necessitates somewhat unequal magnetic circuits, this connection will average up the unequal induction in the various coils, and thereby diminish the sparking that would otherwise occur.

CHAPTER II.

DOUBLE-WOUND GRAMME RINGS.

FIGURE 9 and the immediately following diagrams relate to a class of very great importance, which are known as double, triple, quadruple, etc., windings.

Very satisfactory results have been attained by the use of windings of this class. The most important advantage of the double winding is that the current is commutated at two different parts of the bearing surface of the brush; each independent volume of current being, therefore, only one-half of what it would be for a single winding. The importance of this feature has in practice been found to be very great.

Another important feature of this winding is that the successive commutator bars of one winding are not adjacent to each other, but alternate with the bars of the other winding; the two windings being put in parallel by the use of wide brushes. The result is that a section is very unlikely to be short-circuited by dirt or an arc. It also makes a very flexible winding, owing to the readiness with which any number of parallels may be arranged. Thus, in a six-pole field, we may have four, six, eight, etc., parallels.

It is necessary for a double winding that the brush should bear over a surface greater than the width of one segment (plus insulation); for a triple winding, greater than the width of two segments, etc.

In Fig. 9, which represents a two-circuit, doubly re-entrant, double-wound, simple gramme ring, the circuits through the armature are, —

After the armature has revolved through $\frac{360}{20 \times 2} = 9^\circ$, coils 3 and 8 will be short-circuited, and the circuits through the armature will become, —

	ſ 9	10	1	2	1.	
	17	6	5	4	ſŦ	
\rightarrow	[9'	10'	1'	2'	3'] ,	\rightarrow
	-18'	71	6'	5'	4' } +	

Thus it will be seen that there will be a lack of balance between the two windings. First they will be of equal length; after 9° revolution, one will have one less section in series between the brushes; 9° later they will be equal again; and after still another 9° the other winding will have the smaller number of turns. This lack of symmetry will be less apparent as the number of sections is increased, and becomes of very little importance with the large numbers of conductors employed in practical work.



Fig. 9 TWO CIRCUIT DOUBLE WINDING





FOUR CIRCUIT DOUBLE WINDING.

Figure 10 shows a similar winding in a four-pole field. The circuit through the armature in the position shown is, —

$-{16 \\ 15}$	17 14	18 13	19 12	20 11 \rightarrow +	
$-\left\{rac{16'}{15'} ight.$	17' 14'	18' 13'	19' 12'	20' + 11' +	
$-\left\{ \begin{array}{c} 6\\5 \end{array} ight.$	7 4	8 3	9 2		
$-\left\{\begin{array}{c}6'\\5'\end{array}\right.$	7' 4'	8' 3'	9' 2'	10' + 1' +	

After turning through $\frac{360}{40 \times 2} = 4.5^{\circ}$, coils 15', 20', 5', and 10' will be short-circuited, and the circuits through the armature will be, —



Here can be seen again the lack of symmetry noted in remarks on Fig. 9. A very useful winding is that shown in Fig. 11. It, also, is a four-circuit double winding. It is one of a class with very interesting properties. It differs from the double winding shown in Fig. 10, in that the two windings are components of one re-entrant system. Any one section is no longer exclusively an element of one of two windings, but changes from one winding to the other four times per revolution, being short-circuited at the neutral point for a brief period at the occurrence of each of these transfers. These features are secured by adding one section to the doubly re-entrant double winding shown in Fig. 10, and, as in that figure, making the connections, not between adjacent sections, but always by passing over one section. The number of sections being odd, it will be seen that after having progressed twice around the ring, all sections will have been passed through, and the winding will have arrived at the other terminal of the section from which it started.

Triple, quadruple, and higher orders of windings may be treated analogously.¹

The circuits through the armature in the position shown in Fig. 11 are, -



Coil 10 is, at this instant, short-circuited. An instant later coil 10 becomes active, and coil 2 becomes short-circuited. The circuits through the armature then become, —



The order in which the various coils will be short-circuited is 10, 2, 15, 7, 20, 12, 4, 17, etc., so that the 21 coils will each have been short-circuited once when the armature shall have revolved through $\frac{360^{\circ}}{4} = 90^{\circ}$. Therefore the angular interval between corresponding positions of two successive short circuits is $\frac{90^{\circ}}{21} = 4.28^{\circ}$.

¹ Such windings will be designated as singly re-entrant, to distinguish them from others, such as those of Figs. 9 and 10, which are doubly re-entrant.

20

CHAP. H.



Fig. 11 FOUR CIRCUIT DOUBLE WINDING



CHAP. II.

All of the windings so far described have as many circuits through the armature as there are pole pieces, and form a class by themselves known as multiple-circuit windings. Four-pole fields have usually been considered, but the modifications of the diagrams and text to apply them to larger numbers of poles, are obvious.

In general, the number of sets of brushes equals the number of poles and the number of eircuits through the armature. Different numbers of segments and brushes are due to modifications, and do not affect the underlying character of the windings as a class. Some of these modifications have been described. Others can be worked out as the occasion requires.

Too much importance cannot be attached to the general rule that interpolations and eross-connections are almost always very undesirable.

CHAPTER III.

TWO-CIRCUIT, SINGLE-WOUND, MULTIPOLAR RINGS.

THE next windings to be considered form a class which, independently of the number of poles, have only two circuits through the armature. These are known as two-circuit windings. Such windings possess the practical advantage that the number of conductors, as compared with multiple-circuit windings, is only $\frac{2}{N}$ as great, hence the space required for insulation is only $\frac{2}{N}$ as great as with the multiple-circuit windings, in consequence of which the diameter of the armature, or the depth of space occupied by the armature conductors, may be less than with the multiple-circuit windings, thereby diminishing the cost of material.

Further, on account of the lesser number of conductors, the cost of the labor of winding is correspondingly diminished.

In practice, the two-circuit gramme windings have been applied only to armatures of small output, under which condition lack of symmetry of the armature coils with respect to the points of commutation is not particularly objectionable. Only two sets of collecting brushes are necessary for the collection of current; in practice generally but two sets have been used.

In the "short-connection"¹ type of two-circuit gramme windings, the circuits from brush to brush consist of conductors influenced by all the poles, so that the electromotive forces generated in the two circuits are necessarily equal, a feature that may prove advantageous when the depth of air-gap is so small that any slight eccentricity of the armature affects the magnetic flux at the different poles.

In the "long-connection" type of two-circuit gramme winding, the two circuits from brush to brush consist of conductors influenced by only one-half of the poles, so that the electromotive forces generated in the two circuits are unequal, unless the sum of the lines at the poles of the same sign is equal to the sum of the lines at the poles of the opposite sign. In magnetic circuits of ordinarily good design this condition is fulfilled even though the fluxes at the different poles are unequal. So the winding is practically as good as the "short-connection" winding, and possesses certain other advantages stated in the text, that make its use preferable.

For armatures the outputs of which are so great that several sets of collecting brushes are required, these windings possess the same disadvantages as two-circuit drum windings, a discussion of which is to be found under that caption.

¹ Called "short-connection" type because coils in *adjacent* fields are connected together. This distinguishes it from the "long-connection" type, in which coils twice as far apart are connected together.

Figure 12 represents one of the most practicable two-circuit windings for multipolar-ring armatures. It may be designated as the long-connection type of the two-circuit gramme winding, and one of its chief advantages is, that no great differences of potential exist between adjacent coils.

In the figure is shown the case of a four-pole, two-circuit, single-wound, long-connection ring armature. In the position chosen, the circuits through the armature are, —

$$\longrightarrow - \left\{ \begin{array}{rrrr} 11 & 4 & 12 & 5 & 13 & 6 & 14 \\ 2 & 9 & 1 & 8 & 15 & 7 & - \end{array} \right\} + \longrightarrow$$

Coils 3 and 10, in series, are at this instant short-circuited by the negative brush. A little later, coils 7 and 15 will be short-circuited by the positive brush. When this occurs, the negative brush will bear upon the middle of a segment.

The number of commutator segments is equal to the number of coils, and must be odd for armatures with an even number of pairs of poles; but may be odd or even for armatures with an odd number of pairs of poles. The relation that must subsist in two-circuit, multipolar-ring, long-connection windings, between the number of coils (*) and the number of poles (n), is, —

$$s=\frac{n}{2}y\pm 1,$$

where y = pitch. (The pitch is the number of coils to be advanced through in arranging the end connections. In the diagram, for instance, the pitch y = 7, and the end of coil 1 is joined to the beginning of coil 1 + 7 = 8; the end of 8 to the beginning of 8 + 7 = 15; the end of 15 to the beginning of 15 + 7 = 22 (or 7), etc.) Mr. Gisbert Kapp has prepared the following table for two-circuit, multipolar-ring, long-connection windings by substituting numerical values for n in the above formula:—

Two-Circuit, Multipolar-Ring, Long-Connection Windings.

	. MACHINE HAS					
	4 poles	6 poles	8 poles	10 poles	12 poles	·14 poles
The number of coils must be equal to	$2y \pm 1$	$3y \pm 1$	$4y \pm 1$	$5y \pm 1$	$6y \pm 1$	$7y \pm 1$

For two-circuit, multipolar-ring machines with long-connection windings, y, the pitch, may be any integer. (Note that these conditions do not hold for drum windings.)

Mr. Kapp has also prepared the following table, showing the practicable choice of angular distances between brushes in these two-circuit, multipolar windings:--

NUMBER OF POLES.	А	NGULAR DIST	TANCE BETW	EEN BRUSHI	28.
2	180				
4	90				
6	60	180			
8	45	135			
10	36	108	180		
12	30	90	150		
14	25.7	77	128	180	
16	22.5	67.5	112	158	
18.	20.	60	100	140	180
20	18	54	90	126	162

The smaller possible angles, namely, 20° for 18 poles, and 18° for 20 poles, are in practice too small to be admissible, and are, therefore, not given in the table.

[CHAP. III.



TWO CIRCUIT, SINGLE WINDING.



TWO CIRCUIT, SINGLE WINDING.

Figure 13 represents a two-circuit, single-wound, longeonnection, ten-pole ring armature. Substituting in the formula for the number of coils

$$s = \frac{n}{2} y \pm 1$$

the pitch, y = 10, and the number of poles, n = 10, gives $s = \frac{10}{2} \cdot 10 \pm 1 = 51$ or 49. 51 coils are taken in this case. The end of coil 1 is joined to the beginning of coil 1+10=11; the end of 11 to the beginning of 21, etc.

The brushes are shown 180° apart, and at the position given the negative brush short-circuits the coils 9, 19, 29, 39, and 49. The circuits through the armature are, —

 $\begin{array}{c} 8-18-28-38-48-& 7-17-27-37-47-6-16-26-36-46-5-15-25-35-45-4-14-24 \\ 50-40-30-20-10-51-41-31-21-11-1-42-32-22-12-2-43-33-23-13-3-44-34 \end{array} \right)$

This diagram and table show very clearly that with an odd number of pairs of poles and an odd number of coils, an odd number of coils are short-circuited at one time, so that, as the total number of coils is odd, an even number is left to be divided between the two armature circuits, which are, therefore, equal. Referring back to Fig. 12, it will be seen that in the case of an even number of pairs of poles, an even number of coils are short-circuited, and as the total number of coils is necessarily odd, an odd number remains to be divided between the two armature circuits, so that these are necessarily unequal.



[СНАР. 111.

If, however, in Fig. 13 the brushes are put 108° apart instead of 180°, coil 24 would be taken from the circuit given in the upper line of numbers and put in the other circuit. There would then be 24 coils in one circuit, and 22 in the other, instead of 23 in both. With the large number of coils used in practice, however, these slight inequalities cause no trouble.

If y were chosen odd, 9 for instance, s would equal 46 or 44.

 $S = \frac{n}{2} \cdot y \pm 1 = \frac{10}{2} \cdot 9 \pm 1 = 46 \text{ or } 44.$

This is in accordance with the observation made above, that in the case of an odd number of pairs of poles the number of coils may be even. The diagram for this case is given in Fig. 14, where s=46, n=10, y=9. In the position shown, coils 8, 17, 26, 35, and 44 are short-circuited by the negative brush, and coils 31, 40, 3, 12, and 21 by the positive brush. The circuits through the armature are, —

giving, as in Fig. 13, two equal paths through the armature.



TWO CIRCUIT, SINGLE WINDING.



TWO CIRCUIT, SINGLE WINDING.

In Fig. 15 is given a winding that has been used in practice with considerable success, owing partly to the extreme regularity of all connections, and still more to the fact that it involves the use of twice as many commutator segments as coils. Only one coil in series is short-circuited at each brush, and the volts per segment are one-half what they would be in the unmodified long-connection winding. The number of coils to be used is, as in the unmodified winding, $s = \frac{n}{2} \cdot y \pm 1$. Thus, in Fig. 15, n=4, y=9, $s = \frac{4}{2} \cdot 9+1 = 19$. Coil 1 is connected to coil 10, etc.

It will also be noted that those segments $\begin{bmatrix} 360 \\ -\frac{n}{2} \end{bmatrix}^{\circ}$ from each

other are connected together. The number of segments = $\frac{n}{2} \cdot s$, of which $\frac{n}{2}$, at distances of $\left[\frac{360}{\frac{n}{2}}\right]^{\circ}$ from each other, are

connected together. If every other one of the radial connections from the coils to the commutator are discarded, the winding becomes once more the plain, long-connection, twocircuit, gramme winding.

At the position shown, coil 13 is short-circuited by the negative brush, and the circuits through the armature are, —

$$\longrightarrow - \left\{ \begin{array}{c} 3-12-2-11-1-10-19-9-18\\ 4-14-5-15-6-16-7-17-8 \end{array} \right\} + \longrightarrow$$

ARMATURE WINDINGS OF ELECTRIC MACHINES.

[CHAP. 111.

Figure 16 is an application of the same type of winding to a six-pole gramme ring. n=6, y=6, $s=\frac{n}{2}y\pm 1=\frac{6}{2}\cdot 6+1=19$. There are $19\times\frac{6}{2}=57$ segments. All segments distant from each other by $\frac{360}{n}=120^{\circ}$ should be connected together. Some of the cross-connections are shown inside the armature.

At the position shown, coil 12 is short-circuited by the positive brush. The circuits through the armature are -

$$\longrightarrow -\left\{\begin{array}{c}9-3-16-10-4-17-11-5-18\\15-2-8-14-1-7-13-19-6\end{array}\right\} + \longrightarrow$$

If the connections shown inside the commutator, together with one-third of the segments, had been omitted, there would have been an unequal distribution of potential about the commutator. Between two segments would be found a certain voltage, V, and between the next two 2V; then V again, etc.

If it should be desirable to diminish the number of commutator segments to one-half the number of coils, it may be done by the method of connection shown in Fig. 17, page 34, which will be recognized at once as the multipolar ring counterpart of the two-circuit winding as applied to multipolar drums. This winding will be referred to as a "short connection," two-circuit gramme winding. In the "long-connection" type, examples of which have just been given, connection has been made between coils situated in fields of like polarity. But in the "short-connection" type, connection is made between coils in adjacent fields. Both methods are feasible in ring windings, because the two ends of a coil located at a certain point of the periphery are accessible for connection at the commutator end if desired, but in drum windings only one end of a conductor located at a given point of the periphery is accessible at the commutator end, the other end of the conductor being necessarily connected across at the opposite end of the armature, and in consequence, also, must be connected over to a conductor in an adjacent field of unlike polarity, in order that the electromotive force, which is, say, from front to back in the first conductor, may add itself to that in the second conductor, which must therefore be from back to front; that is, the second conductor must be situated in a field of opposite polarity. Thus there are two sub-classes of two-circuit, multipolar ring windings, in the first of which (the "long-connection" winding) coils in fields of like polarity are connected in succession, and in the second of which, as in the two-circuit, multipolar drum winding, the conductors immediately succeeding each other are situated in fields of opposite polarity.

In this "short-connection" winding for two-circuit multipolar rings the formula for determining the proper number of coils, s, for any number of poles, n, is —

 $s = ny \pm 2,$

where y, the pitch, may equal any integer, odd or even.

In connecting up this "short-connection" type of winding the following additional rule should be borne in mind in the interpretation and application of the meaning of the pitch, y: The number of coils in this winding, being from the formula always even, if y is also even, it is necessary in connecting up to use as the pitch, alternately, (y-1) and (y+1) instead of always y. Otherwise, if the coils are numbered successively

32



TWO CIRCUIT, SINGLE WINDING.



Fig. 17 TWO CIRCUIT, SINGLE WINDING.

CHAP. III.]

TWO-CIRCUIT, SINGLE-WOUND, MULTIPOLAR RINGS.

from No. 1 on, the even-numbered coils would never be touched, if an odd-numbered conductor were started with, and *vice versa*. If y were used every time as the pitch, a double winding would be obtained. This case will be treated later.

It may also be well to note that (y-3) and (y+3) could be used alternately as the pitch. It is thought, however, that no advantages, and several disadvantages, would result from such a choice of pitches.

Figure 17 represents a two-circuit, single-wound, four-pole ring of the "short-connection" type just described.

$$n = 4, y = 8, s = ny \pm 2 = 4 \times 8 + 2 = 34.$$

This is the case referred to above, in which, s being even and also y, (y-1) and (y+1) must be used alternately as the pitch in connecting up. The sequence of connections will be seen in the figure to be 1, 1+7=8, 8+9=17, 17+7=24, etc.

Number of commutator segments $=\frac{3}{2}=17$.

In the position shown, coils 7, 14, 23, and 30, in series, are short-circuited at the negative brush, and the circuits through the armature are, —

There are 14 coils in one path and 16 in the other. A little later, coils 6, 33, 24, and 17, in series, will be short-circuited by the positive brush, and coils 7, 14, 23, and 30 will take their place, the circuits through the armature then becoming, —

 $\longrightarrow -\left\{\begin{array}{c} 7-14-23-30-5-12-21-28-3-10-19-26-1-8-3-3-20-19-26-1-8-3-3-22-15\\ 32-25-16-9-34-27-18-11-2-29-20-13-4-31-22-15\end{array}\right\}+$

A further inspection of the diagram will show the unsymmetrical arrangement of the short-circuited and adjacent coils, causing the induction in some coils to act in opposition to that in others with which it is in series. This is less marked with large numbers of coils.

The chief disadvantages of the "short-connection" winding are that adjacent coils have between them, periodically, the full E.M.F. of the armature, and that the end windings are complicated.



[CHAP. III.

Figure 18 represents another two-circuit, single-wound, "short-connection" gramme winding, in which $s = ny \pm 2$ $=4 \times 5 \pm 2 = 22$. In this case y, the pitch, is odd, and consequently the sequence of connections is 1, 1+5=6, 6+5=11, 11+5=16, etc., thus advancing each time by 5, and not, as in the case of Fig. 17, page 34, where y was even, alternately by (y+1) and (y-1). Corresponding ends of coils are connected together; thus, the end of 1 and the end of 6, the beginning of 6 and the beginning of 11, etc.

At the position shown, coils 5, 10, 15, and 20 are short-circuited by the negative brush, and the circuits through the armature are, -

 $\longrightarrow -\left\{ \begin{array}{c} 22-17-12-7-2-19-14-9 \\ 3-8-13-18-1-6-11-16-21-4 \end{array} \right\} + \longrightarrow$

The winding is subject to the disadvantages noted in connection with Fig. 17, page 34.

Instead of having the objectionable crossings at the terminals of the coils, as shown in Fig. 18, page 37, alternate coils should be wound right and left handedly. This would only be useful in cases where all the connecting is done at one end, which should be avoided when possible.



Fig. 18 TWO CIRCUIT, SINGLE WINDING.



Fig. 19 TWO CIRCUIT, SINGLE WINDING.

Instead of connecting together in pairs coils lying in fields of opposite polarity, as in Figs. 17 and 18, adjacent coils may be connected together as shown in Fig. 19, and these connected across to coils in the nearest field of like polarity. The number of commutator segments is equal to one-half of the number of coils. The inherent identity of this and the "long-connection" winding may be seen by doing away with the leads to the commutator segments, and substituting leads from the eleven points lettered a, b, c, d, etc. The result will be a simple "long-connection" gramme winding, with half as many coils of twice as many turns each.

Therefore, the best way of laying out such a winding is to apply the rules for the "long-connection" winding, and make the connections shown in Fig. 19, instead of those of the regular "long-connection" gramme winding.

This winding gives half as many commutator segments as coils.

In the position shown, coils 5, 14, 15, and 2 are shortcircuited by the positive brush, and the circuits through the armature are, -

 $\longrightarrow -\left\{ \begin{array}{c} 8-21-20-11-10-1-22-13-12-3\\ 9-18-19-6-7-16-17-4----- \right\} + \longrightarrow \right\}$



CHAPTER IV.

TWO-CIRCUIT, MULTIPLE-WOUND, MULTIPOLAR RINGS.

THE next class is that of the two-circuit, multiple-wound, long-connection ring windings. The general formula is, —

$$s = \frac{n}{2} \times y \pm m,$$

s = number of coils,

where

n = number of poles, y = pitch,

m = number of windings.

The "m" windings will consist of a number of independently re-entrant windings equal to the greatest common factor of "y" and "m."

Therefore, when it is desired that the "m" windings shall combine to form one re-entrant system, it will be necessary that the G.C.F. of "y" and "m" shall be made equal to 1.

Figure 20 represents a two-circuit, doubly re-entrant, double-wound ring armature.

$$s = 26,$$
 $n = 4,$ $m = 2.$
 $s = \frac{n}{2} \times y \pm m,$ $26 = \frac{4}{2} \times y + 2,$ $\therefore y = 12.$

Greatest common factor of y(12) and m(2) is 2. Therefore the winding will be doubly re-entrant.

At the position shown, coils 24 and 12, in series, are short-circuited by the negative brush. The circuits through the armature are, -

$$\rightarrow \left\{ \begin{array}{c} -\left\{ \frac{25-13-1-15-3-17-}{26-14-2-16-4-18-}\right\} + \\ -\left\{ \frac{10-22-8-20-6}{11-23-9-21-7-19-5}\right\} + \end{array} \right\} \rightarrow$$

ю



Fig. 20 TWO CIRCUIT, DOUBLE WINDING,



TWO CIRCUIT, DOUBLE WINDING.

Figure 21 represents a two-circuit, singly re-entrant, double-wound ring armature.

In this case y=11, n=4, and m=2. $s=\frac{4}{2} \times 11 \pm 2 = 20$ or 24. 24 coils are taken. G.C.F. of "y" and "m" being 1, the winding is singly re-entrant.

In the position given, coils 9 and 22 are short-circuited at the negative brush, and 4 and 15 at the positive. The circuits through the armature are, —

$$\longrightarrow \left\{ \begin{array}{c} -\left\{ \begin{array}{c} 20-7-18-5-16 & \\ 21-8-19-6-17 & \\ -\left\{ \begin{array}{c} 11-24-13-2 & \\ 10-23-12-1-14-3 \end{array} \right\} + \right\} \quad \longrightarrow \quad \end{array} \right.$$



Figure 22 represents another two-circuit, singly reentrant, double-wound ring armature.

$$m=2, n=6, y=7, s=\frac{n}{2}y \pm 2 = \frac{6}{2} \times 7 \pm 2 = 19 \text{ or } 23.$$

"y" and "m" being prime, the winding is singly reentrant.

At the position shown, coils 4, 11, and 18 are shortcircuited at the positive brush, and the circuits through the armature are: —

$$\longrightarrow \left\{ \begin{array}{c} -\left\{ \frac{15-22-6-13-20}{14-21-5-12-19} \right\} + \\ -\left\{ \frac{8-1-17-10-3-}{7-23-16-9-2-} \right\} + \end{array} \right\} \longrightarrow$$

Two two-circuit, singly re-entrant, triple windings for gramme rings are given below without diagrams: —

$$m=3, n=6, y=7, s=\frac{n}{2} \times y \pm 3 = \frac{6}{2} \times 7 + 3 = 24.$$

The connections would be, -

$$\begin{array}{r} 1-8-15-22-5-12-19-2-9-16-23-6-13-20-3-10-17-24-7-14-21\\ -4-11-18-1\end{array}$$

$$m=3, n=10, y=10, s=\frac{10}{2} \times 10 - 3 = 47.$$

 $\begin{array}{r} 1-11-21-31-41-4-14-24-34-44-7-17-27-37-47-10-20-30-40-3\\ -13-23-33-43-6-16-26-36-46-9-19-29-39-2-12-22-32-42\\ -5-15-25-35-45-8-18-28-38-1\end{array}$



Fig. 22 TWO CIRCUIT, DOUBLE WINDING.



Fig. 23 TWO CIRCUIT, TRIPLE WINDING.

CHAP. IV.]

TWO-CIRCUIT, MULTIPLE-WOUND, MULTIPOLAR RINGS.

Figure 23 represents a two-circuit, singly re-entrant, triple winding.

$$m=3, n=4, y=10, s=\frac{4}{2} \times 10 \pm 3 = 23.$$

"m" and "y" being prime, the winding is singly re-entrant.

In the position shown, coils 5 and 15, in series, are short-circuited by the positive brush. The circuits through the armature are, —

$$\rightarrow \left\{ \begin{array}{c} -\left\{ \begin{array}{c} 22-9-19-6-16\\ 21-8-18\\ 20-7-17\\ \end{array} \right\} + \\ -\left\{ \begin{array}{c} 12-2\\ 11-1-14-4\\ 10-23-13-3 \end{array} \right\} + \right\} \rightarrow$$

The extreme irregularity of the various circuits in multiple is not characteristic of the winding, but is merely due to the very small number of coils chosen. In practical cases it would be negligible.

From the formula and conditions of page 40, and from the examples just given, it will be seen that twocircuit, multiple-wound, ring windings may be divided into the three following cases: —

CASE I. — "y" and "m" are mutually prime. This gives a singly re-entrant winding of "m" multiple windings.

Illustration: $n = 4, y = 7, m = 4, s = \frac{4}{2} \times 7 + 4 = 18.$

Connections are, -1-8-15-4-11-18-7-14-3-10-17-6-13-2-9-16-5-12-1.

May be expressed symbolically as (000).

CASE II. - "y" a multiple of "m." This gives "m" independently re-entrant windings.

Illustration : ---

 $n=4, y=8, m=4, s=\frac{4}{2} \times 8 + 4 = 20.$

Connections are, -

1 - 9 - 17 - 5 - 13 - 1
2-10-18-6-14-2
3-11-19-7-15-3
4-12-20-8-16-4

May be expressed symbolically as $\bigcirc \bigcirc \bigcirc \bigcirc$.

CASE III. — "y" and "m" have common factors. This gives a number of independently re-entrant windings, equal to the greatest common factor of "y" and "m."

Illustration : --

$$n=4, y=6, m=4, s=\frac{4}{2}\times 6+4=16.$$

The result is a two-circuit, quadruple winding with two independently re-entrant windings, because 2 is the greatest common factor of "y" and "m."

The connections are, -

1-7-13-3-9-15-5-11-1 and 2-8-14-4-10-16-6-12-2

May be expressed symbolically as \bigcirc \bigcirc .

Case II. is really a special instance of Case III.

The above formula and controlling conditions will be found to hold for all numbers of poles, coils, pitches, and windings of the two-circuit, long-connection type of gramme-ring armature windings.



CHAP. IV.

Figure 24 is a two-circuit, singly re-entrant triple winding of the type described in connection with Figs. 15 and 16, which, it should be remembered, is only a modification of the long-connection type.

$$n=4, y=10, m=3, s=\frac{n}{2} \times y \pm m = \frac{4}{2} \times 10 + 3 = 23.$$

At the position shown, coil 21 is short-circuited at the negative brush, and coils 3 and 4 at the positive brush. The circuits through the armature are, —

$$\rightarrow \begin{cases} - \begin{cases} 8-18-5 \\ 9-19-6-16 \\ -20-7-17 \end{cases} + \\ - \begin{cases} 22-12-2-15 \\ -11-1-14 \\ -10-23-13 \end{cases} + \end{cases} \rightarrow$$

Figure 24 should be compared with Figs. 15 and 16.



Fig. 24 TWO CIRCUIT, TRIPLE WINDING.




CHAPTER V.

DRUM ARMATURE WINDINGS.

In drum windings, all connections from bar to bar must be made upon the rear and front ends exclusively, it not being practicable to bring connections through inside from back to front as is the case with rings. Consideration of this limitation will show that the two sides of any one coil must be situated in fields of opposite polarity, so that the electromotive forces, generated in the active conductors of a coil by their passage through their respective fields, shall be in the same direction.

In the case of a drum, it should also be noted that a coil is linked with the whole or nearly the whole flux from one pole piece, instead of, as in the ring armature, with only onehalf of the flux.

BIPOLAR DRUM WINDINGS.

The winding of bipolar armatures is much less simple in the case of drums than in that of rings, and it will therefore be necessary to give considerable attention to the various methods in which such windings may be carried out.

Figure 25 represents essentially the winding devised by von Hefner-Alteneck. It is used chiefly for small, smooth-core, wire-wound armatures, and the element of the winding, represented in the diagram by a pair of face conductors, and a back connection consists usually, in practice, of a coil of several turns, eomparable in some respects to the coil of the ring windings; but in the diagram only one turn per coil will be shown. This will also be advantageous, inasmuch as large, iron-clad, bar-wound, multipolar drum armatures are derived from, and diagrammatically are very analogous to, the wire-wound, smooth-core armatures now under consideration.

An examination of Fig. 25 shows that, starting from a commutator segment, the winding proceeds over the front end to conductor No. 1; down No. 1 over the back to conductor No. 8, which, it should be noted, is adjacent to the conductor diametrically opposite No. 1. From No. 8 the winding returns to the next commutator segment, and is then carried to conductor No. 3 (skipping No. 2, which will later be joined over the back to a conductor almost diametrically opposite to it), down No. 3, over the back to No. 10, etc. From this it is seen that the "pitch" on the back end is 7 and on the front end is -5.

In the position shown, the circuits through the armature are, ---

 $\longrightarrow \quad -\left\{ \begin{array}{c} 10- \begin{array}{c} 3-8- \begin{array}{c} 1- \begin{array}{c} 6-15 \\ 7-14-9-16-11- \end{array} \right\} + \quad \longrightarrow \quad$

The coil represented by the conductors 13 and 4 is short-circuited at the positive brush, and coil 12–5 at the negative brush.

The eustomary convention is adopted in the diagram, \otimes indicating a current from the observer into the paper, and \otimes a current up out of the surface of the paper toward the observer.

A serious fault of this winding is that large differences of potential exist between adjacent conductors (or, usually, groups of conductors). This would be of no importance with the small numbers of conductors represented in these diagrams, but in actual cases, large numbers of conductors are used, and are placed close together in order to waste no available space.



Fig. 25 TWO CIRCUIT, SINGLE WINDING.



Fig.'26 TWO CIRCUIT, SINGLE WINDING.

CHAP. V.]

Figure 26 gives the diagram of a winding discussed by Swinburne. Its characteristic feature is the use of a small pitch (in the figure the pitch at the back end is 11, and at the front end it is -9), whereby the turns consist of conductors separated by a much smaller angular distance than in the von Hefner-Alteneek winding.

An advantage of this winding is that there is much less crossing of the end connections than is the case where the pitch is taken larger. Thus the difficult question of insulation at the ends of the armature is greatly simplified.

Still further, it has been pointed out by Swinburne that the demagnetizing effect of the armature on the field is reduced, as may be seen from the fact that the currents in the conductors in the demagnetizing belt between the pole tips, namely, 23, 24, 25, and 26, and in 7, 8, 9, and 10, are alternately in opposite directions, and thus neutralize each other.

A serious disadvantage is that the short-circuited coils, 6-27 and 11-22, are considerably removed from the neutral line. This, together with the fact that the counter-electromotive forces present in several conductors of the eircuit between brushes detract from the volts per unit of length of armature wire, reduces to rather small limits the extent to which such connecting over short chords should be earried.

In the position shown, the circuits through the armature are, —



[CHAP. V.

In Fig. 27 it will be seen that the number of coils is odd (in the two preceding diagrams it was even), with the result that the two active sides of such coils may now be diametrically opposite.

This would not, however, usually be advisable, as it makes many more crossings at the ends, and therefore increases the difficulty of insulating.

Some advantage results from bringing the short-circuited coil (in the figure, coil 24–9 is short-circuited by the negative brush), exactly in the neutral line, this being, of course, only possible when the conductors forming its active sides are diametrically opposite.

The circuits through the armature in the position shown are, -

The pitch on the back end is 15, and on the front end it is -13.

Owing to the number of segments being odd, only one coil is short-circuited at once, unless wide brushes are used.



Fig. 27 TWO CIRCUIT, SINGLE WINDING.



-

Fig. 28 TWO CIRCUIT, SINGLE WINDING.

In Fig. 28 there is also an odd number of coils (and therefore an odd number of commutator segments). But instead of connecting over the back from No. 1 to No. 16 (the conductor diametrically opposite No. 1) as in Fig. 17, connection is made over the back from No. 1 to No. 14, then over the front to No 3, etc., the pitch at the back end being 13, and on the front end -11. It is, therefore, a mild form of the Swinburne chord winding, as described in connection with Fig. 26. The end connections are better distributed and have fewer crossings than was the case in Fig. 27, where diametrically opposite conductors were connected into coils.

In the position shown, coil 22-9 is short-circuited at the negative brush, and the circuits through the armature are, —



CHAP. V.

In Fig. 29 the winding is carried on over a still shorter chord, the pitch at the back end being 11 and at the front end -9.

It is very instructive to compare Figs. 27, 28, and 29, all of which have 30 face conductors (15 coils). But in Fig. 27 diametrically opposite conductors are connected over the back, the back pitch being 15. Figure 28 is a weak chord winding, the back pitch being 13. Figure 29 is a decided chord winding, the back pitch being 11. The points to be compared are the positions of the short-circuited conductors with reference to the neutral line; the amount of neutralizing of the effect of the demagnetizing belt between pole tips, and the comparative amount of crossing of connectors at the ends.

In Fig. 27 it was shown that diametrically opposite conductors could be connected into coils if the number of coils were chosen *odd*.

The same object may be attained with an *even* number of coils by winding them in two layers instead of in one layer, as has been the case in all the heretofore described bipolar drum armatures.

It should be again noted that the term "conductors" is used in these explanations, although "groups of conductors" could often be substituted therefor in small, smooth-core, wire-wound armatures.

Thus the set of "one-layer windings," just described, are those in which "conductors" or "groups of conductors" are, in the completed winding, arranged in one layer, although the individual wires of such a group may optionally occupy one or several layers. In the same way, the two-layer windings now to be described are those in which the completed winding consists of "conductors" or "groups of conductors" arranged in two layers, although the actual depth of individual wires may, when desirable, be greater than two.



Fig. 29 TWO CIRCUIT, SINGLE WINDING.











Fig. 30 a,b,c and d.

DRUM ARMATURE WINDINGS.

CHAP. V.]

In Fig. 30, diagrams a and b represent a single-layer bipolar drum winding with an odd number of coils, in which diametrically opposite conductors are connected together into coils. In diagram a the first half of the winding is carried out and proceeds from a commutator bar to conductor No. 1, to 8, to 3, to 10, to 5, to 12, to 7, to 14, and is then ready for the second half. It will be seen that at this stage only every other coil is connected up, and that only one-half of the commutator segments arc utilized. Diagram b shows the winding completed. This winding, which is of the type shown in Fig. 27, is given here for comparison with the two-layer winding shown in diagrams c and d. In Fig. c it will be seen that the first half is exactly the same as the first half of the one-layer winding (except that it contains eight conductors instead of seven), and at the completion of the first half all the conductors of the lower layer are connected up in the order 1-9-3-11-5-13-7-15, and only one-half of the commutator segments are connected in. The coils remaining for the second half, instead of lying between those of the first half, occupy an outer layer. Diagram d shows the completed winding, with all the coils and commutator segments utilized.



Figure 31 represents a two-layer winding with thirty-two conductors, with diametrically opposite conductors connected into coils over the back end.

These back-end connections are not shown, because they would interfere with the elearness of the diagram. The connections are 1-17-3-19-5-21, etc. In the position shown, coil 25-9 is short-circuited at the negative brush and 26-10 at the positive brush, and the eircuits through the armature are, —

 $\longrightarrow -\left\{ \begin{array}{c} 23-7-21-5-19-3-17-1-16-32-14-30-12-28\\ 11-27-13-29-15-31-18-2-20-4-22-6-24-8 \end{array} \right\} + \longrightarrow$

It will be seen from this table that maximum difference of potential exists between conductors lying directly over each other in different layers, such as 27 and 28, or 7 and 8. But *adjacent* conductors have only small differences of potential; therefore, the two layers should be carefully insulated from each other.

It is an advantage to have the conductors 25–9 and 26–10 of the two short-circuited coils all situated on one diameter, as they may therefore be brought diametrical, and therefore are capable of being short-circuited more nearly in the neutral position.

A disadvantage of the winding is that, one-half being wound exclusively in the lower layer and the other half in the upper, they have unequal lengths and different peripheral speeds, and in those recurring positions in which the two circuits through the armature consist respectively of the lower and the upper layer, the condition will be unbalanced.

In practice, however, it is frequently found expedient to use this connection because of the ease of winding, the inequality being made as small as possible. It will be shown later how this inequality may be obviated; the winding will be, however, less easy to execute.



Fig. 31 TWO CIRCUIT, SINGLE WINDING.



Fig. 32 TWO CIRCUIT, SINGLE WINDING

In Fig. 32 the winding is of the Swinburne type, being connected over the ends along a short chord. Thus, starting from a commutator segment, it passes down No. 1, over the back to No. 13, over the front to No. 3, and so on through 3, 15, 5, 17, 7, 19, 9, 21, 11, 23; but coming over the front from 23 it would naturally go to 13 of the lower layer. This, however, is already used, so the winding continues by No. 14, which is directly over No. 13 in the top layer, and then on through 25-16-27-18-29-20-31-22. From 22 it would naturally go to No. 1, but, as the winding is not yet completed, it must go instead to No. 2, which is directly over No. 1, and then proceed from 2 through 24-4-26-6-28-8-30-10-32-12, and then it closes on itself at No. 1. This winding is not at all difficult, because, although the lower layer is not entirely completed before beginning to wind the upper layer, yet in that part of the armature on which it is desired to wind the upper layer, the lower layer is entirely completed, and for quite a distance beyond, so that there would be no trouble in inserting the necessary insulation, etc.

In the position shown, coil 28–8 is short-circuited at the positive brush, and coil 23–11 at the negative brush. It is a disadvantage to have the short-circuited coils so far from the neutral line.

The circuits through the armature in the given position are, -

$$\longrightarrow - \left\{ \begin{array}{c} 21- \ 9-19- \ 7-17- \ 5-15- \ 3-13-1-12-32-10-30 \\ 14-25-16-27-18-29-20-31-22-2-24- \ 4-26- \ 6 \end{array} \right\} + \longrightarrow$$

It will be seen that in this armature there can be no position in which one layer belongs exclusively to one circuit and the other to the other circuit. Therefore the discrepancy in lengths and peripheral speeds of the two circuits through the armature will, at the most unfavorable moment, be less than when diametrically opposite conductors are connected into coils. The winding has, in common with all chord windings, the advantage of less crossings of the end connections. The diagram shows particularly well the absence of demagnetizing action in the zone of conductors between pole tips.

If, in Fig. 32, page 66, conductor No. 1 had been connected over the back to No. 15 instead of to No. 13, it would still have been a chord winding, but with somewhat less marked characteristics than that of Fig. 32. All the advantages and disadvantages would have been on a smaller scale.

CHAP. V.

Figure 33 represents a winding in which coils of the outer and inner layer are alternately connected. The rearend connections are not drawn, but are diametrical. Thus the series is 1-15-4-18-5-19-8-22-9-23-12-26-13-27-16-2-17-3-20-6-21-7-24-10-25-11-28-14-1. This makes both circuits through the armature of very nearly equal length and of very nearly equal average peripheral speed.

In the position shown, coil 21–7 is short-circuited by the positive, and 22–8 by the negative brush. The circuits through the armature are, —

 $\longrightarrow -\left\{ \begin{array}{c} 19- \ 5-18- \ 4-15- \ 1-14-28-11-25-10-24 \\ 9-23-12-26-13-27-16- \ 2-17- \ 3-20- \ 6 \end{array} \right\} + \quad \longrightarrow$

For this winding to be regular, the number of conductors must be an *odd* multiple of **4**.

Other bipolar drum windings have been proposed by Hering, Western Electric Company, and others, each of which possesses certain special advantages. It might be well especially to consult an article by Hering in "Electrician and Electrical Engineer," Vol. 4, 1885, p. 423, and Vol. 5, 1886, p. 84.



Fig. 33 TWO CIRCUIT, SINGLE WINDING.



Fig. 34 SIX CIRCUIT, SINGLE WINDING.

8/138

CHAPTER VI.

MULTIPLE-CIRCUIT, SINGLE-WOUND, MULTIPOLAR DRUMS.

FOR multiple-circuit, multipolar drums, the condition to be fulfilled to make the winding re-entrant is that there shall be an even number of bars. The pitch at one end of the armature must exceed that at the other end by 2 (for single windings), each of these pitches being odd. If n is the number of poles and C the number of face conductors, the average pitch should not differ much from $\frac{C}{n}$; for if it is much less, two successive conductors will often lie under the same pole piece, and their induced electromotive forces will be in opposition to each other, whereas they should be additive. If the average pitch is much greater than $\frac{C}{n}$, the cross-connections will be unnecessarily long, and the armature resistance and cost of copper unnecessarily high. Suppose a preliminary calculation for a single-layer, six-pole machine shows that about 49 conductors are required, it will be seen that $\frac{C}{n} = \frac{49}{6} = 8.17$. The two-end pitches must both be odd numbers, and must differ by 2. Therefore, take 7 and 9. The mean pitch is 8. The condition to be fulfilled by the total number of conductors is that it shall be an even number. Let it be 50.

This case is shown in Fig. 34. In this diagram the radial lines represent the face conductors. The connecting lines on the inside represent the end connections at the commutator end, and those on the outside represent the end connections at the pulley end. The brushes are placed inside the commutator for convenience.

At the position shown, the conductors without arrow-heads are short-circuited. The circuits through the armature are, --



The front-end pitch is y=9, and the back-end pitch is y=-7.

If the pitches had been taken 7 and -5 instead of 9 and -7, retaining the same number (50) of face conductors, the diagram given in Fig. 35 would have been the result. This, it will be seen, is an application of the ehord winding to a multipolar armature. The current in the conductors in the neutral zone is alternately in opposite directions, so that the demagnetizing action of the armature is small. The end connections are shorter, occupying less room and reducing the armature resistance and cost of copper. The short-circuited conductors are, however, at some distance from the neutral lines, and, although the electromotive forces in each pair will partly neutralize each other, it would be advisable, in cases where such chord windings are adopted, to have as great distances between pole tips as other circumstances permit.

In the given position, the short-circuited conductors are 4-49, 12-7, 20-15 28-23, 38-33, 46-41. The armature circuits are, --



The front-end pitch is y=7, and the back-end pitch y=-5.

If it should be considered desirable to have all the paths through the armature contain *exactly* the same number of conductors, then the number of face conductors should be chosen a multiple of the number of poles. But with a large number of conductors this would generally not be an important consideration.

In modern practice the conductors in large multipolar machines frequently consist of bars arranged in slots. The end connections then become strips arranged in two or more spiral layers at each end. If there were only one conductor per slot, two layers at each end would still be necessary, as it would be the same as if the lower conductors were brought up side of the upper conductors, and every other conductor would, therefore, as before, be connected over in an opposite direction from its neighbor.

For multiple-circuit, *single-wound* armatures there may be any *even* number of conductors per slot, and *any* number of slots. No new diagrams are necessary to show the cases of two or more conductors per slot, as Figs. 34 and 35 may be interpreted as having twenty-five slots and two conductors per slot, in which case odd-numbered conductors may be considered to belong to the upper layer, and even-numbered conductors to the lower layer. Connection is always made between odd and even numbered conductors, the pitch being always odd. The front-end and back-end pitches must differ by 2, and must have opposite signs.



Fig. 35 SIX CIRCUIT, SINGLE WINDING.



Fig. 36 SIX CIRCUIT, SINGLE WINDING.

Figure 36 represents a six-circuit, single-wound, drum winding with eighty conductors. The number of conductors is purposely taken large, so that a study of the diagram and winding table may show the magnitude of the differences of potential in neighboring conductors.

At the given position, conductors 75-6, 9-20, 21-32, 35-46, 49-60, and 61-72 are short-circuited at the brushes. The circuits through the armature are, —



An inspection of the above table will show that the full difference of potential exists at recurring intervals between each pair of sequential conductors, such as 7 and 8, or 47 and 48. In practice, such conductors will often consist of two bars lying one above the other in the same slot. This shows that such upper and lower layers in a slot should be carefully insulated. On the other hand, alternately sequential conductors, as 5 and 7, or 47 and 45, have between them only the small difference of potential of two conductors in series; so that, in practice, where such conductors usually belong both to the upper or both to the lower layer of the same slot, comparatively thin layers of insulation suffice. For instance, it is often the case in multiple-circuit windings that there are four conductors per slot, arranged two wide and two deep. This case would require that the horizontal layer of insulation between conductors should be much thicken than the vertical layer.

For this class of windings (multiple-circuit, single-wound drums) a formula is superfluous, and the following summary of conditions will suffice : —

There may be any even number of conductors, except that in ironclad windings the number of conductors must also be a multiple of the number of conductors per slot.

The front and back pitches must both be odd, and must differ by 2; therefore the average pitch is even.

The average pitch "y" should not be very different from $\frac{c}{n}$, where c = number of conductors, and n = number of poles. For chord windings, "y" should be smaller than $\frac{c}{n}$ by as great an amount as other conditions will permit.



CHAPTER VII.

MULTIPLE-CIRCUIT, MULTIPLE-WOUND, MULTIPOLAR DRUMS.

THE next windings to be considered are multiple-circuit, multiple-wound, multipolar drums.

The following rules control these windings : --

The number of conductors, C, must be an even number. The pitches must be odd. If y= frontend pitch, then -(y-2m)= back-end pitch, where m= number of windings (double, triple, quadruple, etc.).

These "m" windings may form one re-entrant winding, "m" independent re-entrant windings, or a number of re-entrant windings equal to some factor of "m," each of which re-entrant windings is composed of two or more components.

To determine the proper number of conductors for any of the above cases, the following rule should be observed : ---

If "m" equals the number of windings, and "C" equals the number of face conductors, then the number of independently re-entrant windings will be equal to the greatest common factor of $\frac{C}{2}$ and m.

For instance, if a quadruple winding has 28 conductors, then the greatest common factor of (m=4) and $\left(\frac{C}{2}=\frac{28}{2}=14\right)$ is 2, and the quadruple winding will consist of *two* independent double windings, each of the two being re-entrant. This may be represented symbolically as \bigcirc \bigcirc .

If C=24, and m=4, the greatest common factor of $\left(\frac{C}{2}=\frac{24}{2}=12\right)$ and (m=4) is 4, and the quadruple winding will be made up of *four* independent single windings. This may be represented symbolically as 0000.

If C=26 and m=4, the greatest common factor of $\left(\frac{C}{2}=\frac{26}{2}=13\right)$ and (m=4) is 1, and the quadruple winding will consist of *one* singly re-entrant quadruple winding. This may be represented symbolically as $\overline{(000)}$.

The above rule applies to any winding (double, triple, quadruple, etc.).

It is interesting to note that, for "multiple-*circuit*" windings, the rule for the number of multiple windings is independent of the number of poles and of the pitch.

The number of conductors, "C," the average pitch, "y," and the number of poles, "n," should be so chosen that $n \times y$ shall be somewhere nearly equal to C, being preferably a little smaller than C.



Figure 37 which, like Figs. 34 and 35, has six poles and fifty conductors, is a singly re-entrant triple winding. C=50; m=3. Greatest common factor of $\frac{C}{2}$ and m is 1. Therefore, by the preceding rule, the result is one singly re-entrant triple winding. The winding may be represented symbolically as 0.

The average pitch should be a little less than $\frac{C}{n} = \frac{50}{6} = 8.33$, and the forward and backward pitches must differ by (2m=6). Therefore the front end pitch is taken y=11, and the back-end pitch y=-5.

In the given position, conductors 49 and 4 are short-circuited at a negative brush, and 12 and 7 at a positive brush. The circuits through the armature are, -







Fig. 38 FOUR CIRCUIT, QUADRUPLE WINDING.

Figure 38 is a four-circuit, doubly re-entrant quadruple winding in which n=4, C=44, and m=4. The greatest common factor of $\frac{C}{2}$ and "m," *i.e.*, of 22 and 4, is 2; therefore there are two independent, singly re-entrant, double windings. The winding may be represented symbolically by $\bigcirc \bigcirc$. These two windings are represented on the diagram by full and dotted lines. The front-end pitch has been taken 13, and the back-end pitch -5, the difference being necessarily 2m=8. Inspection will show that the two windings are, —

 $\begin{array}{c} 1-14- \ 9-22-17-30-25-38-33-2-41-10-5-18-13-26-21-34-29-42-37-6-1\\ \text{and}\\ 3-16-11-24-19-32-27-40-35-4-43-12-7-20-15-28-23-36-31-44-39-8-3\\ \end{array}$

In the given position, 9-14 and 31-36 are short-circuited at the positive brushes. The eircuits through the armature are, ---



The extreme irregularity exhibited in the diagrams and tables of the multiple windings is due to the necessarily small numbers of conductors chosen. With the magnitudes taken in practical work, everything will be sufficiently regular.



Figure 39 is the same quadruple winding as Fig. 38, except that the pitches are taken 15 and -7 instead of 13 and -5. This was drawn to emphasize the fact that there is nothing absolute in the choice of the pitch in these multiple eircuit armatures, except that in the case of the *multiple windings*, the numerical differences between the forward and backward pitches must be equal to 2 m, where "m" is the number of windings. As before stated, the average pitch should not differ much from $\frac{C}{n}$, and should be somewhat less, rather than greater.

Figure 38, which partakes in a small degree of the nature of the short chord windings (as compared with Fig. 39), has a very much larger percentage of the conductors subjected to counter-induction than would be the case in actual practice with large numbers of conductors.

For instance, the average pitch might often be represented by some such number as 75. If it were to be a quadruple winding, the two pitches should differ by 2m or 8. Therefore the forward pitch would be taken 79, and the backward pitch -71, so that the order of the winding would be 1-80-9-88, etc., whereas in the case of small numbers of conductors, such as in Fig. 38, the order of the winding was 1-14-9-22-17-30, etc. It will be evident that the distinction between these two cases is, that with the larger number of conductors there are many forward and backward steps before the original loop is crossed, thus: --



But in the ease of the small number of conductors the loop is crossed almost at once, thus: ---



In other words, with multiple windings and small numbers of conductors, the numerical differences between the forward and backward pitches is a large percentage of the average pitch, whereas with the large numbers of conductors used in practice, it is a very small percentage of the average pitch.

The fact that irregularities are much exaggerated by the necessary choice of rather small numbers of conductors should be borne in mind in the study of these diagrams, particularly those of multiple windings.

If, instead of the quadruple windings consisting of two independent doubly re-entrant windings of Figs. 38 and 39, one singly re-entrant quadruple winding is desired, a number of conductors must be



FOUR CIRCUIT, QUADRUPLE WINDING.





SIX CIRCUIT, DOUBLE WINDING.

CHAP. VII.] MULTIPLE-CIRCUIT, MULTIPLE-WOUND, MULTIPOLAR DRUMS.

chosen such that $\frac{C}{2}$ and "m" (4) shall be mutually prime. Take C=42. Then $\frac{C}{2}=21$, and m=4, which are mutually prime. If the forward pitch is taken y=13, and the backward pitch y=-5, the winding will be, —

$$\begin{array}{l} 1-14-9-22-17-30-25-38-33-4-41-12+7-20-15-28-23-36-31-2-39-10-5-18-13-26\\ -21-34-29-42-37-8-3-16-11-24-19-32-27-40-35-6-1\end{array}$$

This would be represented symbolically as (000), and would be a singly re-entrant quadruple winding.

If four entirely independent windings are desired, $\frac{C}{2}$ and "m" must have 4 for their greatest common factor. Taking C=40, and making the front and back pitches respectively y=13 and y=-5, the winding would be, —

This could be represented symbolically as $\bigcirc \bigcirc \bigcirc \bigcirc \bigcirc$, and would be a quadruply re-entrant, quadruple winding.

In Fig. 40 is shown a six-circuit, singly re-entrant, double winding. C=50, n=6, m=2. The greatest common factor of $\frac{C}{2}$ and "m" being 1, the winding is singly re-entrant, and may be represented symbolically as \bigcirc .

The forward pitch is y=9, and the backward pitch is y=-5.

In the given position, conductors 49-4, 7-12, and 15-20 are short-eircuited. The eircuits through the armature are, —






CHAPTER VIII.

TWO-CIRCUIT, SINGLE-WOUND, DRUM ARMATURES.

THE "two-circuit" windings now to be considered are distinguished by the fact that the *pitch is always forward*, instead of alternately forward and backward, as in the "multiple-circuit" windings, just described.

The sequence of connections leads the winding from a certain bar opposite one pole piece to a bar similarly situated opposite the next pole piece, and so on, so that as many bars as pole pieces are passed through before another bar in the original field is reached. Such progression around the armature is continued until all the bars are connected in, and the winding returns on itself.

Two-circuit, drum windings, like the two-circuit, gramme-ring windings, have for a given voltage the fraction $\frac{2}{n}$ as many conductors as multiple-circuit windings, with the attendant advantages, stated for the two-circuit, gramme-ring windings. The advantages, that the circuits from brush to brush consist of conductors influenced by all the poles, are — when there is but one turn in each coil — the same as in the two-circuit, short-connection ring winding. When there are several turns in the coil, the advantages are subject to the same reservations as in the two-circuit, long-connection, ring winding. The advantages, due to such arrangements of the conductors, have been confined to machines of small electrical output. In machines of large electrical output, in which there are a number of sets of brushes of the same sign (otherwise the cost of the commutator is excessive), the advantages possible from equal currents in the circuits have been overbalanced by the increased sparking due to unequal division of the current between the different sets of brushes of the same sign.

An examination of the diagrams will show that in the two-circuit windings the drop in the armature, likewise the armature reaction, is independent of any manner in which the current may be subdivided among the different sets of brushes, but depends only upon the sum of the currents at all the sets of brushes of the same sign. There are, in the two-circuit windings, no features that tend to cause the current to subdivide equally between the different sets of brushes of the same sign, and, in consequence, if there is any difference in contact resistance between the different sets of brushes, or if the brushes are not set with the proper lead with respect to each other, there will be an unequal division of the current.

When there are as many sets of brushes as poles, the density at each pole must be the same, otherwise the position of the different sets of brushes must be shifted with respect to each other to correspond to the different intensities, the same as in the multiple-circuit windings.

In practice it has been found difficult to prevent the shifting of the current from one set of brushes to another. The possible excess of current at any one set of brushes increases with the number of sets; likewise the possibility of excessive sparking. For this reason the statement has been sometimes made that the disadvantages of the two-circuit windings increase with the number of poles.

ARMATURE WINDINGS OF ELECTRIC MACHINES.

CHAP. VIII.

From the above, it may be concluded that any change of the armature with respect to the poles will in the case of two-circuit windings be accompanied by shifting of the current between the different sets of brushes; therefore to maintain a proper subdivision of the current the armature must be maintained in one position, with respect to the poles, and with exactness, since there is no counter action in the armature to prevent the unequal division of the current.

In the case of multiple-circuit windings, it will be noted that the drop in any circuit, likewise the armature reaction in the field in which the current is generated, tends to prevent the excessive flow of current from the corresponding set of brushes. On account of these features, together with the consideration that when there are as many brushes as poles the two-circuit armatures require the same nicety of adjustment with respect to the poles as the multiple-circuit windings, the multiple-circuit windings are generally preferable, even when the additional cost is taken into consideration.

Denoting the number of face conductors by "C," the number of poles by "n," and the average pitch by "y," the formula controlling the two-circuit, single-wound, multipolar drum, is, —

$C = ny \pm 2.$

It is preferable to have the pitch "y" the same at the two ends, because the two sets of end connections will then be of the same length, but the choice of the number of conductors "C" for any particular case is less restricted (when the number of poles is greater than four) if the front and back pitches are permitted to differ by 2. Each pitch, must, moreover, be an odd number, as, in order that the winding may pass through *all* the conductors before returning upon itself, it must pass alternately through odd and even numbered conductors. Also when, as is usually the case, the bars occupy two layers, it is necessary to connect from a conductor of the upper to one of the lower layer so as to obviate interference in the positions of the spiral end connections. Where different pitches are used at the front and back ends, each being odd, the *average* "y" appearing in the formula will be even.

In Fig. 41 is given a two-circuit, single winding for a four-pole drum. The pitch is y=9 at both ends.

$$C = ny \pm 2 = 4 \times 9 \pm 2 = 34$$
 or 38.

Thirty-four conductors were taken. If it is necessary to have thirty-four conductors, it would be better to take the average "y" equal to eight, and then to use y=9 at one end and y=7 at the other. It is thus possible to shorten the end connections at the end at which the shorter pitch is used, and thus avoid using an unnecessary amount of copper. This will also make the armature resistance less, and will give more room for the end connections.



Fig. 41, TWO CIRCUIT, SINGLE WINDING.



Fig. 42 TWO CIRCUIT, SINGLE WINDING,

CHAP. VIII.]

TWO-CIRCUIT, SINGLE-WOUND, DRUM ARMATURES.

91

In Fig. 42 this has been done, the front-end pitch being y=9 as before, but the back-end pitch being y=7. The average pitch is y=8.

$$C = ny \pm 2 = 4 \times 8 \pm 2 = 30$$
 or 34.

Thirty-four conductors have been taken.

If thirty-eight conductors should be preferable to thirty-four, then the best arrangement would be to use y=9 at both ends.

$$C = n\eta \pm 2 = 4 \times 9 \pm 2 = 34$$
 or 38.

This case has not been drawn, but it would be the proper method for thirty-eight conductors, as the only other way would be to have a front-end pitch y=11 and a back-end pitch y=9, giving an average pitch y=10.

$$C = ny \pm 2 = 4 \times 10 \pm 2 = 38$$
 or 42.

This last choice, *i.e.* pitches of 9 and 11, would be undesirable, as the connections at the end with a pitch of 11 would be unnecessarily long. Therefore, as a general rule, the pitch should be chosen a little less than $\frac{U}{n}$, and when this would result in an even pitch, the pitch at one end may be made (y+1) and at the other end (y-1). Of course, the advantage of having both sets of end connections exactly equal might offset the small saving in material. This would have to be determined for the case in hand. Often, however, even where the same pitch is used at both ends, other considerations make it necessary to use two differently proportioned sets of connecting strips.

This matter of the possibility of using two different pitches, so that the "y" of the equation $C=ny\pm 2$ may be any integer, odd or even, is not so very important in the case of *four*-pole armatures, as it does not increase the range of choice of conductors. But for six, eight, and higher numbers of poles the introduction of even integers for "y" gives many more possible numbers of conductors than if it were necessary to be confined to odd integers.

Thus, for the case of six-pole windings, the formula $C = ny \pm 2$ becomes $C = 6y \pm 2$. If "y" is put successively equal to 10, 11, 12, 13, 14, and 15, the possible numbers of bars will become as follows:—

 $y=10 \quad C=60\pm 2=58 \text{ or } 62$ $y=11 \quad C=66\pm 2=64 \text{ or } 68$ $y=12 \quad C=72\pm 2=70 \text{ or } 74$ $y=13 \quad C=78\pm 2=76 \text{ or } 80$ $y=14 \quad C=84\pm 2=82 \text{ or } 86$ $y=15 \quad C=90\pm 2=88 \text{ or } 92.$

Thus it may be seen that if it were only permissible to use odd integers for "y," the possible conductors for this range would be limited to 64, 68, 76, 80, 88, and 92; but by using unequal pitches at the two ends, the average "y" becomes even, and the possible numbers of conductors to which the choice is limited is doubled. It is very important that this point should be borne in mind, as the rule often used for four-pole machines that C must equal number of poles times an odd number, plus or minus two, is sometimes mistakenly extended to larger numbers of poles, and a number of conductors is chosen either larger or smaller than is desired; whereas, if different pitches at the two ends had been used, a much more suitable choice might have been made.

ARMATURE WINDINGS OF ELECTRIC MACHINES.

Another limiting consideration is, that the numbers of conductors <u>per slot</u> is governed largely by the capacity and voltage of the machine, so that sometimes two, sometimes four, and in exceptional cases even six or eight, bars might be desired per slot, therefore, the total number of conductors "C" must be a multiple of 2, 4, 6, or 8, as the case may be. If, in the case of a six-pole armature, only two conductors per slot are desired, the pitch may be either odd or even; but it will be found that where four conductors per slot are wanted, and where, therefore, "C" must be a multiple of 4, that only the numbers of conductors obtained by making "y" an odd integer meet the requirement. And if six conductors per slot should be wanted (and it seldom would be, because the mechanical fitting of the connections would be so troublesome), neither the use of an odd nor of an even integer would (in the case of a six-pole armature) give a possible number for "C."

In the following illustrative diagrams it will not be necessary to take pains to show how many conductors there are per slot. They will be drawn with the conductors spaced at equal intervals, and one, two, four, or more, as desired, may be supposed to be brought together in a slot.

In Fig. 43 is given a diagram for a six-pole, two-circuit, single-wound, drum armature. The pitch is y=11 at both ends.

$$C = ny \pm 2 = 6 \times 11 \pm 2 = 66 \pm 2 = 64$$
 or 68.

Sixty-eight conductors were taken, and they could be arranged one, two, or four per slot, as other conditions might determine.

In the position shown, the positive brush short-circuits the group of conductors 5-62-51-40-29-18, all in series. The circuits through the armature are, —

An examination of the preceding table will show that immediately sequential conductors, such as 6 and 7, have between them, at recurring periods, the full difference of potential of the winding. But *alternately* sequential pairs of conductors, as 6 and 4, or 63 and 65, have between them only the difference of potential of "n" bars.

For the above analysis, only the two full-lined brushes were supposed to be in service. If, however, the four brushes shown by the dotted lines were added, the short-circuited bars would consist of groups of two each, in series between *different* brushes of like sign. In the given position, these groups would be 5-62, 51-40, and 29-18 at the positive brushes, and 63-52, 41-30, and 17-6 at the negative brushes. The circuits through the armature would be the same, with the exception that the bars short-circuited by the negative brushes would now disappear from the list. These six conductors, 6, 17, 63, 52, 41, 30, have been underlined in the table, and are marked on the diagram by small circles.





Fig. 44 TWO CIRCUIT, SINGLE WINDING.

In Fig. 44 is given a diagram for a two-circuit, six-pole armature. The back-end pitch is y=7, and the front-end

$C = ny \pm 2 = 6 \times 8 \pm 2 = 46$ or 50.

pitch is y=9. Therefore the average pitch is y=8.

Fifty conductors are taken. As in the preceding diagram, only the six conductors without arrow-heads are short-circuited when the two full-line brushes alone are active. But when all six brushes bear on the commutator, the conductors designated by small circles are also shortcircuited.



TWO-CIRCUIT WINDINGS WITH CROSS-CONNECTED COMMUTATORS.

Figures 45, 46, 47, and 48 are illustrative of a class of two-circuit windings that possess the distinctive feature that the number of coils may bear a relation to the number of poles not possible with the other two-circuit windings described. An examination of the diagrams will show that the different coils of a winding may be subdivided in groups, each group having either as many coils as there are pairs of poles, or half as many, these different groups being connected in series by a cross-connected commutator.

Figure 45 is an example of this class. As will be seen, it consists of an eight-pole drum armature, with fifty-six conductors connected up as a two-circuit, single winding.

The underlying principle is best understood by noting one "element" of the winding, such as the eight polar conductors drawn with very heavy lines. It starts from a certain commutator segment, and after proceeding under each of the eight pole pieces, it returns to the adjacent segment. It should be further observed that, unlike the heretofore described two-circuit drum armatures, the conductors of this element are separated from each other by an angular distance equal exactly to $\frac{360}{8} = 45^\circ$, instead of, as in the ordinary two-circuit drum windings, being separated by an angular distance a little greater or less than this.

$$C=56, n=8, y$$
 (the "pitch") $=\frac{56}{8}=7.$

It should be particularly noted that, with this winding, a number of conductors is used which is an exact multiple of the number of poles. This, of course, is not possible with the ordinary two-circuit drum windings, which are controlled by the formula —

$$C = ny \pm 2.$$

As will be seen from the diagram, this winding requires cross-connection of the commutator, but in many machines this disadvantage might be offset by the fact that, owing to the symmetrical arrangement of the conductors with reference to the pole pieces, the objectionable "selective commutation" of the ordinary type would probably be avoided.

To return to a study of the diagram, it will be seen that there are $\frac{C}{n} = \frac{56}{8} = 7$ sets of "elements" exactly the same as that above described, except that each is located at an angular distance of $\frac{360}{7}$ from the preceding one. To facilitate comprehension of the diagram, these seven "elements" have been drawn in with different styles of lines, and are readily distinguishable.

It is therefore obvious that, if it were not for the commutator cross-connections, the winding would consist of seven sets of eight conductors each, and that each such set has its two terminals at a pair of adjacent segments. These individual coils are put in the proper series relation between brushes by the commutator cross-connection. The resultant design is perfectly symmetrical.





Fig. 46

~

Figure 46 differs only in having forty-eight conductors, with the necessary consequence that, the pitch being even $(\frac{4_8}{8}=6)$, it has to be different at the front and back. It is seven at the commutator end, and five at the other end. This slight irregularity makes the wording of the description of Fig. 45 not absolutely applicable to this diagram, the chief difference being that, although every pair of successive conductors are exactly similarly located with respect to a pair of poles as every other pair, the same cannot be said of every individual conductor of an element, the distance between them being successively greater and less than $(\frac{360^\circ}{8})$.



Figure 47 represents a two-circuit single-winding, identical with Fig. 45, except that the connecting leads at the front end are twice as long.

This is used in some "form" windings, where the two ends of a coil are brought out in front at a point half-way between the two slots holding the wires of a coil. The long front connections would never be used in bar windings, where each face conductor of the diagram represents only one conductor, for it would be a waste of copper. Short leads such as those of Fig. 45 would, for such bar windings, always be used.

An "element" of the winding may be readily seen from the heavy lining in the diagram.

Windings of same type as Fig. 47 could be made corresponding to Fig. 46, as well as to Fig. 45. In fact, the underlying principle of this winding is identical with that of the type illustrated by Figs. 45 and 46.







Fig.48

Figure 48 represents a two-circuit single winding for an eight-pole machine, in which four conductors constitute an element. The number of conductors is here taken to be fifty-two. There are therefore $\frac{5.2}{4} = 13$ elements. It is a condition of this winding that the number of elements *must* be an odd number. From this it follows that the total number of conductors cannot be a multiple of the number of poles.

It serves, therefore, for numbers of conductors with which the previously described winding (where C is a multiple of n) could not be used. It probably, however, would not be so well balanced as in the case where C is a multiple of n. The commutator requires cross-connecting, as shown in the diagram. The cross-connections at the front end are of twice the usual length.



WENSTRÖM TWO-CIRCUIT, WIRE-WOUND ARMATURE.

Figure 49 represents a winding devised by Wenström to lessen the depth of the end windings of wire wound armatures.

The particular case represented by the diagram had thirty-five lozenge-shaped slots, each containing four conductors. For the sake of clearness only the connections of the wires between two adjacent commutator segments are shown, and no difficulty will be found in completing the winding, by continuing on through the remaining segments.

This method is, of course, only suitable for wire-wound armatures and like most such wire windings, it is difficult to repair.

It is to be noted that these armatures, which have been quite extensively used, were completely ironclad, there being no slot opening.



•

Fig. 49



TWO CIRCUIT, SINGLE WINDING.

CHAPTER IX.

INTERPOLATED COMMUTATOR SEGMENTS.

In Fig. 50 is given a two-eireuit single winding. n=6, y=13, $C=ny\pm 2=6\times 13\pm 2=76$ or 80. Eighty conductors have been taken. This would naturally give forty commutator segments. Suppose speed, strength of field, and active length of conductors to be of such magnitudes as to generate one volt per conductor. Noting that, as shown in the figure, twelve conductors are short-circuited, there will be $\frac{80-12}{2}=34$ active conductors in series between brushes. Therefore the total E.M.F. will be 34 volts. There would be (before interpolating) $\frac{40-6}{6}=5.67$ segments between every two neutral points of the commutator. Therefore there would be $\frac{34}{5.67}=6$ volts between every two adjacent segments.

Suppose this to be higher than is desired. It might then be proposed to double the number of segments by the method of cross-connecting shown in Fig. 50. This will increase the number of segments to eighty. Following the circuit through from the negative to the positive brush, the conductors have been labeled 1 volt, 2 volts, 3 volts, etc., adding one volt for each conductor. Taking the potential of the negative brush as zero, this gives the potential of each conductor. Following down from each conductor to its attached segments, they have been numbered in a corresponding manner; thus the four segments connected to the two bars at 20 volts potential have been marked 20, etc.

An examination of the figure will now make it apparent that proceeding from the neutral points (at zero potential) the voltage increases alternately by two and by four volts per segment, the average being three volts per segment. Therefore, although the average volts per segment have been decreased to one-half of what they were for forty segments, half of the segments have between them only one-third, and the remainder, two-thirds, of the original volts per segment Therefore, for a six-pole armature, the volts per segment cannot be halved by interpolation. And in order to reduce them to one-third throughout, it is not sufficient to cross-connect as shown in the figure, but it is necessary to triple the natural number of segments and cross-connect every three corresponding segments. This would be far from simple.

107



A fairly large number of conductors was taken in Fig. 50, in order to give a thorough explanation of the principles involved in interpolating segments. The further study of the subject can, however, be more satisfactorily carried on with small numbers of conductors.

In Fig. 51 is shown another two-circuit, single winding, with n=6, y=7, $C=ny\pm 2=6\times 7\pm 2=40$ or 44. Forty-four conductors are taken. Without interpolation, twenty-two segments would be used. Here $3\times 22=66$ segments are used. This is arrived at by connecting together every three corresponding commutator segments.

If, as in the preceding figure, only two segments had been cross-connected, the connections shown by the full lines would have sufficed. Crossconnecting every three corresponding segments involved the addition of the dotted line connections. This, as the diagram shows, doubles the total number of commutator cross-connections, and is therefore mechanically objectionable.

But the volts between bars are now everywhere equal instead of being alternately V and 2V as in Fig. 50. This may be seen by an examination of the numbers on the conductors and segments, which have been arranged according to the conventional method described.

Thus, proceeding from the segments under the negative brush, the voltage would increase regularly by two volts per segment up to the positive brush, so that whereas, in the former cases, the order was 2, 4, 8, 10, 14, 16, etc., it is now 2, 4, 6, 8, 10, 12, 14, 16, etc.





TWO CIRCUIT, SINGLE WINDING.

In Fig. 52 is given the diagram of a two-eircuit, singlewound, eight-pole armature with forty-two conductors. $C=ny\pm 2$; $8\times 5+2=42$. It is given to show that, with even numbers of pairs of poles, the number of commutator bars may be doubled by interpolation, and that the result will be to halve the volts between every two segments instead of producing the unsymmetrical result observed in the ease of an odd number of pairs of poles.

An examination of Fig. 52 will show that commutator segments 180° apart are cross-connected. The scheme of studying the relative potential of conductors and commutator segments is the same as that used in the case of the two preceding figures, and can be followed through without trouble. Some confusion may result from the fact that owing to the small number of conductors taken, the length of the two eircuits through the armature are quite unequal, one path consisting of twelve conductors, and the other of fourteen. As the positive neutral points where these two paths meet must be at the same potential, all the segments at these positions have been indicated as being at a potential of fourteen volts, so that the sequence of figures giving the potentials of the segments is, in four of the eight cases, 0, 4, 8, 12, 14; increasing regularly by four volts until the very end, where the increase is but two volts.

In the other four cases, for the same reason, the sequence is 0, 2, 6, 10, 14, showing the irregularity at the negative neutral points. . With the large number of conductors used in practice no misunderstanding would result.



With an even number of pairs of poles it is not necessary to be confined to using only twice the natural number of commutator segments. Thus in Fig. 53 is given the same eight-pole winding as in Fig. 52, with the exception that eighty-four segments are used instead of forty-two. The natural number of segments would be twenty-one.

As the conventions used in the previous descriptions are followed in mapping out the relative potentials of the various parts, no further explanations will be necessary.



TWO CIRCUIT, SINGLE WINDING.



CHAPTER X.

TWO-CIRCUIT, MULTIPLE-WOUND, DRUM ARMATURES.

THE next class is that of the two-circuit, multiple-wound, drum armature.

The general formula is : ---

where

 $C = ny \pm 2 m$,

C = number of face conductors, n = number of poles, y = average pitch, m = number of windings.

The "m" windings will consist of a number of *independently* re-entrant windings, equal to the greatest common factor of "y" and "m." Therefore, where it is desired that the "m" windings shall combine to form *one re-entrant* system, it will be necessary that the greatest common factor of "y" and "m" be made equal to 1.

Also, when "y" is an even integer, the pitch must be taken alternately as (y-1) and (y+1).

In Fig. 54 is reproduced a winding described by E. Arnold ("Die Ankerwicklungen der Gleichstrom-Dynamomaschinen," p. 70, Fig. 80), and by Dr. Kittler ("Handbuch der Elektrotechnik," 2d ed., p. 535, Fig. 403, b). It is classified by them as a four-circuit, single winding. They show four narrow brushes, and point out that the winding has the peculiarities that, in connecting up, the pitch is always taken forward, and that the short-circuiting of a coil occurs between opposite brushes of like polarity, instead of entirely at one brush, as is usually the case. They give no further instances of the application of this winding, except that Herr Arnold proposes for it the formula:—

 $C = n(y \pm 1),$

and adds that if $\frac{C}{2}$ and "y" have a common factor, a singly re-entrant winding is not obtained, several independently re-entrant windings being the result. He follows this statement with a diagram having C=28, n=4, and y=6. [28=4(6+1)],

which gives two independently re-entrant windings, and shows, as before, four points of commutation.

Returning to a consideration of Fig. 54, it may be seen that at the given position, conductors 5–12 and 21–28 are short circuited at the negative brushes, and 13–20 and 29–4 at the positive.

The circuits through the armature are, —

$$\rightarrow \begin{cases} -\begin{cases} 3-10-17-24-31-6\\ 30-23-16-9-2-27\\ -\begin{cases} 14-7-32-25-18-11\\ 19-26-1-8-15-22 \end{cases} + \\ 114 \end{cases} \rightarrow$$





Fig. 55 TWO CIRCUIT, DOUBLE WINDING.

Now in Fig. 55 will be found the very same winding as in Fig. 54, with the exception that two wide brushes are shown instead of four narrow ones. Short-circuiting of a coil now necessarily occurs at one brush, and a study of the winding shows that it is one of the singly re-entrant multiple-wound type, this particular one being a two-circuit, singly re-entrant, double winding.

At the position shown, conductors 7-14-21-28 are short-circuited at the negative brush, and 15-22-29-4 at the positive. The circuits through the armature are : —



It will be seen that, owing to the very small number of conductors, the winding is extremely irregular, but it will not be difficult to perceive that the nature of the course taken by the current through the armature remains essentially unaltered from that of Fig. 54, consisting, as there, of four paths with an average of six conductors in series per path. The current, however, enters the armature from one wide brush, which always spans more than one segment, and departs from a similar wide brush $\left(\frac{360}{n}\right)^{\circ}$ removed. But in the former case (Fig. 54), it entered two of the paths by one narrow negative brush, and the other two by another, situated $\left[\frac{360}{\frac{n}{2}}\right]^{\circ}$ distant.

It appears, therefore, conclusive that Fig. 54 is in all essential respects identical with a two-circuit, singly re-entrant, double winding, but this was probably not perceived by the above-mentioned authors: otherwise they would undoubtedly have extended the principle to higher orders of multiples and other numbers of poles. An *eight*-pole, two-circuit, singly re-entrant, triple winding (which would, of course, follow *six* paths through the conductors of the armature) would probably not have been considered possible, their conception of the winding apparently being that it was a multiple winding with as many paths through the conductors of the armature as the machine had poles. The formula and rules enunciated in this investigation follow naturally from the true conception of this winding, whereas the formula and condition stated by Herr Arnold may be seen, by a few attempts to apply it, to be entirely inadequate for the purpose of obtaining the necessary data for constructing such windings.



[CHAP. X.

The two preceding figures (54 and 55) were given for the purpose of showing in how far the two-eireuit, multiple windings have been understood in the past. The numbers of conductors were, however, entirely inadequate to fully illustrate the nature of the windings.

As this class promises to have a somewhat wide application, it is proposed to give a good many examples, selecting for the purpose various values of "C," "n," "y" and "m," and briefly analyzing each case on the basis of the rules given on page 114.

The symbolical representations heretofore used will be continued, thus :--

will represent a singly re-entrant single winding,
will represent a singly re-entrant double winding,
will represent a doubly re-entrant double winding,
will represent a singly re-entrant triple winding,
will represent a triply re-entrant triple winding,
will represent a singly re-entrant quadruple winding,
will represent a doubly re-entrant quadruple winding,

According to the above nomenelature, Fig. 40 would be a six-eircuit, singly re-entrant, double winding [O]; Fig. 37 would be a six-eircuit, singly re-entrant, triple winding [O]; and Fig. 38 a four-circuit, doubly re-entrant, quadruple winding [O]. The use of the middle expression, "singly, doubly, etc., re-entrant," is unavoidable for absolute definiteness, but it will in most cases be sufficiently definite to speak, for example, of a "six-eircuit, triple winding" and a "two-eircuit, quadruple winding," where absolute exactness would require them to be spoken of respectively as a "six-eircuit, singly re-entrant, triple winding" and a "two-eircuit, doubly re-entrant, quadruple winding."

Figure 56 is a four-pole, two-circuit, singly re-entrant, triple winding. It is represented symbolically thus: 00. n=4, and m=3. In order that it should be singly re-entrant, it was necessary for the greatest common factor of "m" and "y" to be 1. Therefore "y" was taken equal to 16.

$$C = ny \pm 2 m = 4 \times 16 \pm 2 \times 3 = 58 \text{ or } 70.$$

Seventy conductors have been taken, and "y" is alternately 15 and 17, it being, of course, impossible to use 16.

In the position shown, the conductors without arrowheads are short-circuited, and the eircuits through the armature are :----

 $\rightarrow - \begin{cases} 67-50-35-18-3-56-41-24 \\ 65-48-33-16-1-54-39-22 \\ 63-46-31-14-69-52-37-20-5-58-43-26 \\ 10-27-42-59-4-21-36-53-68-15 \\ 8-25-40-57-2-19-34-51-66-13 \\ 6-23-38-55-70-17-32-49-64-11 \\ \end{cases} + \rightarrow$





BRAR J

RSITY

r

JX



TWO CIRCUIT, TRIPLE WINDING.

Figure 57 is a four-pole, two-circuit, triply re-entrant, triple winding. It would be represented symbolically as $\bigcirc \bigcirc \bigcirc \bigcirc$. n=4, and m=3. In order that it should be triply re-entrant, it was necessary for the greatest common factor of "m" and "y" to be 3. Therefore "y" was taken equal to 15.

 $C = ny \pm 2m = 4 \times 15 \pm 2 \times 3 = 54$ or 66.

Sixty-six conductors have been taken. The three independently re-entrant windings have been shown by three different styles of lines.

In the position shown, the conductors without arrowheads are short-circuited, and the circuits through the armature are: —

_ {		+ -	
	$\begin{array}{cccccccccccccccccccccccccccccccccccc$		

It is interesting to compare this winding and table with the preceding, and to notice how very slightly they differ.



Figure 58 is a six-pole, two-circuit, singly re-entrant, double winding. It would be represented symbolically as \bigcirc . n=6, and m=2.

In order that it should be singly re-entrant, it was necessary for the greatest common factor of "m" and "y" to be 1. Therefore "y" was taken equal to 9.

 $C = ny \pm 2 m = 6 \times 9 \pm 2 \times 2 = 50 \text{ or } 58.$

Fifty-eight conductors have been taken.

In the position shown, the circuits through the armature are : --

 $\longrightarrow \ \ - \left\{ \begin{matrix} 57-48-39-30-21-12-3-52-43-34-25-16 \\ 55-46-37-28-19-10-1-50-41-32-23-14 \\ 6-15-24-33-42-51-2-11-20-29-38-47-56-7 \\ 4-13-22-31-40-49-58-9 \end{matrix} \right\} +$


TWO CIRCUIT, DOUBLE WINDING.



TWO CIRCUIT, DOUBLE WINDING.

125

Figure 59 is a six-pole, two-circuit, doubly re-entrant, double winding, the symbolical representation being $\bigcirc \bigcirc$. n=6, and m=2. In order that it should be doubly reentrant, it was necessary for the greatest common factor of "m" and "y" to be 2. Therefore "y" was taken equal to 8.

 $C = ny \pm 2m = 6 \times 8 \pm 2 \times 2 = 44$ or 52.

Fifty-two conductors have been taken, and "y" is alternately 7 and 9, it being, of eourse, impossible to use y=8.

In the position shown, the conductors without arrowheads are short-circuited, and the circuits through the armature are: --

 $\longrightarrow - \begin{cases} 51-44-35-28-19-12 \\ 49-42-33-26-17-10-1-46-37-30-21-14 \\ 6-13-22-29-38-45-2-9-18-25-34-41-50-5 \\ 4-11-20-27-36-43-52-7 \\ \end{cases} + \longrightarrow$

As frequently remarked in connection with other diagrams having small numbers of conductors, the very unequal lengths of the different paths through the armature is entirely caused by this choice of a small number of conductors, and would, to a large extent, disappear with all practicable numbers of conductors.

The two independently re-entrant windings are drawn respectively with full and with dotted lines.



Figure 60 is a six-pole, two-circuit, triply re-entrant, triple winding. It would be represented symbolically as $\bigcirc \bigcirc \bigcirc$. n=6, and m=3. In order that it should be triply re-entrant, it was necessary for the greatest common factor of "m" and "y" to be 3. Therefore "y" was taken equal to 9.

 $C = ny \pm 2m = 6 \times 9 \pm 2 \times 3 = 48$ or 60.

Sixty conductors have been taken.

The three independently re-entrant windings have been represented by three different styles of lines.

In the position shown, the circuits through the armature are : —

 $\rightarrow - \begin{cases} 59-50-41-32-23-14 \\ 57-48-39-30-21-12 \\ 55-46-37-28-19-10-1-52-43-34-25-16 \\ 6-15-24-33-42-51-60-9 \\ 4-13-22-31-40-49-58-7 \\ 2-11-20-29-38-47-56-5 \\ \end{cases} + -$



TWO GIRCUIT, TRIPLE WINDING.

and a second



TWO CIRCUIT, TRIPLE WINDING.,

Figure 61 is a six-pole, two-circuit, singly re-entrant, triple winding. It may be symbolically expressed as 0. n=6, and m=3. In order that it should be singly reentrant, it was necessary for the greatest common factor of "m" and "y" to be 1. Therefore "y" was taken equal to 8.

 $C = ny \pm 2m = 6 \times 8 \pm 2 \times 3 = 42$ or 54.

Fifty-four conductors have been taken, "y" is alternately 7 and 9, as it would, of course, be impossible to let y=8.

In the position shown, the circuits through the armature are : ---

	$ \begin{bmatrix} 53-46-37-30-21-14 \\ 51-44-35-28-19-12 \\ 49-42-33-26-17-10- \ 1-48-39-32-23-16 \end{bmatrix} $	
→ -·	8-15-24-31-40-47- 2-9- 6-13-22-29-38-45-54-7- 4-11-20-27-36-43-52-5-	}+ →

Figure 62 is a six-pole, two circuit, triply re-entrant, triple winding. It would be represented symbolically as $\bigcirc \bigcirc \bigcirc & n=6, m=3$. In order that it should be triply re-entrant, it was necessary for the greatest common factor of "y" and "m" to be 3. Therefore "y" was taken equal to 12.

 $C = ny \pm 2 m = 6 \times 12 \pm 2 \times 3 = 66$ or 78.

Seventy-eight conductors have been taken, and "y" is alternately 11 and 13, as it would not be possible to let "y"=12.

The three independently re entrant windings have been represented by three different styles of lines.

In the position shown, the short-eircuited conductors are those without arrow-heads. The eircuits through the armature are :---

_

 $\left\{ \begin{matrix} 75-64-51-40-27-16-3-70-57-46-33-22 \\ 73-62-49-38-25-14-1-68-55-44-31-20 \\ 71-60-47-36-23-12-77-66-53-42-29-18 \\ 10-21-34-45-58-69-4-15-28-39-52-63-76-9 \\ 8-19-32-43-56-67-2-13-26-37-50-61-74-7 \\ 6-17-30-41-54-65-78-11 \\ \end{matrix} \right.$



Fig. 62 TWO CIRCUIT, TRIPLE WINDING.



Fig. 63 TWO CIRCUIT, QUADRUPLE WINDING

Figure 63 is a six-pole, two-circuit, singly re-entrant, quadruple winding. Symbolically = $\bigcirc \bigcirc \bigcirc$. n=6, and m=4. In order that it should be singly re-entrant, it was necessary for the greatest common factor of "y" and "m" to be 1. Therefore "y" was taken equal to 7.

 $C = ny \pm 2$ $m = 6 \times 7 \pm 2 \times 4 = 34$ or 50.

Fifty conductors have been taken.

In the position shown, the circuits through the armature are : ---

	[1-44-37-30	
	49-42-35-28	
	47-40-33-26	
	45-38-31-24-17-10- 3-46-39-32	
- {		}+ -
	8-15-22-29-36-43-50-7-14-21	
	6-13-20-27-34-41-48- 5-12-19	
	4-11-18-25	
	2- 9-16-23	

Figure 64 is a six-pole, two-circuit, quadruply re-entrant, quadruple winding. It would be represented symbolically as $\bigcirc \bigcirc \bigcirc \bigcirc \bigcirc$. n=6, and m=4. In order that it should be quadruply re-entrant, it was necessary for the greatest common factor of "y" and "m" to be 4. Therefore "y" was taken equal to 8.

 $C = ny \pm 2m = 6 \times 8 \pm 2 \times 4 = 40$ or 56.

Fifty-six conductors have been taken. "y" is alternately 7 and 9, as it is obviously impossible to let y=8.

In the position shown, the circuits through the armature are : ---

	[55-48-39-32	1
	53-46-37-30	
	51-44-35-28-19-12- 3-52-43-36	
	49-42-33-26-17-10- 1-50-41-34	1246
> - ·		+
	8-15-24-31-40-47-56-7-16-23	
	6-13-22-29-38-45-54-5-14-21	
	4-11-20-27	North State
	2- 9-18-25	



Fig. 64. TWO CIRCUIT QUADRUPLE WINDING.





Fig. 65 TWO CIRCUIT, QUADRUPLE WINDING.

Figure 65 is a six-pole, two-circuit, doubly re-entrant, quadruple winding. It would be represented symbolically as $\bigcirc \bigcirc$. n=6, and m=4. In order that it should be doubly re-entrant, it was necessary for the greatest common factor of "y" and "m" to be 2. Therefore "y" was taken equal to 10.

 $C = ny \pm 2 m = 6 \times 10 \pm 2 \times 4 = 52$ or 68.

Sixty-eight conductors have been chosen. "y" is alternately 9 and 11, because its average value, being even, could not be used.

The two independently re-entrant windings have been represented respectively by light and by heavy lines.

In the position shown, the circuits through the armature are : --

	67-58-47-38 63-54-43-34-23-14- 3-62-51-42	
	65-56-45-36-25-16-5-64-53-44 61-52-41-32-21-12-1-60-49-40	
→ - ·	$ \begin{bmatrix} 10 - 19 - 30 - 39 - 50 - 59 - 2 - 11 - 22 - 31 \\ 6 - 15 - 26 - 35 - 46 - 55 - 66 - 7 - 18 - 27 \end{bmatrix} $	+ ->
	8-17-28-37-48-57-68- 9-20-29 4-13-24-33	

Figure 66 is a six-pole, two-circuit, quadruply re-entrant, quadruple winding $[\bigcirc \bigcirc \bigcirc \bigcirc \bigcirc \bigcirc]$. n=6, and m=4. In order that it should be quadruply re-entrant, it was necessary that the greatest common factor of "y" and "m" should be 4. Therefore "y" was taken equal to 12.

 $C = ny \pm 2$ $m = 6 \times 12 \pm 2 \times 4 = 64$ or 80.

Eighty conductors have been taken. "y" is alternately 11 and 13, its average value being even.

The four independently re-entrant windings have been represented by four varieties of lines.

In the position shown, the circuits through the armature are : --

 $\begin{array}{c} \checkmark \qquad - \left\{ \begin{matrix} 77-66-53-42-29-18-5-74-61-50\\ 75-64-51-40-27-16-3-72-59-48\\ 73-62-49-38-25-14-1-70-57-46\\ 71-60-47-36-23-12-79-68-55-44\\ 10-21-34-45-58-69-2-13-26-37\\ 8-19-32-43-56-67-80-11-24-35\\ 6-17-30-41-54-65-78-9-22-33\\ 4-15-28-39-52-63-76-7-20-31 \end{matrix} \right\} + \quad - \\ \end{array}$



Fig. 66 TWO CIRCUIT, QUADRUPLE WINDING.





TWO CIRCUIT, QUADRUPLE WINDING.

Figure 67 is a six-pole, two-circuit, quadruply re-entrant, quadruple winding. It would be represented symbolically as $\bigcirc \bigcirc \bigcirc \bigcirc \bigcirc$. n=6, and m=4. In order that it should be quadruply re-entrant, it was necessary that the greatest common factor of "y" and "m" should be 4. Therefore "y" was taken equal to 16.

 $C = ny \pm 2 m = 6 \times 16 \pm 2 \times 4 = 88$ or 104.

One hundred and four conductors have been taken. "y" is 17 at the front end, and 15 at the back end, thus averaging 16.

The four independently re-entrant windings have been represented by four different styles of lines.

In the position shown, the circuits through the armature are : --

[49-34-17- 2-89-74-57-42-25- 10-	
47-32-15-104-87-72-55-40-23- 8	
45-30-13-102-85-70-53-38-21- 6	
43-28-11-100-83-68-51-36-19- 4-91-76-59-44-27-12	
	+ -
64-79-96-7-24-39-56-71-88-103-16-31-48-63-80-95	
62-77-94- 5-22-37-54-69-86-101	
60-75-92- 3-20-35-52-67-84- 99	
58-73-90- 1-18-33-50-65-82- 97	



Figure 68 differs from Fig. 67 in the use of the negative instead of the positive sign in the formula. It is given to emphasize the fact that this has no influence on the type of winding. It requires, however, a greater length of copper for a given number of conductors. Like Fig. 67, it is a six-pole, two-circuit, quadruply re-entrant, quadruple winding. It would be represented symbolically as $\bigcirc \bigcirc \bigcirc \bigcirc$. n=6, and m=4. In order that it should be quadruply reentrant, it was necessary for the greatest common factor of "y" and "m" to be 4. Therefore "y" was taken equal to 16.

 $C = ny \pm 2 m = 6 \times 16 \pm 2 \times 4 = 88 \text{ or } 104.$

Eighty-eight conductors have been taken. "y" is 17 at the front, and 15 at the back end.

The four independently re-entrant windings have been represented by different kinds of lines.

In the position shown, the circuits through the armature are: --





TWO CIRCUIT, QUADRUPLE WINDING.



Fig. 69

TWO CIRCUIT, SEXTUPLE WINDING.

The next four diagrams (Figs. 69, 70, 71, 72) form a group of sextuple windings. It is thought that an examination of this group will bring out very clearly the method of applying and the interpretation of the rules concerning two-circuit, multiple windings. The following table will be of assistance in studying them : -

Figure.	n	y	m	C	G.C.F. of m and y .	Name of Winding.	Symbol.
69 70 71 72	6 6 6 6	9 10 11 12	6 6 6 6	$ \begin{array}{r} 66 \\ 72 \\ 78 \\ 84 \end{array} $	$\begin{array}{c}3\\2\\1\\6\end{array}$	Two-circuit, triply re-entrant, sextuple winding. Two-circuit, doubly re-entrant, sextuple winding. Two-circuit, singly re-entrant, sextuple winding. Two-circuit, sextuply re-entrant, sextuple winding.	000 @@ 000000

Figure 69 is a six-pole, two-eircuit, triply re-entrant, sextuple winding. It would be symbolically represented as $\bigotimes \bigotimes \bigotimes$. n=6, and m=6. In order that it should be triply re-entrant, it was necessary that the greatest common factor of "m" and "y" should be 3. Therefore "y" was taken equal to 9.

$$C = ny \pm 2m = 6 \times 9 \pm 2 \times 6 = 42$$
 or 66.

Sixty-six conductors were taken. The three independently re-entrant windings have been represented respectively by light, heavy, and broken lines.

In the position shown, the circuits through the armature are : --

1	[59-50-41-32-23-14- 5-62-53-44]
	61-52-43-34
8	63-54-45-36
	65-56-47-38
	1-58-49-40
	3-60-51-42
{	66_ 9_18_27
	2-11-20-29
	4-13-22-31
	6-15-24-33
	8-17-26-35
	10-19-28-37-46-55-64-7-16-25



Figure 70 is a six-pole, two-circuit, doubly re-entrant, sextuple winding. It would be represented symbolically as 00 00. n = 6, and m = 6. In order that it should be doubly re-entrant, it was necessary that the greatest common factor of "m" and "y" should be 2. Therefore "y" was taken equal to 10.

 $C = ny \pm 2 m = 6 \times 10 \pm 2 \times 6 = 48$ or 72.

Seventy-two conductors have been taken. The two independently re-entrant windings have been represented respectively by full and dotted lines.

In the given position, the circuits through the armature are: --

[63-54-43-34-23-14-3-66-55-46]	
65-56-45-36-25-16- 5-68-57-48	
67-58-47-38	
69-60-49-40	
71-62-51-42	
1-64-53-44	
 	+
2-11-22-31	
4-13-24-33	
6-15-26-35	
8-17-28-37	
10-19-30-39	
12-21-32-41-52-61-72- 9-20-29	



TWO CIRCUIT, SEXTUPLE WINDING.



TWO CIRCUIT, SEXTUPLE WINDING.

Figure 71 is a six-pole, two-circuit, singly re-entrant, sextuple winding. It would be represented symbolically as $\boxed{00000}$. n=6, and m=6. In order that it should be singly re-entrant, it was necessary that the greatest common factor of "m" and "y" should be 1. Therefore "y" was taken equal to 11.

 $C = ny \pm 2 m = 6 \times 11 \pm 2 \times 6 = 54$ or 78.

Seventy-eight conductors have been chosen.

In the given position, the circuits through the armature are : --

69-58-47-36-25-14- 3-70-59-48	}	
71-60-49-38-27-16- 5-72-61-50		
73-62-51-40	-	
75-64-53-42		
77-66-55-44		
1-68-57-46		
 40 00 01 15 54 45 50 44 00 00	} + -	
12 - 23 - 34 - 45 - 56 - 67 - 78 - 11 - 22 - 33		
10-21-32-43-54-65-76- 9-20-31		
8-19-30-41		
6-17-28-39		
4-15-26-37		
2-13-24-35		

 $C = ny \pm 2m = 6 \times 12 \pm 2 \times 6 = 60$ or 84.

Eighty-four conductors have been taken.

The six independently re-entrant windings are represented respectively by different styles of lines. "y," of course, is taken alternately 11 and 13.

In the given position, the circuits through the armature are : —





TWO CIRCUIT, SEXTUPLE WINDING.



Fig. 73 TWO CIRCUIT, DOUBLE WINDING.

153

Figure 73 is an eight-pole, two-circuit, doubly re-entrant, double winding. It would be represented symbolically as $\bigcirc \bigcirc$. n=8, and m=2. In order that it should be doubly re-entrant, it was necessary that the greatest common factor of "m" and "y" should be 2. Therefore "y" was taken equal to 10.

$$C = ny \pm 2m = 8 \times 10 \pm 2 \times 2 = 76 \text{ or } 84.$$

Eighty-four conductors have been taken.

The two independently re-entrant windings are represented respectively by full and dotted lines. "y" is taken alternately 11 and 9, the average pitch being 10.

In the given position, the circuits through the armature are: -

Figure 74 is an eight-pole, two-circuit, singly re-entrant, double winding. It would be represented symbolically as \bigcirc . n=3, and m=2. In order that it should be singly re-entrant, it was necessary that the greatest common factor of "y" and "m" should be 1. Therefore "y" was taken equal to 11.

 $C = ny \pm 2m = 8 \times 11 \pm 2 \times 2 = 84$ or 92.

Eighty-four conductors have been taken just as in the preceding figure. In the given position, the circuits through the armature are : —

 $\begin{array}{l} 8-19-30-41-52-63-74-1-12-23-34-45-56-67- \\ 6-17-28-39-50-61-72-83-10-21-32-43-54-65-76-3-14-25-36-47-58-69- \\ 81-70-59-48-37-26-15-4-77-66-55-44-33-22-11-84-73-62-51-40-29-18-7-80-20-20-20-20-20-20-20-20-20-20-20-$



Fig. 74 TWO CIRCUIT, DOUBLE WINDING.





Fig. 75 TWO CIRCUIT, DOUBLE WINDING.

Figure 74 was obtained by using the negative sign in the formula —

$C = ny \pm 2 m$.

This is, as has been pointed out, rather wasteful of copper, and was only done to demonstrate the fact that in certain cases with a given number of conductors, either a singly or a doubly re-eutrant, double winding may be used.

In Fig. 75, the positive sign was used. It will, however, not be necessary to analyze it, it not being materially different from Fig. 74.

Numerous interesting deductions concerning two-circuit, multiple-wound, drum armatures may be made from the data contained in the tables in Chapter XVIII.

CHAPTER XI.

THE SAYERS WINDING.

THE armature coils of dynamos have, in addition to their function of establishing the electromotive force required external to the armature, the function of setting up in the arc of commutation an electromotive force to reverse the current in them as they successively pass the collecting brushes (by arc of commutation is meant the arc in which the current in the armature coils is reversed, the extent of this arc being determined by the length of the arc of contact of the collecting brushes). In the ordinary methods of armature winding the electromotive force for reversing the current in the coils is obtained by giving the collecting brushes an angular lead, the amount of which depends upon the distribution of the magnetic flux in the air gap, the coefficient of self-induction of the armature coils when in the arc of commutation, and the rate of change of the current in the coils, while the current is being reversed. In generators this angular lead is in such direction that the magnetomotive force of the armature is opposed to the magnetomotive force of the field magnets to an extent proportional to the angle of lead, in consequence of which the reversing field becomes of diminished intensity for an increase of current in the armature, when it needs to be increased.

Mr. Sayers, of Glasgow, has patented a winding in which the commutation of the current in the main armature coils is effected by an additional set of coils which may be termed commutating coils. These coils are applicable to any form of armature winding suitable for commutating machines. One of these coils is connected between each commutator bar and the connections joining the main armature coils in series with each other. These commutating coils are located on the periphery of the armature in such a position with respect to the main coils that the magnetomotive force of the main coils tends with increasing current to increase the flux through them, and further so that the magnetomotive force of the armature acts with the magnetomotive force of the field magnets instead of against it as in ordinary dynamos. It is possible, therefore, through a certain range of output to sparklessly operate a generator at constant voltage without changing the lead of the brushes or the excitation of the field magnets. It may be noted that when one of the main coils is short-circuited by the collecting brushes it is through two of these commutating coils, and the electromotive force from these coils effective for reversing the current in the main coil is the excess of the electromotive force generated in the leading coil over that in the following coil. The position, then, of the reversing field, if effective, is fixed as to angular extent between very narrow limits. It does not appear to the writers that the reversing field can be so localized for great changes of current in the armature as one might infer from reading the discussion of Mr. Sayers' paper at the Institution of Electrical Engineers. (See Vol. XXII., pages 377-441, Journal Ins. Elect. Engrs., London). Within certain limits, however, it appears that the magnetomotive force of the armature may be utilized in creating proper strength of reversing field.

This method, as applied to a bi-polar drum winding, is illustrated in Fig. 76. It will be seen to consist of a regular drum winding, with the difference that the connections from the winding to the commutator segments,
CHAP. XI.]

THE SAYERS WINDING.

instead of consisting of short leads, consist of auxiliary force conductors which pass from the winding, backward, a short distance against the direction of rotation, and then parallel to the regular face conductors to the back of the armature. The conductor then passes forward in the direction of rotation, and again crossing the armature, is carried to the commutator segment.

In the diagram, the current in the coil A^2 has just been reversed. The coil A^1 is, by the two adjacent commutator segments under the brush, short-circuited while its main conductors are still moving through intense fields, tending to maintain the current in its original direction. But this short circuit contains, in series with the main coil, the two connections to the commutator segments, both of which are so linked with the magnetic flux from the pole piece, that electromotive forces are induced. Of the electromotive forces induced in the two commutator loops, that in the loop drawn in the figure is added to that of the short-cireuited main coil, but this loop is farther out of the magnetic field than the remaining loop (not drawn) of the short-circuited section. This latter loop, leading from the segment next adjacent on the left of that shown at



Fig. 76.

C, being well under the pole pieces, has induced in it a strong electromotive force, which opposes that in the rest of the short-circuited section, and enables a current to be generated in the direction of that in the half of the armature circuit of which it is soon to become a part.

In such a drum winding, Mr. Sayers refers to these commutator connections as "reverser bars." As they carry the current only during the short time that their corresponding sections are passing under the brushes, they may be of much smaller cross-section than the main conductors.

It will be seen from the above description that the winding is particularly adapted for use with ironclad armatures with very small air gaps, for the effectiveness of the arrangement is largely dependent upon the differential inductive action upon two successive reverser bars, and the more abrupt the demarcation of the magnetic flux, the greater will be this differential effect.

It should be clearly understood that this winding is equally applicable to rings, discs, and other types of armature.





PART II.

WINDINGS FOR ALTERNATING-CURRENT DYNAMOS AND MOTORS.





CHAPTER XII.

ALTERNATING-CURRENT WINDINGS.

In general, any of the continuous-current armature windings may be employed for alternating-current work, but the special considerations leading to the use of alternating currents generally make it necessary to abandon the styles of winding best suited to continuous-current work, and to use windings specially adapted to the conditions of alternating-current practice.

Attention should be called to the fact that all the re-entrant (or closed circuit) continuous-current windings must necessarily be two-circuit or multiple-circuit windings, while alternating-current armatures may, and almost always do from practical considerations, have one-circuit windings, *i.e.* one circuit per phase. From this it follows that any continuous-current winding may be used for alternating-current work, but an alternating-current winding cannot generally be used for continuous-current work. In other words, the windings of alternating-current armatures are essentially non-re-entrant (or open circuit) windings, with the exception of the ring-connected polyphase windings, which are re-entrant (or closed circuit) windings. These latter are, therefore, the only windings which are applicable to alternating-continuous current, commutating machines.

Usually, high voltages are desired, and in such cases windings are generally adopted in which heavily insulated coils are imbedded in slots in the armature surface. Often, for single-phase alternators, one slot or coil per pole piece is used, as this permits of the most effective disposition of the armature conductors as regards generation of electromotive force. If more slots or coils are used, or, in the case of face windings, if the conductors are more evenly distributed over the face of the armature, the electromotive forces generated in the various conductors are in different phases, and the total electromotive force is less than the algebraic sum of the effective electromotive forces induced in each conductor. But, on the other hand, the subdivision of the conductors in several slots or angular positions per pole, or, in the case of face windings, their more uniform distribution over the peripheral surface, decreases the self-induction of the windings with its attendant disadvantages. It also utilizes more completely the available space and tends to bring about a better distribution of the necessary heating of core and conductors. Therefore, in cases where the voltage and the corresponding necessary insulation "permit, the conductors are sometimes spread out to a greater or less extent from the elementary groups necessary in cases where very high potentials are used.

Windings in which such a subdivision is adopted, will be referred to as having a multi-coil construction, as distinguished from the form in which the conductors are assembled in one group per pole piece, which latter will be called uni-coil windings.

The terms uni- and multi-*slot* have been applied to alternating-current ironclad armatures, but the modified nomenclature described in the preceding paragraph will be preferable, in that it does not distinguish between armatures where the groups are arranged on the periphery, and those in which the groups are imbedded in slots. A little consideration will show the advisability of this nomenclature, as it will often permit one description to suffice for a winding which may be used either for ironclad or smooth-core construction. It will be seen later, that in most *multiphase windings*, multi-coil construction involves only very little sacrifice of electromotive force for a given total length of armature conductor, and in good designs is generally adopted to as great an extent as proper space allowance for the insulation will permit.

Often in alternating current installations, step-up or step-down transformers, or both, are used, and in such cases the other extreme is approached, and the apparatus is built for very low voltages. This permits the use of very small space for insulation; and conductors of large cross-section, often arranged with only one conductor per group, are used. Here the multi-coil construction is less difficult, although still attended to some extent with the disadvantage of obtaining less than the maximum possible voltage per unit length of armature conductor.

Examples of windings adapted respectively to both of the above extremes will be given in the following chapters.

It will now be readily understood that the ordinary continuous-current windings are not, in the great majority of cases, adaptable to the work to be done. They should, however, always be kept in mind, and will often be found to work in nicely in special cases.

A class of apparatus, best termed alternating continuous-current, commutating machines, is now being found of much value in various ways. They are in a general way used for feeding continuous-current circuits, from single-phase or multiphase circuits (or *vice versa*), and also sometimes for feeding alternating circuits of one class (for example, single- or quarter-phase) from those of another (say three-phase). This type of armature may usually be best laid out by employing regular continuous-current windings and tapping them off in the proper manner. Examples will be given.

A wide variety of styles of armature construction have been employed in alternating-current machinery. Rings, drums (both ironclad and smooth-core), discs, and very many other types have been successfully built. Iron cores are used by some makers, and carefully avoided by others. Internal and external rotating parts have each found advocates. This great variety renders detailed treatment difficult, and in the following discussion it has been generally assumed that the windings are laid on the periphery of a drum, either on the surface, or imbedded in slots, and that the necessary connections are made at the ends of the armature. These peripheral conductors are represented diagrammatically by radial lines, and the end connections by crooked lines. Thus, re-entrant polygons drawn with heavy lines may be taken to represent coils of the desired number of turns, the lighter lines representing the connections of these coils to each other.

In the case of bar windings, no difficulty will be found in understanding the diagrams, as they correspond quite nearly to the continuous-current windings. Small, heavy circles in the middle of the diagram represent collector rings. If a winding is desired, for a disc or some other type, the diagrams will generally be found amply suggestive. Pancake coils and other types of windings, not specifically described, may be readily planned by slight modifications of the diagrams.

No examples have been given of gramme-ring alternating-current windings, as these may be found in text books, and are so easily understood as to require no discussion.

Before concluding these general considerations, it is desirable to emphasize the following points regarding the relative merits of uni- and multi-coil construction : —

With a given number of conductors arranged in a multi-coil winding, less terminal voltage will be obtained at no load than would be the case if they had been arranged in a uni-coil winding, and the discrepancy will be greater in proportion to the number of coils into which the conductors per pole piece are subdivided, assuming that the spacing of the groups of conductors is uniform over the entire periphery.

Thus, if the terminal voltage at no load be taken as 1 for a uni-coil construction, it will, for the same total number of conductors, be .707 for a two-coil, .667 for a three-coil, .654 for a four-coil, etc.

But when the machine is loaded, the current in the armature causes reactions which play an important part

CHAP. XII.]

ALTERNATING-CURRENT WINDINGS.

in determining the voltage at the generator terminals, and this may only be maintained constant as the load comes on, by increasing the field excitation, often by a very considerable amount. Now, with a given number of armature conductors, earrying a given current, these reactions are greatest when the armature conductors are concentrated in one group per pole piece, that is, when the uni-coil construction is adopted, and they decrease to a considerable degree as the conductors are subdivided into small groups distributed over the entire armature surface, that is, they decrease when the multi-coil construction is used. The ratios given above for the relative voltages at no load, for uni- and multi-coil construction, do not, therefore, represent the relative values of the windings under working conditions, and it is believed that careful consideration should in many cases be given to both styles of winding, before deciding upon the one best suited for the purpose.

Multi-coil design also results in a much more equitable distribution of the conductors, and, in the case of ironelad construction, permits of coils of small depth and width which cannot fail to be much more readily maintained at a low temperature for a given cross-section of conductor, or, if desirable to take advantage of this point in another way, it should be practicable to use a somewhat smaller cross-section of conductor for a given temperature limit. And similarly, when we consider smooth-core construction, we find that the distribution of conductors over the entire surface carries with it great advantages from a mechanical standpoint.



CHAPTER XIII.

SINGLE-PHASE WINDINGS.

FIGURE 77 is a diagram of a winding for single-phase alternating-current generators and synchronous motors, which has been very extensively used. It has one group per pole piece, consisting of adjacent halves of two coils of the proper number of turns. These are interconnected as shown by the light lines. The adjacent halves of the two coils are usually arranged side by side, but it might sometimes be of advantage to place them one over the other. The arrangement of two coils side by side has been satisfactorily applied in various types of ironclad armatures. In Figs. 102 and 119 are given examples of this style of winding connected respectively for quarter-phase and for three-phase work. It should be noted, however, that the same armature can be used for three-phase purposes only by having fields with different numbers of pole pieces.

The avoidance of crossings at the ends, and the extreme simplicity of this style of winding, are its chief advantages.

166



Fig. 77



Fig. 78

In Fig. 78 is given another uni-coil winding, but here only one coil is placed in each slot. In many cases this might be preferable to the arrangement shown in Fig. 77, but the ends of the armatures are not so completely occupied by the ends of the coils, which wastes room and tends to bring about a less even distribution of the loss by heating. The use of only half as many coils is, of course, generally an advantage, on account of simplicity, but it is usually necessary for each coil to be wound deeper, which is objectionable from a thermal standpoint, as well as from the fact that a greater depth of space has to be allowed for the winding at the ends of the armature.

It should not be overlooked that if half the number of pole pieces is odd, the armature coils could not be connected up in two parallels, which would in practice be a very considerable objection, as it would limit the use of the armature for other purposes than that contemplated in laying out the original design.

One feature of this winding worthy of consideration is the great ease of insulation, it being, in this respect, superior to Fig. 77, one of the groups of which consists of adjacent halves of two coils, having between them the entire voltage of the armature.



[CHAP. XIII.

Figure 79 is a bar winding, with one bar per pole piece, corresponding to the coil winding of Fig. 78. This would be used for low voltages, and in the case of generators of large capacity, such windings are practicable for high voltages. It is typical of the simplest form of a multipolar, single-phase alternator, and has been used in some very large machines.





Fig. 80

Figure 80 is another uni-coil winding. It is given largely as a matter of interest; for, as will be seen, it has undesirable crossings and very long end connections, which would be very wasteful of copper unless the length of the magnet cores parallel to the shaft is great compared with the length of the pole arc. Even in such a case there would be no advantage over Fig. 78, unless for the fact that Fig. 80 is a very good winding for a three-phase alternator of one-third the number of poles, and the case might occur where it would be of advantage to use the same armature and winding for both cases. This would make an excellent three-phase winding for one-third as many poles, and would then be similar to the three-phase winding given in Fig. 116.

The corresponding diagram for a bar winding, with one bar per pole piece, is sufficiently evident from Fig. 80, and, in view of its unimportance, will not be given.



The following diagrams are multi-coil, single-phase alternators. As a class they have been very thoroughly discussed in the general remarks of the preceding chapter.

Figure 81 represents a very simple two-coil winding. It is to be noted that this winding is mechanically identical, with the exception of the interconnection of the coils, with the winding of Fig. 78, but it is put in a frame with *half as many* poles as there are groups of conductors, instead of, as was the case in Fig. 78, being laid out for a frame with a number of poles *equal* to the number of groups of conductors.

As already pointed out, such multi-coil windings do not at no load generate so great an electromotive force per unit of length of face conductor, as uni-coil windings. It has, however, been also shown on page 164 that this objection does not have such great weight as would at first sight appear to be the case.



Fig. 81



Fig. 82

Figure 82 gives a bar winding with two bars per pole piece. It corresponds to the coil winding of Fig. 81. These two windings (Figs. 81 and 82) could probably be used to advantage in many cases, but, of course, their disadvantages should be carefully considered.



[CHAP. XIII.

Figure 83 represents another two-coil winding. It would seldom be used, as it has the faults and lacks the merit of the winding given in Fig. 81.

If, however, the coils, instead of being evenly spaced, were brought into groups of two, not very far apart, it would, to some extent, have part of the advantages of the uni-coil construction, and would partly overcome some of the faults of the latter. If modified in this way, it would partake of the nature of the windings given in Figs. 97, 98, and 99, and the remarks made in connection with these figures should be referred to.

1

If Figs. 81 and 82 should be similarly treated (that is, if the coils should be brought into groups of two coils each, not very far apart), the result would be a winding comparable to those given in Figs. 97 and 99.





Fig. 84

Figure 84 is a diagram of another two-coil winding. It is connected as a single-phase alternator, but except for the manner of interconnection of the coils it is identical with the quarter-phase winding given in Fig. 100. It will give the same voltage as would Fig. 100, if the two components of the quarter-phase winding should be connected in series.

For this reason (that is, because when reconnected, it makes a good quarter-phase winding), it might sometimes be used, but of course, would, as stated in connection with previous windings, require a greater length of wire to generate the same voltage than a uni-coil winding, and would naturally have a greater armature self-induction. But, of course, the decrease in self-induction due to the multi-coil construction would somewhat compensate for this increase. Figure 85 gives a diagram for a single-phase bar winding, corresponding to Fig. 84. It is only of interest as showing that it is identical with Fig. 82, except that the long-end connections which were at the collector ring end in Fig. 82 are now at the other end.

It should be noted that all these multi-coil windings now under consideration would, for a given terminal voltage, require much more field excitation at no load than corresponding uni-coil windings. But at full load they would, in some cases, require little if any more field excitation than would be the case with uni-coil windings. As a result of these considerations it will be seen to be necessary in any particular case to observe the requirements for the field excitation as regards permissible regulation, heating, etc., when deciding upon the type of armature winding to adopt.





Fig. 86

Figure 86 should be compared with Fig. 80. It is quite like the latter, except that it has two coils per pole piece instead of one. It would, of course, not be used, as it has such long end connections.

The number of poles is sixteen. Such a winding with twelve, eighteen, or twenty-four poles could be used in a three-phase armature of one-third the number of poles by merely changing the interconnections of the coils. Figure 123 gives such a diagram for a three-phase alternator in an eight-pole frame.

The mechanical arrangement of such windings as those given in Figs. 80, 86, and 123 is exceptionally good, although in the case of Figs. 80 and 86, they are much less simple, as single-phase windings, than those that do not cross. Figure 87 represents a winding with two groups of coils per pole, and two coils per group. It will be seen to be identical with the two-phase winding of Fig. 103, except that it is connected up as a single-phase winding. With the exception of the sequence of interconnection of the coils, it may be considered to be two windings like Fig. 77, one of which is displaced 90°, so that its conductors lie half way between those of the other.

Its end connections permit of good mechanical arrangement; very much, in fact, like that of Figs. 80, 86, and 123.



Fig. 87



Fig. 88'

Figure 88 shows a useful three-coil winding. It has all the advantages and disadvantages already noted of multi-coil armatures.

The end connections can be very nicely arranged, so as to permit of winding on forms and slipping them into slots. Only two different shapes of forms are necessary; one-half of the coils would be wound in one of them, and the rest in the other.

It will be seen that it is really the three-phase winding of Fig. 116 connected up as a single-phase winding. For this reason, among others, it might be expected to be of service where it would be of advantage to have armatures which could be used interchangeably for single- or three-phase work. Most three-phase windings could, of course, be similarly used.

As a single-phase winding *per se*, Fig. 88 is excelled by the windings of Figs. 92 and 94, which require a smaller length of cnd conductors.



Figure 89 is the bar winding corresponding to the coil winding of Fig. 88. It is not a generally useful winding. Among other faults it has three different lengths of end connections, half of them being very long. In this respect it is excelled by the winding given in Fig. 93. The end connections at one end are perfectly regular, but this would seldom be considered to compensate for the needlessly great length of copper employed.

This winding is an example of the importance of thoroughly examining many diagrams before adopting a winding for a certain case; for it is not at once apparent that this winding could be improved upon, and if thought of first, might be chosen without further investigation.



Fig. 89



Fig. 90

Figure 90 gives a coil winding very similar to that of Fig. 88. But the end crossings would render it very inconvenient, and the space at the ends of the armature is not so well utilized as it was in Fig. 88. This would tend to an undesirable concentration of the heating.

Unlike Fig. 88, the winding would not interfere with the armature, being made in segments for convenience of shipment. But Figs. 92 and 94, which require less copper in the end connections, also possess this advantage, Fig. 94 to the greatest extent of all.



Figure 91 has all the faults of Figs. 89 and 90. It is the bar winding corresponding to Fig. 90. It is inferior to the winding shown in Fig. 93.

It has the advantage that the winding is more symmetrical as a whole than many better windings, and it is for this reason readily constructed and connected up, with little liability of error. It is a great help for the winder to be able to intelligently perform his work, and windings that are, electrically and mechanically, to a small extent inferior, might in some cases consistently be adopted because of the simplicity of winding. They also permit of the more ready locating and correcting of faults that are liable to develop during the practical operation of the machinery.




Fig. 92

Figure 92 is another three-coil winding. It gives the same results as Figs. 88 and 90, but with less copper, as it has shorter end connections. It is also simpler, as there is much less overlapping at the ends. Only two sizes of coils are necessary.

The chief point of inferiority to Figs. 88 and 90 is that it cannot be connected up as a three-phase armature.

Even Fig. 92 is not so good as Fig. 94 (to be described later), which latter has still shorter end connections and less crossings.

There is no good bar winding corresponding to Fig. 92.

Figure 92 possesses the advantage noted in the discussion of Fig. 90, that the armature may be built and shipped in sections without interfering with the winding. Figure 93 is the best bar winding for three bars per pole piece. It is distinctly superior to Figs. 89 and 91, as it has much shorter end connections. It requires, moreover, only two different lengths of end connections, whereas Figs. 89 and 91 each require three.

The following diagram is a section of a bar winding with five bars per pole piece : -







Fig. 94

Figure 94 is the coil winding corresponding to the bar winding of Fig. 93.

This coil winding is superior to that of Figs. 88, 90, and 92, in that it gives the same result with much shorter end connections and with fewer crossings of the end connections. Like Fig. 92, it eannot be connected up as a three-phase alternator, it being in this respect inferior to Figs. 88 and 90.

The winding of Fig. 94 could readily be built in sections in cases where it would be necessary to ship the armature in segments.

THP ERSI

Figure 95 is a coil winding electrically equivalent to Figs. 88, 90, 92, and 94.

Windings of this class may readily be derived from the example given in Fig. 95, for any desired number of coils per pole piece. It often works out well from a mechanical standpoint, and although the end connections are necessarily longer than in the preceding windings, it will frequently be found useful.

The various coils might with advantage be grouped to a greater or less extent, in accordance with the principles exemplified in Figs. 97, 98, and 99, which, together with the accompanying text, should be consulted in this connection.





Fig. 96 `

Figure 96 gives a coil winding with one and one-half coils per pole piece. It has two coils per group. It is really a winding such as Fig. 77, put in a field with two-thirds as many poles as the armature has coils. Thus in Fig. 96 there are thirty armature coils and twenty field poles. There is disadvantageous counter-induction which makes the use of more armature copper necessary than would be used in a uni-coil winding. The armature could, however, be used interchangeably in fields with n and with $\frac{2}{3}n$ poles, which property permits of the use of the armature in cases where different speeds or periodicities may be called for.

Also by changing the interconnections of the coils, an excellent three-phase armature is obtained. The three-phase connections of such a winding are given in Fig. 119.

Moreover, owing to the fact that when one side of a coil is under a field pole, the other is between two poles, the selfinduction of such a winding is low, and is fairly uniform for all positions of the armature. Many of the multi-coil windings given heretofore have been somewhat undesirable by reason of the counter-induction, which made it necessary to have a greater length of conductor for a given voltage than would have been necessary if the conductors had been concentrated in one coil per pole piece.

Figure 97 is a winding which, while retaining to a great extent many of the advantages of multi-coil windings, is usually as good with regard to its freedom from counterinduction as a uni-coil winding with evenly spread coils.

It is in fact one of the two windings of the quarter-phase diagram of Fig. 104.





Figure 98 does not differ essentially from Fig. 97 as far as regards the point that it is intended to illustrate. It, also, is one of the two windings of a quarter-phase armature, being in fact derived from the quarter-phase diagram of Fig. 112.

Other excellent diagrams of this type may be derived by eonsidering one of the two windings of the quarter-phase armatures shown in Figs. 105, 106, 107, and 111.

Figure 99, like its predecessors, Figs. 97 and 98, has its coils arranged in groups in the periphery of the armature. It has to some extent their advantages and disadvantages. It differs from them in utilizing two-thirds of the available space, instead of one-half, and is more of a compromise with the uniformly distributed windings.

It is obvious that windings such as the three just given may readily be derived from any of the evenly distributed multiphase windings by simply discarding one or more of the windings belonging to the respective phases of such diagrams. They may also be derived from many of the single-phase windings by shifting the coils laterally from the normal position into the desired groups.





Fig. 100

CHAPTER XIV.

QUARTER-PHASE WINDINGS.

FIGURE 100 represents a quarter-phase coil winding with one group of conductors per pole piece per phase. In accordance with the nomenclature already adopted, this would be known as a uni-coil winding; although it has but one coil per pole piece per phase, it has two coils per pole piece.

The two windings are represented, respectively, by full and broken lines. The winding is quite simple, but has the objection of crossings at the ends. In this respect it is inferior to the style of winding represented by the diagram of Fig. 102.

Three collector rings could be used, one of them being common to each winding. In the diagrams, however, four collector rings will be shown, this being the method now generally used. In connection with a system employing three collector rings, the standard quarter-phase commutating machines (to be described later) could not be used.

213



Figure 101 is the bar winding corresponding to Fig. 100. It does not well utilize all of the available space on the armature ends. This is generally not a great objection in the case of uni-coil windings, as there is in such cases plenty of room on the ends, but, other things being equal, it is of course preferable to have windings uniformly distributed at the ends as well as on the surface. In this connection Fig. 109 should be studied, and it will be seen that by placing two conductors in a group a perfectly symmetrical design is obtained with one group per pole piece.

A decided objection to this arrangement would be that adjacent conductors would have between them large differences of potential, whereas in Fig. 101 there are but few points in which neighboring conductors have between them any considerable percentage of the total terminal voltage.





CHAP. XIV.]

Figure 102 is a non-overlapping quarter-phase winding with one group of conductors per pole piece per phase. It has the advantage over Fig. 100 that there are no crossings at the ends of the armature, and that it utilizes the end space more completely, thus bringing about a better distribution of the necessary heating losses in the copper. Its chief fault is that if the width of the pole face is over one-half of the distance between pole centers, the coils never embrace the total flux from one pole piece. However, at full load, the area occupied by the flux is narrower, and a greater portion would be included than at no load, so that this objection would not be so serious as would appear at first sight. Moreover, the necessary space allowance for the field winding will in many cases not permit the width of the pole piece to be sufficiently great to cause any trouble in this respect. Mechanically, this is an excellent winding, being, in fact, the single-phase winding given in Fig. 77, for double the number of poles.

The remarks made in connection with Fig. 96 (singlephase alternating winding with one and one-half slots per pole piece) should also be considered in studying this winding. Consult also Fig. 119 and corresponding text.



Figure 103, which like Fig. 102 has two coils per group, is not open to the objection discussed on the preceding page. It has, however, crossings at the ends. It is to be preferred to Fig. 100 for the reason that the end space is more effectively utilized, but the additional crossings would require a somewhat greater length of wire than would be necessary in Fig. 100.

Bar windings could be built corresponding to the coil windings of Figs. 102 and 103. They would not be symmetrical at both ends, but might advantageously prove applicable for certain cases. The two bars of a group could be placed either over each other, or side by side. With smooth-core construction the latter arrangement would be adopted, and often also in ironclad armatures with bar windings.





Figure 104 is a quarter-phase coil winding with two conductors per pole piece per phase. It is entirely symmetrical, and utilizes all the winding space to the best advantage. The crossings at the ends are unavoidable, but may be made thoroughly satisfactory from a mechanical standpoint by proceeding in the manner shown most clearly in the diagram of Fig. 123.

Such windings are applicable to quarter-phase armatures with any even number of coils per pole piece per phase.

In studying Fig. 104 it will be instructive to examine Fig. 97, which is one of the two windings of Fig. 104.



Figure 105 is electrically equivalent to Fig. 104. The winding might sometimes be used, although it would for most purposes be excelled by Fig. 104.

It will be noted that the end connections are longer, and that they occupy a greater depth. Much of the end space is wasted. This winding is superior to that of Fig. 104, in that the coils are so located as to make it very plain how the connections should run. This would be of great assistance to the winder, and would, moreover, facilitate the detection and correction of faults that might develop in practical working.

An armature with such a winding could be built and shipped in segments.





Figure 106 is a bar winding differing but little in principle from the coil winding of Fig. 105. The space is uniformly occupied at the collector ring end, but is not at the other end.

This lack of uniformity in end connections is not of very great moment in bar windings with few bars per pole piece. Other things being equal, however, it would on the whole seem best to avoid it, although in special cases such disposition of the end-connections allows room much needed for mechanical arrangements.



Figure 107 is a bar winding corresponding to Fig. 104. It is a good example of the fact that very symmetrical coil windings often correspond to very unsymmetrical bar windings, and *vice versa*. But, as noted on the preceding page, this lack of symmetry is in such cases not a great objection, and has, incidentally, some redeeming features.

One of the two windings of this diagram would, as mentioned on page 209, work out very well for a single-phase armature.





Figure 108 is a much better bar winding than Fig. 107, though electrically equivalent.

It will be seen to be unsymmetrical at two points at the end distant from the collector This irregularity consists in the end connections of the two adjacent bars starting off in the same direction, instead of, as in all other parts of the winding except these two, going in opposite directions. Four of the end connections have to be longer than the rest.

This winding is practically the same as the following one, Fig. 109, except that the above described irregularity is introduced instead of making use of the cross-connections shown in Fig. 109.



Figure 109 is a symmetrical quarter-phase bar winding with two conductors per pole piece per phase. If used for an ironclad or projection armature, it may have four slots per pole piece with one conductor per slot, or two slots per pole piece with two conductors per slot.

Examination will show that it is essentially a twelve-pole armature with four separate series of windings of twelve bars each. These four windings are connected up into two windings of twenty-four conductors each.

At the front end y=5, and at the back end y=3, therefore average y=4.

As pointed out in the discussion of Fig. 101, Figs. 108 and 109 have the fault that neighboring conductors have between them large percentages of the total potential of the armature, and this would sometimes be objectionable in cases of high potential windings.

It will doubtless have been observed that in the case of quarter-phase windings, multi-coil construction does not have to so great an extent the fault pointed out in the case of corresponding single-phase windings, of useless counter-electromotive forces.

The coils of one phase usually embrace practically the entire flux, because the two groups of conductors, forming respectively the two sides of a coil, are usually separated by a group forming one side of a coil belonging to the winding of the other phase.

This advantage is possessed in a still greater degree by the three-phase windings, which will be discussed later.

Exceptions to the above statement often occur in cases where single and multi-phase alternating windings are obtained from ordinary directcurrent windings.




0

Figure 110 represents a quarter-phase coil winding with three slots per pole piece per phase. It does not utilize very uniformly the end space on the armature, the end connections being three layers deep at some points and much less at others.

An advantage of this winding is the well-defined nature of the coils, rendering it easy to see just how they should be connected. The winding might also be necessary, if it should be required that the armature should be built so that it could be shipped in segments.



Figure 111 is electrically equivalent to Fig. 110, but the end connections are only two layers deep, are shorter, and are better distributed over the ends of the armature. Where the number of coils per pole piece per phase must be odd, windings such as those given in Figs. 110 and 111 must for quarter-phase armatures often be chosen. It is quite apparent that, except in special cases, the style of diagram shown in Fig. 111 will give the best result.





Figure 112 is a bar winding corresponding to the coil winding of Fig. 111. Although not symmetrical, the end connections are fairly well distributed, and there would be in but very few places any great percentage of the total difference of potential between adjacent conductors. Several different lengths of end connections would necessarily have to be employed.

One of the two windings of this diagram has already been given in Fig. 98 in Chapter XIII. on Single-Phase Windings.



[CHAP. XIV.

Figure 113 represents a quarter-phase bar winding with four conductors per pole piece per phase. It is perfectly symmetrical, and may have one, two, or four conductors per slot, as desired.

This winding is like that of Fig. 109, except that four sets of elementary windings are connected in series to form one of the two phases, instead of two sets, as was the case in Fig. 109.

If one-half or one-quarter as great a terminal electromotive force should be desired, two, or all four, of these elementary windings could be connected in parallel between the collector rings, instead of joining them in series as shown.





Fig. 114

TWO-CIRCUIT WINDING FOR QUARTER-PHASE CONTINU-OUS CURRENT COMMUTATING MACHINE.

Figure 114 is the diagram for the winding for a commutating machine for deriving a continuous current from a quarter-phase alternating supply, or *vice versa*, or for a generator for supplying both continuous and quarter-phase systems.

Examination will show that it is the two-circuit single winding of Fig. 43 (Chap. VIII.), tapped off from four approximately equidistant points to four collector rings. As the winding consists of sixty-eight conductors, there should be seventeen conductors in each section, but for the convenience of having all the connections to the collector rings made at one end, the divisions are 16, 16, 18, and 18. With the large numbers of conductors used in practice, the irregularity produced by one conductor more or less would be of less importance, though always undesirable. In such a winding four points only of the armature are tapped independently of the number of poles.



TWELVE-CIRCUIT WINDING FOR QUARTER-PHASE CON-TINUOUS-CURRENT COMMUTATING MACHINE.

Figure 115 is another winding for a quarter-phase continuous-current commutating machine. It is fundamentally a multiple-circuit, continuous-current winding, and requires four leads (one to each collector ring) for each *pair* of poles.

It is to be remembered that in quarter-phase continuouscurrent commutating machines, the effective voltage between collector rings 180° apart equals the continuous-current voltage multiplied by .707 (or divided by 1.414).





Fig. 116

CHAPTER XV.

THREE-PHASE WINDINGS.

FIGURE 116 is a three-phase coil winding with one set of conductors per pole piece per phase. The coils belonging to the three windings may be distinguished from each other by the three different styles of lines. The armature is connected in a manner technically known as the "Y" connection. The characteristic of this style of connecting three-phase windings is that one end of each of the three windings is brought to a common connection, the other three ends being carried to three collector rings.

Inasmuch as three-phase alternators have but recently been used to any considerable extent in practice, it may not be out of place to give as concisely as possible a few of the leading considerations involved in their practical construction and operation, as far as relates to the armature windings.

One complete cycle is passed through by any armature conductor while passing from a certain point opposite one pole piece, say the middle of the north pole, to the corresponding point opposite the next pole piece of the same polarity. This angular distance is usually spoken of as 360°, independently of the number of poles of the machine. Now, a three-phase armature winding is merely three single-phase windings, laid on the same armature, the conductors of the three windings, however, being located 120° (one-third of a cycle) behind each other. Any conductor of one winding is, therefore, at any instant, in a different phase from that of the conductors of the other windings. Thus, in the position represented in Fig. 116, the conductors represented by heavy lines are directly opposite the middle of the pole pieces, the light line conductors are located 120° behind them, and the dotted conductors are 120° behind the light conductors and 240° behind the heavy conductors.

Now it follows from the relative positions of the conductors of the three phases, that the electromotive forces generated in the three windings are 120° behind each other, and if they are sine waves, they may be represented, as in the following figure, by three sine curves displaced 120° behind each other.



If the three circuits are equally loaded, these curves may also be considered to represent the corresponding instantaneous values of the current.



ARMATURE WINDINGS OF ELECTRIC MACHINES.

CHAP. XV.

It will be noted that at every instant, the algebraic sum of the three currents is zero. Now instead of having three *pairs* of lines and brushes and collector rings, one end of each of the three windings is brought to a common connection, and a conductor from this common connection could be used as a common return for each of the three circuits. But, since the resultant current at every instant is zero, this conductor becomes superfluous and is omitted.

If the voltage between any ring and the common connection, that is, the voltage per phase, is equal to v, then the volts V between any pair of collector rings will be, —

$$V = \sqrt{3} v \text{ or } 1.732 v.$$

The effective current will be equal in each of the three lines, and may be represented by C. With a non-inductive load, the watts output, W, will be, —

$$W=3 \ Cv = \frac{3 \ CV}{\sqrt{3}} = 1.732 \ CV.$$

If the load is inductive, the current C, for a given output W, will be greater than with a non-inductive load.

A safe and easily understood way of connecting the three windings correctly to the three collector rings and the common connection, is to consider that the winding whose conductors occupy the position in the middle of the pole piece, is carrying the maximum current, and to indicate its direction on the winding diagram by an arrow. The currents at the same instant in the conductors immediately next to it on the right and left are in the same direction, and should be so marked by arrow-heads. Now, from the sine curves given above, it will be seen that where one curve has a maximum value, the other two have a value half as great, and in the opposite direction. Therefore consider that the current in the winding occupying the position at the middle of the pole face is flowing away from the common connection. Then the currents in the other two windings, which are each of half the magnitude of the former, must both be flowing into the common connection; therefore join those ends of the three windings to the common connection, which will bring about this condition at this instant. Carry the other three ends to the three rings. This has been done in the upper diagram of Fig. 117, which represents a "Y" connected three-phase winding.

Another way of connecting up three-phase armatures is to connect the three windings in series in a closed circuit, and at every third of the total way through the circuit thus formed, to carry off a lead to one of the collector rings.

In the case of this, technically called the "delta" (Δ) connection, the current C in the line (*i.e.* beyond the collector rings) is $C = \sqrt{3}c$, or C = 1.732c, where c = current in the winding. The volts per winding are in this case equal to the volts between each pair of collector rings; that is, to the volts per phase. The watts output of a machine are, —

$$W = 3 \, cV = \frac{3 \, CV}{\sqrt{3}} = 1.732 \, CV.$$

Examples of each of these two connections are given in Fig. 117.

The upper diagram represents a "Y" connected three-phase armature, and the lower diagram represents the very same armature, but with a "delta" (Δ) connection.

In connecting up the separate windings for a "delta" (Δ) connection, it is most convenient to choose the instant when the conductors of one phase are opposite the middle of a pole piece. Then assume these conductors to be carrying the maximum current, which is illustrated in the figure by the larger arrow-head.



Fig. 117





Fig. 118

THREE-PHASE WINDINGS.

CHAP. XV.]

The other two windings are at the same instant having induced in them currents of only one-half this magnitude. The condition of affairs in line and in winding is, for the instant, as represented in the follow-ing diagram.

From this it is seen, that, starting from the middle collector ring (corresponding to point a in the diagram), and following the direction of the current, we must pass through the heavy winding, carrying the large current to the outer ring (corresponding to point b of diagram). In the other direction, we must pass from the middle ring (*i.e.* point a), through the dotted winding, which carries one-half as great a current, to the inner collector ring (corresponding to point c of diagram). Then we must continue through the light winding, still in the direction of the current, until we again reach the outer collector ring, or point b of diagram.

Any of the following three-phase diagrams may be connected either "delta" or "Y," but they will usually be shown with the "Y" connection.



It is well to keep in mind that if a "Y" connected armature is changed over to the "delta" connection, it may with the same regulation and heating give 1.732 times as much current, but only $\frac{1}{1.732}$ times the voltage. The reverse holds true in changing from "delta" (Δ) to "Y."

Figure 118 is the bar winding corresponding to Fig. 116. It has one bar per pole piece per phase. This winding, while partaking of all the advantages and disadvantages of multi-coil construction, would be particularly unsatisfactory for a three-phase *motor* on account of the dead points that it would develop at starting. These dead points are much less marked with multi-coil windings and with windings like those in Figs. 119 and 120.

In the case of induction motors, it is customary to make use of such windings as those given in Figs. 126 and 127, where smoother action is obtained partly by virtue of the choice of a number of conductors, prime, or nearly so, to the number of poles.



Figure 119 is a non-overlapping, three-phase, coil winding, with only one and one-half coils per pole piece per phase. It is the winding which was given with its singlephase connection, in Fig. 96. This should make a very excellent three-phase winding, as there is no crossing of the coils. It is a regular thirty-pole, single-phase winding, connected up as a three-phase armature for twenty poles. This diagram should be compared with Fig. 77, Fig. 96, and Fig. 102. It should be particularly suitable for use in threephase motor work, as it should have very weakly defined dead points. In a projection armature, when a slot is opposite a certain pole-piece, spaces between two slots will be opposite the adjacent pole pieces, thus giving a more equitable distribution of the magnetic flux.

The inductance of such a winding is low and fairly uniform, for the reason that when one side of a coil occupies a position under a pole piece, the other side of the coil is between two pole pieces.



Fig. 119



Fig. 120

Figure 120 represents the corresponding bar winding. In the case of projection or ironclad armatures, it would have two bars per slot, which might be arranged one over the other or side by side. It is interesting to note that each slot would contain one bar of each of two windings, two bars of the same winding never occupying the same slot.

All the remarks regarding the winding of Fig. 119 apply equally well to Fig. 120.



[CHAP. XV.

Figure 121 is a three-phase coil winding, with two groups of conductors per pole piece per phase. The mechanical arrangement of the coils at the ends of the armature could not be designed nearly so satisfactorily from a mechanical point of view, as in the style of winding given in Fig. 123. It is believed that in most instances the style of winding shown in Fig. 123 will be found to give the best results.





Figure 122 is the bar winding corresponding to Fig. 121. The end connections are perfectly symmetrical and well distributed at one end, but are far from it at the other. Its point of superiority over Fig. 124 is that it has, as a rule, no great differences of potential between adjacent conductors.

As already stated, the irregular distribution of the end conductors is not, at least in the case of bar windings, so great an objection in cases where there are comparatively few bars per pole picce. And in this instance there is a sort of a regularity about their grouping, that might be found of advantage on account of the large spaces that it makes available for mechanical arrangements.



CHAP. XV.

Figure 123, which was devised by Mr. Thorburn Reid, who has devised a number of useful windings, is superior in the mechanical arrangement of the coils, to the winding of Fig. 121. The corresponding bar winding is not drawn, but it may be readily seen that it would have no very obvious advantages.

Coil windings of the same style as that of Fig. 123 may be constructed with any number of coils per pole piece per phase, and are frequently superior to other arrangements.

It is thought that the style of lining adopted in the diagram will indicate fairly well the arrangement of the end connections, if care is taken to note that the conductors of some groups of coils are carried directly over in the same planc as the face wires, to the conductors forming the other side of the group. The end conductors of the other coils have to be bent down out of the plane of the face conductors and then back again into their plane. The coils are usually wound in forms and then laid in place on the armature.





Figure 124 is a three-phase bar winding, with two bars per pole piece per phase. It is perfectly symmetrical, and may have either one or two conductors per group. It is inferior to Fig. 122, in that, from the nature of the winding, there are much greater differences of potential between adjacent conductors than in Fig. 122.

In Fig. 124, the pitch is 5 at one end and 7 at the other. Two sets of conductors, each set having as many conductors as there are pole pieces, are joined in series to form each one of the three windings. If an armature for half the voltage had been wished, the two sets of conductors forming each winding would have been connected in parallel.

This winding, as well as the next (Fig. 125), is of the same general character as those shown in Figs. 109 and 113.



CHAP. XV.

Figure 125 is similar in all respects to Fig. 124, except that it has three conductors per pole piece per phase. The pitch is 9 at both ends. It could be connected so as to give one-third as great a terminal electromotive force by joining the three elementary groups of which each winding is formed, in parallel, instead of in series.

In connection with Figs. 124 and 125, emphasis should be laid on the fact that in virtue of the nature of these windings, whereby adjacent conductors have between them large differences of potential, valuable space has to be sacrificed to make room for the proper thickness of insulation, which, with types of winding not possessing this character, could be usefully employed.





Fig. 126

Figure 126 is a four-pole, three-phase bar winding of a very irregular character. It has fifty-one conductors, seventeen per phase. There are, therefore, unequal numbers of conductors, both per phase and per pole, opposite the different pole pieces.

This style of winding has been used with success in induction motors, where it is important to choose a number of slots on the armature, which is prime, or nearly so, to the number of slots on the field. It may be well to state that, in the case of induction motors, the field, in the most successful types, consists merely of an assembly of annular punchings with radial slots within which the cylindrical drum *armature* revolves. It is practically a transformer, one of the elements, usually the secondary, being movable. It has become customary to call the moving element, the armature, and the stationary, the *field*. In the types, and for the voltages generally employed, it has been found best to use a coil winding for the field, the coils often being wound on forms and slipped into the slots. In the armature, which is practically a short-circuited secondary, the number of conductors and slots is determined by the permissible inductance, the actual voltage of the armature being to a great extent immaterial. In certain types the ratio of field to armature conductors has been something like 6:1. It is in connection with such motors as these, that the winding diagram of Fig. 126 will be found of greatest service. There cannot well be more than one bar per slot, because of the irregularity of the end connections.



[CHAP. XV.

Figure 127 is another three-phase bar winding with fiftyone conductors. It has six poles, and is even more irregular than the winding of Fig. 126. It, like Fig. 126, will find its chief use in the design of induction apparatus. Windings, almost as irregular, might be used in large polyphase generators, where it is desired to have but one conductor per slot.


Fig. 127



Fig. 128

TWO-CIRCUIT WINDING FOR THREE-PHASE CONTINUOUS-CURRENT, COMMUTATING MACHINE.

Figure 128 represents the same winding as Fig. 114, except that here it is tapped off at three nearly equidistant points instead of at four, as was the case in Fig. 114.

The result is a winding for a three-phase, continuouscurrent, commutating machine.

The total sixty-eight bars are divided up into sets of twenty-two, twenty-two, and twenty-four conductors, respectively, which are represented on the diagram by heavy, light, and dotted lines.

If the conductors are arranged in groups of two each, as would frequently be the case in projection armatures, where two conductors would often be placed together in each slot, it is of interest to note that these two conductors never belong to the same phase.

SIX-CIRCUIT WINDING FOR THREE-PHASE, CONTINUOUS-CURRENT, COMMUTATING MACHINE.

Figure 129 is still another three-phase, continuous-current, commutating machine, but with a six-circuit winding. It requires three leads per pair of poles; therefore, in this case, nine leads. It is quite analogous to the quarter-phase, continuous-current, commutating machine of Fig. 115.

It is of interest to notice the relation of the voltage between collector rings to the continuous-current voltage at the commutator, in the case of three-phase, continuous-current, commutating machines. It will have been observed that they have "delta" connected windings.

Let V = continuous-current voltage at the commutator; then, taking the point of zero potential to be at the middle of the winding, the electromotive force of each half of the winding is $\frac{V}{2}$. But the corresponding *effective* alternating electromotive force will be $\frac{V}{2\sqrt{2}}$. This, therefore, will correspond to the voltage between common connection



(point of zero potential), and collector ring, for an equivalent "Y" connected three-phase armature winding. Now the voltage between the collector rings of the "delta" connected armature winding will be $\sqrt{3}$ times as great as the voltage to the common connection of this equivalent "Y" winding, therefore the voltage between the collector rings will be, —

$$\frac{\sqrt{3}V}{2\sqrt{2}} = .612V,$$

where V =continuous-current voltage at commutator.

Inasmuch as a "delta" connected winding cannot be readily conceived to have a point of zero potential, the above subterfuge of substituting for it, the *equivalent* "Y" connected winding, will often be found to facilitate the handling of three-phase winding problems. When doing so, the *equivalent* "Y" potential and the *equivalent* "Y" current may be spoken of as attributes of a "delta" connected armature. In the accompanying figure, an *equivalent* "Y" connected winding is diagrammatically shown dotted within a "delta" connected winding.



Fig. 129



PART III.

WINDING FORMULÆ AND TABLES.





CHAPTER XVI.

618) 4446

FORMULÆ FOR ELECTROMOTIVE FORCE.

COMPREHENSIVE formulæ for the calculation of the electromotive force set up in armatures may be derived from the formula for the voltage in a circuit, in which the variation of magnetic flux is a simple harmonic function of the time. These formulæ are :---

- 1.000 1. $V = 6.28 TNM 10^{-8}$, the maximum voltage set up in a cycle;
- 2. $V = 4.44 \ TNM \ 10^{-8}$, the effective voltage set up in a cycle :
- 3. $V = 4.00 TNM 10^{-8}$, the mean or average voltage set up in a cycle, 637

where V is the voltage generated, in volts; T the number of turns in series, M the number of cgs lines included or excluded by each of the T turns in a magnetic cycle, and N the number of magnetic cycles per second.

In armatures of alternators, the effective, or square root of the mean square of the electromotive forces is required, since this is proportional to the effective voltage, *i.e.* the voltage to maintain current C (square root of the mean square of the current), in a non-inductive resistance. In this case it is supposed that the T turns are so situated as to be simultaneously affected by any change of the magnetic flux, otherwise the voltage for each of the turns differently situated must be calculated separately and properly combined to obtain the resultant voltage.

In the case of multi-phase alternating-current machines, the voltage in each circuit should be calculated, and the resultant voltage derived according to the method of connection, and addition of vectors according to the angle by which the several phases differ from each other.

In quarter-phase machines with common connection, the resultant voltage is $\sqrt{2}$, or 1.414 times the voltage generated in one circuit.

In three-phase apparatus, the resultant voltage is the same as the voltage generated in one circuit when the circuits are connected "delta"; and $\sqrt{3}$, or 1.732 times the voltage generated in one circuit when the circuits are connected "Y."

In alternating-current commutating machines, the ratio of the voltage between the continuous and the alternating current circuits is 1:.707 in the case of single-phase and quarter-phase commutating machines, and 1:.612 in the case of three-phase commutating machines. In other words, if the voltage at the continuous current side is known, the voltage between collector rings will be .707 times as great in the case of single and quarter phase commutating machines, and will be .612 times as great in the case of three-phase commutating machines.

In armatures of continuous-current dynamos, the voltage at the terminals is constant during any period considered, and is the integral of all the voltages successively set up in the different armature coils according to their position in the magnetic field; and since in this case only average voltages are considered, the resultant voltage is independent of any manuer in which the magnetic flux may vary through the coils.

Formula 3 is applicable to all continuous-current armatures, whether ring, drum or disc, two-circuit or multiple circuit, and whether the winding be single or multiple.

The simplicity and wide applicability of these formulæ make them preferable to many others that are difficult to interpret, because of the many accessory conditions that must be kept in mind.

Although, by the constants given above, the voltages may be obtained at the alternating current, as well as at the continuous current terminals of commutating machines, the former, *i.e.* the voltages at the alternating current terminals, may be obtained from the following formulæ, in which V is the required voltage between collector rings, T is the number of turns in series between collector rings, M is the magnetic flux from one pole piece into the armature, and N is the number of cycles per second:—

For single and quarter phase commutating machines, $V=2.83 \ TNM \ 10^{-8}$. For three-phase commutating machines, $V=3.69 \ TNM^{-8}$.

CHAPTER XVII.

METHOD OF APPLYING THE ARMATURE WINDING TABLES.

THE nature and use of the tables may be most easily understood by applying them to the solution of a few examples.

EXAMPLE 1. — If we wish a two-circnit, triple winding for a drum armature, with about 670 conductors and six poles, what is the exact number of conductors that must be employed to give ns a singly reentrant winding?

Turning to page 312, we find that a two-circuit, triple winding with 670 conductors, is impossible for six poles, but that 672 conductors may be used; and to have the winding singly re-entrant, the front and back pitches must each equal 113. If the front and back pitches should be taken equal to 111, a triply re-entrant winding would result.

EXAMPLE 2. — We next wish to ascertain how many volts this machine will give when the armature is driven at 440 r.p.m., if the flux from each pole piece into the armature equals 2.25 megalines.

The table of Drum Winding Constants on page 280 tells us that with 100 conductors, 100 r.p.m., and a flux equal to one megaline, the terminal volts will, for a six-pole machine, be equal to 1.667. Therefore, in the case before us, we have

 $V = 1.667 \times 6.72 \times 4.40 \times 2.25 = 111$ volts.

From the same table we find that for a two-circuit, triple winding with six poles, we have .200 average volts between commutator segments per megaline and per 100 r.p.m. So, in this case, we shall have $.200 \times 2.25 \times 4.40 = 1.98$ average volts between commutator segments.

EXAMPLE 3. — Certain conditions fix the flux of a dynamo from one pole piece into the armature at 8.30 megalines, and the speed at 100 r.p.m. If we wish to employ an eight-pole, two-circuit, double winding, how many conductors do we need, to obtain 150 volts?

Consulting the table of Drum Winding Constants, on page 280, we find that for eight-pole, two-circuit, double windings, we have 3.33 volts per 100 conductors with 100 r.p.m., and one megaline of flux. Therefore, we shall require $\frac{150}{3.33} \times \frac{100}{8.30} = 544$ conductors.

By reference to page 301, it will be seen that for eight poles, the nearest number of conductors that we can use in order to have a two-circuit, double winding, is 540 or 548. Suppose we use 540 conductors. If we wish a doubly re-entrant winding, we shall take the pitch at one end equal to 67, and that at the other end equal to 69.

EXAMPLE 4. — A slotted armature is to have ten poles, and a two-circuit, triple winding, with eight conductors per slot.

ARMATURE WINDINGS OF ELECTRIC MACHINES.

By reference to the table of Summarized Conditions for Two-Circuit, Triple Windings, on page 283, we find that it may be either singly or triply re-entrant, according to the number of conductors used.

The winding is to have 424 conductors. Turning to page 310, it is seen that the pitch must be 43 at both ends, and that for 424 conductors the winding must be singly re-entrant.

If the flux is 20.0 megalines, and the speed 105 r.p.m., we find from page 280 that the voltage will be

$$2.78 \times 4.24 \times 1.05 \times 20.0 = 247$$
 volts.

The average volts per bar are

 $.556 \times 20.0 \times 1.05 = 11.7$ volts.

EXAMPLE 5. — An eight-pole armature has a multiple-circuit, double winding, with 1258 conductors. By consulting page 343, we find that it is singly re-entrant, and that the pitch should be 155 at one end, and 159 at the other. It is, of course, understood that these pitches are taken in opposite directions. One of them might have been indicated as positive, and the other as negative. It may be well to point out here that the letters F and B at the head of the tables, meaning respectively, "front" and "back," are interchangeable, meaning merely that the one figure represents the pitch at one end, and the other figure, that at the other end. This is true in regard to all the tables, both two-circuit and multiple-circuit.

Returning to Example 5, the voltage of the machine, assuming the flux equals 7.85 megalines, and a speed of 300 r.p.m., is found by the table of Drum Winding Constants on page 280, to be

 $.833 \times 12.58 \times 3.00 \times 7.85 = 247$ volts.

The average volts per bar are

 $.1333 \times 7.85 \times 3.00 = 3.14$ volts.

EXAMPLE 6. — A two-circuit, single winding is wanted, with four conductors per slot.

From the table of Summarized Conditions for Two-Circuit, Single Windings, on page 281, it may be seen that this is only possible with 6, 10, 14, etc., poles; being impossible with 4, 8, 12, 16, etc., poles. The winding is designed for fourteen poles, and 660 conductors. We find from page 329, that the pitch is 47 at both ends. The machine gives 160 volts, and the speed is 75 r.p.m. By the aid of the table on page 280, we find that the flux is equal to

 $\frac{160}{11.67 \times 6.60 \times .75} = 2.77$ megalines.

Average volts per commutator segment = $3.27 \times 2.77 \times .75 = 6.80$ volts.

The above examples have all been chosen merely to illustrate the use of the tables, and the relative magnitudes employed in any one example are *not* such as would occur in practice.

The tables on pages 280, 281, 282, and 283 are constructed on the assumption that no interpolated commutator segments are employed, and that no portion of the normal number of commutator segments is omitted, and when this is not the case, the results should be properly modified, as may readily be done.

In all the tables, a proper interpretation of the term "conductors" should be made. As stated in the introductory chapter, "groups of conductors" may often be substituted therefor.

It is believed that after becoming familiar with the arrangement of the tables, their use will be found to be of value in a great variety of problems connected with armature windings. Any single result can, however, be obtained by an application of the rules and formulæ given in the text, but after these rules and formulæ are once understood, it will be found that subsequent problems will generally be most conveniently solved by means of the tables.

278

CHAPTER XVIII.

ARMATURE WINDING TABLES.

						NUMB	ER OF F	POLES		
		CLA	SS OF WINDING.	4	6	8	10	12	14	16
	RS	w F	Single	1.667	1.667	1.667	1.667	1.667	1.667	1.667
	ND ND.	TIP	Double	.833	.833	. 833	.833	.833	.833	.833
	M. A M. A	MUI	Triple	.556	.556	.556	.556	.556	.556	.556
	M P C		a: 1	0.00	5.00	0.07	0.00	10.00	11.07	10.00
С Ш	0 B 0		Single	3.33	5.00	6.67	8.33	10.00	11.67	13.33
JRI	7 100 X	0 V	, Double	1.667	2.50	3.33	4.17	5.00	5.83	6.67
T	PEF	CIRC	Triple	1.111	1.667	2.22	2.78	3.33	3.89	4.44
WP	IOA									
AR		шь	Single	.1333	.200	.267	.333	.400	.467	.583
W	MMUT MEGA R MEGA P. M. CONDS.	TIPI	Double 🛞	.0668	.100	.1333	.1667	.200	.233	.267
DRL	OO B CO	CIF	Triple 🛞	.0445	.0667	.0888	.1111	.1333	.1555	.1778
ч	RA LICE									
	AVER BAKW PER ENT O		Single	.267	.600	1.068	1.668	2.40	3.27	4.27
	S BE S BE ENDE	wo	Double 🛞	.1333	.300	.534	.834	1.200	1.635	2.14
	VOLT LIN NDEP	CIF	Triple 🛞	.0888	.200	.356	.556	.800	1.09	1.42

DRUM WINDING CONSTANTS.

With Multiple Windings, the maximum Volts per bar is much more greatly in excess of the average Volts per bar than in Single Windings. This may be seen by a careful analysis of such Windings; which also shows that this may be more or less overcome by careful_mutual adjustment of the position of the Brushes. This would not, however, be practicable with present methods.

DATA F	ORAI	PPLY FC	ING T	WO-	CIRCI	UIT, S TURI	SINGL ES.	EWI	NDIN	GS,	PER 100 PER 100 ITH FLUX GALINE	AGE ETWEEN GGTS PER NE & PER . P. M
NUMEER OF POLES				CONE	оистор	RS PER	SLOT				VOLTS F CONDRS. R. P.M. W	AVER VOLTS BI COMR. SE MEGALIN 100 R
4	1	2		6		3.33	.267					
6	1	2	4		8		5.00	.600				
8	1	2		6		10	1.5	14			6.67	1.068
10	1	2	4	6	8		12	14	16		8.33	1.668
12	1	2				10		14			10.00	2.40
14	1	2	4	6	8	10	12		16		11.67	3.27
16	1	2		6		10		14			13.33	4.27
	Ø Inde	ependen	l It of nu	mber of	f Condu	ctors			·	_		

From the above Table the following Rule may be deduced:

In the ordinary two-circuit single winding, "C" is always such a number that the number of conductors per slot, and "n" the number of poles, cannot have a common factor greater than 2.



DATA FO	RAPF	PLYIN FO	G TWO R DRU	D-CIR	CUIT, MATU	DOUI RES.	BLE W	INDIN	IGS,	ER 100 PER 100 TH FLUX GALINE	AGE ETWEEN 3TS. PER P. M.
NUMBER OF	1		(CONDU	CTORS F	PERSL	тс		_	DRS. DRS. 1 ME	AVER. TS BE R. SEG SALIN SALIN
POLES	1	2	4	6	8	10	12	14	16	VOI CON E.P.N	VOL COM MEG
4	00	000	@ 00	1.667	.1333						
6	00	00	00	2.50	300						
8	00	000	00		3,33	.534					
10	00	00	00	00	00		00	00	00	4.17	.834
12	000	00	000		\bigcirc	00		000	Q	5.00	1.200
14	00	00	00	000	00	000	00		00	5.83	1.635
16	@ •••	00	000	00		00	000	00		6.67	2.14
	() Inde	pendent	of numb	er of Co	nductors						

(3) Moreover, in multiple Windings this value is merely nominal, as a careful analysis of Multiple Windings shows that if this value can be approached at all, it is only by means of more careful mutual adjustment of the Brushes than is practicable with present methods.

DATA F	OR AP	PLYIN FOR	IG TW DRU	O-CIF	CUIT MATU	, TRIF RES.	PLEW	INDIN	IGS,	VOLTS PER 100 CONDRS. PER 100	AVERAGE VOLTS BETWEEN COMMR. SEGTS.
NUMBER			(CONDUC	TORS F	PERSLO	т			R.P.M. WITH FLUX = 1 MEGALINE	PER MEGALINE & PER 100 R. P. M.
OF POLES	1	2	4	6	8	10	12	14	16		8
4	000	000			1.111	.0888					
6	@ <u>0</u> 000	000	000	000	1.667	.200					
8	000	(QQ) 000			2.22	.356					
10	000	000	000	000	000		000	000	000	2.78	.556
12	000	QQ 000		(QQ) 000		(QQ) 000		(QQ) 000		3.33	.800
14	000	@ 000	000	000	(QQ) 0000	(QQ) 000	000		@ <u>@</u>	3.89	1.09
16	@ @	000		000		000		000		4,44	1.42
	•	Independ	lent of r	umber o	f Condu	otors					

(1) Moreover, in Multiple Windings this value is merely nominal, as a careful analysis of Multiple Windings shows that if this value can be approached at all, it is only by means of more careful mutual adjustment of the Brushes than is practicable with present methods.



WINDING TABLES FOR TWO-CIRCUIT, SINGLE WINDINGS FOR DRUM ARMATURES.



TAB	BLE C	OF TV	vo-c	IRCU	UIT, s	SING	LEV	VIND	INGS	6, FO	RDR	NUM	ARM	ATU	RES.
rors					FR	ONT	AND	BACK	K PITO	CHES	*				TORS
and		4	E	3	De	3	1	0	1	2	1	4	1	6	NDUC
F CON	PO.	LES	PO.	LES	P0.	LES	PO	LES	POI	LES	PO	LES	POI	LES	DE COI
0°. No.	F	B	F	В	F	B	F	B	F	B	F	B	F	В	No. C
$102 \\ 104$	25	27	17	17	13	13	9								102
106	225	27 27	17	19	13	13			9	9					106
108	07	07	1.0	- 10	10	1.	11	11				0			108
110	27	29	17	19	13	15	11	11	9	9	1	9	1	1	$110 \\ 112$
114	27	29 29	10	10	13	15			-		7	9	7	7	114
116	00	00	19	19	1.5			10							116
$118 \\ 120$	29	81	19	21	15	15	11	13	9						$118 \\ 120$
122	29 31	81 81	19	21	15	15	_11	13	9	11					122
124	81	81	21	21	1.**	17					9	9		0	124
$\frac{120}{128}$	31		21	21	15	11	13	13			9	9	1	9	$120 \\ 128$
130	81 83	83 33	21	23	15	17			11	11			7	9	130
132	83	82	01	00	10	10	13	13		11					132
$\frac{134}{136}$	33	85	21	23	17	17			11						134
138	88 85	85 36	20		_17	17	13	15			9	11			138
140	85	96	23	23	1.P7	10	10			10	0				140
$142 \\ 144$	35	87	23	25		19	13	15	11	13	9	11	9	9	142
146	85 87	87 37	23	25	17	19			11	13			9	9	146
148	87	87	25	25	10	10	1.5	15							148
150 152	37	89	25	25	19	19	15	15			11	11			150
154	87 89	89 89	25	27	19	19			13	13					154
156	39	89	95	07	10	01	15	17	10	10	11	11	0	11	156
$150 \\ 160$	39	41	20	27	19	21	.10	-11	10	10			IJ	11	$100 \\ 160$
162	89 41	41 41			19	21	15	17					9	11	162
164	41	41	27	27	91	01		-	10	15	11	10			164
168		43	41	49	41	41	17	17	_10	10	11	19		_	$100 \\ 168$
170	41 43	43 43	27	29	21	21			13	15	11	13			170
172	43	43	29	29	91	93	17	17					11	11	172
176	43	45	29	29		20	5 7						11		174
178	43 45	45 45	29	31	21	23	17	19	15	15			11	11	178
180	45	45	20		02	93	17	10	15	15	13	13			180
184	45	47	31	$\frac{31}{31}$		- 20	-11	10	10	10	13	13			182 184
186	45 47	47			23	23									186
188	47	47	31	$\frac{31}{22}$	02	95	19	19	15	17			11	12	188
192	47	49	01	00	40	20	19	19	10	11			11	10	190
194	47 49	49 49	31	33	23	25		1.1	15	17	13	15	11	13	194
196 198	49	49	33	33	25	95	10	01			10	15			196
200	49	51	33	33	20	40	19	- 21			13	10			200
	4	4 6			8	3	1	0	1	2	1	4	- 1	6	



TAE	BLE O	OF T	WO-0	CIRC	UIT,	SINC	LE V	VIND	ING	S, FO	R DI	RUM	ARM	ATU	RES.		
TORS					FRO	NT A	ND B	ACK H	PITCH	HES.					TORS		
DUC	4	í		6		8	1	0	1	2	1	4	1	6	DUC		
CON	PO	LES	PO	LES	PC	LES	PO	LES	PO	LES	PO	LES	PO	LES	CON		
No. OF	F	В	F	B	F	B	F	В	F	В	F	B	F	В	No. OF		
202	49 51	61 61	33	35	25	25	19	21	17	17					202		
206	61 51	51 68	33	35	25	27	01	01	17	17	15	15	13	13	206		
208	61 68	53 58		25	25	27	21	21			10	10	13	13	208 210 010		
212	68 63	68 50	35	37	27	27	21	21	17	19	10	10			212		
216	63 55	55 55	35	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													
220	55 55	<u>55</u> 57	31	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													
224	65 57	67 87	37 37	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													
228	57 57	67 89	37	39	29	29	23	23	19	19					228		
232	87 69	69 59	39	39	29	29	23	23			1.5				$\begin{array}{r} 232 \\ \hline 234 \\ \hline \end{array}$		
236	69 59	69 61	39 39	<u>39</u> 41	29	31	23	25	19	21	17	17	15	15	236		
240	69 61	61 61	39	41	29	31	23	25	19	21	17	17	15	15	$\frac{240}{242}$		
244 246	61 61	61 63	41	41	31	31	0"	05	-						$\frac{244}{246}$		
248 250	61 63	68 63	41 41	41 43	31	31	20	20	21	21	17	19			$\frac{248}{250}$		
252	63 63	63 65	41	43	31	_ 33	25	20	21	21	17	19	15	17	252 254		
258	63 55	65 65	43	43	31	33	25	27					15	17	258		
260	65 85	65 67	43 43	43 45	33	33	25	27	21	23	10	10			260		
264 266	65 67	67 67	43	45	33	33	- 07	07	21	23	19	19			264 266		
270	67 67	67 69	40	40	33	35	21	- 41			19	19	17	17	$\frac{208}{270}$		
$\frac{212}{274}$	67 69	69 69	45	47	33	35	41	41	_ 23	23			17	17	274		
278	69 69	69 71	45	47	35	35	27	29	23_	23	19	21			278		
282	69 71	71 71	41	47	35	35	27	29			19	21			282		
286		71 73	47	.49	35	37	00	00	23	25			_17	19	286		
200	71	78 78	47	49	35	37	29	29	23	25	01	01	17	19	200		
292 294 296	7 <u>3</u> 73	78	49	49	37	37	29	29			-01	21			292		
298	78	78 75	49	51	37	37	29	31	25	25					298		
	4	ť -	(3		8	1	0	1	2	1	4	1	6	000		

TAE	BLE C	DF T	WO-0	CIRC	UIT,	SINC	LE V	VIND	INGS	5, FO	RDF	RUM	ARM	ATU	RES.
TORS			h		FRC	DNT A	ND E	BACK	PITC	HES	11				TORS
DUC		4		6		8	1	0	1	2	1	4	1	6	DUC
CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	Pol	LES	CON
No, 01	F	В	F	B	F	В	F	B	F	B	F	В	F	B	No. OF
302	75 75	75 77	49	51	37	39	29	31	25	25			19	19	302
304	75	77	51	- 21	37	39					21	23	19	19	$304 \\ 306$
$\frac{308}{310}$	77	77	<u>51</u> 51	51	39	39	31	31	25	27	21	23			308
312	72	79	MI	50	- 00		31	31				20			312
$\frac{314}{316}$	79	79	53	53	39	39			25	27					$\frac{314}{316}$
318 320	79	79 81	53	53	39	41	31	33			03	02	19	21	318
322	79 81	81 81	53	55	39	41	31	33	27	27	20		19	21	322
$\frac{324}{326}$	81 · 81	81 83	53	55	41	41			27	27	23	23			$\frac{324}{326}$
<u>328</u> 330	<u>81</u>	83	55	55	41	41	33	33							328
332	83	88	55	55		11	33	33							332
334 336	83 83	85	55	57	41	43			27	29	23	25	21		334
338	83 85	85 85	55	57	41	43	33	35	27	29	23	25	21	21	338
$\frac{340}{342}$	85 86	85 87	07	51	43	43	33	35							$\frac{340}{342}$
$\begin{array}{r} 344 \\ 346 \end{array}$	85	81 97	57	$\frac{57}{59}$	43	43			29	29					344
348	 	Q7			10		35	35	40		25	25	24		348
$\frac{350}{352}$	87	89	59	59	43	45	35	35	29	29	25	25	21	23	$\frac{350}{352}$
$\frac{354}{356}$	87 80	89 89	59	50	43	45							21	23	354
358	89 89	89 91	59	61	45	45	35	37	_29	31					358
$\frac{360}{362}$	89 91	91 91	59	61	45	45	35	37	29	31	25	27			$\frac{360}{362}$
364	91	91	61	61	1.5							07	. 00		364
368	91	93	.61	61	49	41	37	37			25	27	23	23	$\frac{366}{368}$
$\frac{370}{372}$	91 03	93 93	61	63	45	47	37	37	31	31			23	_23	370
374	93 93	93 95	61	63	47	47			31	31					374
378	93 95	95 95	03	63	47	47	37	39			27	27			$\frac{376}{378}$
380	95	95	63	63	47	40	27	20	91	22	27	27		05	380
384	95	97	00	00	± (49	01	00		00			23	_25	$\frac{382}{384}$
$\frac{386}{388}$	95 97	97 97	<u>63</u> 65	$\frac{65}{65}$	47	49	39	39	31	33			23	25	386
390	97 97	99 99	0 P	05	49	_49	00	00			27	29			390
<u>392</u> <u>394</u>	97 99	99 99	65	67	49	49	39	39	33	33	27	29			$\frac{392}{394}$
<u>396</u> 398	99	99	65	67	10	51	30	41	22	22			05	05	396
400	99	101	67	67	30	01	09			00			40	20	400
	4	ŧ	(3	8	3	1	0	1	2	1	4	1	6	

TA	BLE	OF T	WO-	CIRC	CUIT,	SIN	GLE	WINI	DING	S, FC	DR D	RUM	ARM	IATU	RES.
rors					FRC	NT A	ND B	ACK	PITCI	HES					rors
CONDUCT	Po	4 LES	PO	6 DLES	Po	8 LES	1 PO	0 LES	1 Po	.2 LES	1 Po	4 LES	1 P0:	6 LES	CONDUC
No. OF	F	В	F	В	F	B	·F	В	F	B	F	В	F	В	No. OF
402	93 101	101	67	67	49	51	39	41			90	90	25	25	402
406	101 101	101 103	67	69	51	51			33	35	20	40			404
408 410	101 103	108 103	67	69	51	51	41	41	33	35	29	29			$\begin{array}{r rrr} 408 \\ \hline 410 \end{array}$
412	108	108	69	69	51	53	41	41					25	27	412
416	103	105	69	69	51		41	49	95	05	00	01	05	07	416
418	105	105	69	11	51	00	41	40	00	30	29	31	20	21	418
$\begin{array}{r} 422 \\ 424 \end{array}$	105	106	69 71	71 71	53	53	41	43	35	35	29	31			422
$\frac{426}{428}$	105 107	107 107	71	71	53	53	43	43							426
430	107 107	107 109	71	73	53	55	10	10	35	37			27	27	430
$\frac{432}{434}$	107	109	71	73	53	55	43	43	35	37	31	31	27	27	<u>432</u> <u>434</u>
436	109	109	73	73	55	55	43	45			31	31			436
440	109	111	73	73			10	10	07	07					440
$\frac{442}{444}$	111	111	73	15	55	50	43	45	37	31					442
$\frac{446}{448}$	m	111 113	73	75	55	57	45	45	37	37	31	33	27	29	$\begin{array}{r} 446 \\ 448 \end{array}$
450	111 113	118 113	75	75	55	57	45	45			31	33	27	29	450
454	118 113	113 115	75	77	57	57	40	40	37	39					454
456 458	118 115	115	75	77	57	57	45	47	37	39					$\frac{456}{458}$
460	115	115	77	77	57	59	45	47			33	33	90	90	460
464	115	117	77	77		50	- 10	- X4			33	33	40	40	464
468	117	117		19	57	59	47_	47	39	39			29	29	$\frac{466}{468}$
$\frac{470}{472}$	117	117 119	77 79	79 79	59	59	47	47	39	39		•			470
474	117 119	119 119	79	79	59	59					33	35			474
478	119 119	119 121	79	81	59	61	47	49	39	41	33	35	29	31	478
$\frac{480}{482}$	119 121	121 121	79	81	59	61	47	49	39	41			29	31	$\frac{480}{482}$
$\frac{484}{486}$	121	121	81	81	61	61									484
488	121	123	81	81	61	61	49	49		41	35	35			488
492	123	198	01	00	01	10	49	49	41	41	35	35			490
494 496	123	123	81 83	83	61	63			41	41			31	81	$\frac{494}{496}$
498 500	123 125	125	83	83	61	63	49	51					31	31	498
	4	, t	6	3	8	3	1	0	1	2	1	4	1	6	000

TAB	LE C	F TV	vo c	IRCU	JIT, S	SING	LEW	IND	INGS	6, FO	RDR	UM	ARM	ATUR	RES.
TORS					FRO	DNT A	AND	BACK	PITC	CHES					TORS
DUC	. 4	Ł	6	3	8	3	1	0	1	2	1	4	1	6	DUCT
CON	PO	LES	PO	LES	PO	LES	PO	LES	Po	LES	PO	LES	PO	LES	CON
No. 01	F	В	F	В	F	В	F	В	F	В	F	В	F	B	No. 0F
502	125 125	125 127	83	85	63	63	49	51	41	43	35	37			502
506	125 127	127 127	83	85	63	63	E1	51	41	43	35	37			506
508 510 510	127 127	127 129	00	00	63	65	51	51					31	33	510
512 514 516	127 129	129 129	85	87 87	63	65		- 16	43	43	07	05	31	33	512
518	129 129	129 131	85	87	65	65	51	53	43	43	37	37			516
<u>520</u> <u>522</u>	129 131	131 131	87	- 07	65	65	51	53			37	37			$520 \\ 522 \\ 524$
524 526	131 . 131	131 133	87	89	65	67		50	43	45			33	33	<u>524</u> <u>526</u>
$\frac{528}{530}$	131 133	133 133	87	89	65	67	00	50	43	45	37	39	33	33	<u>530</u>
<u>534</u>	133 138	133 135	89	89	67	67	53	53			37	39			<u>532</u> 534
538	133 135	185 135	<u>89</u> 89	$\frac{89}{91}$	67	67	53	55	45	45					<u>. 536</u> 538
540	135 135	135 137	89	91	67	69	53	55	45	45			33	35	$\frac{540}{542}$
546 546	135 137	137 137	91	91	67	69					39	39	33	35	$\frac{544}{546}$
$548 \\ 550 $	137 137	137 139	$\frac{91}{91}$	91 93	69	69	55	55	45	47	39	39			$\frac{548}{550}$
<u> </u>	137 139	139 139	91	93	69	69	55	55	45	47					552 554
558 578	139 139	139 141	93	93	69	71	55	57			39	41	35	35	556 558
<u>560</u> 562	139 141	141 141	<u>93</u> 93	93 95	69	71	55	57	47	47	39	41	35	35	560 562
<u>566</u>	141 141	141 143	93	95	71	71			47	47					564 566
<u> </u>	141 143	143	95	95	71	71	57	57							<u>568</u> 570
574	143 143	148 145	95 95	95 97	71	73	57	57	_ 47	49	41	.41	35	37	572
578	143 145	145 145	95	97	71	73	57	59	47	49	41	41	35	37	576 578
582	145 145	145 147	07	91	73	73	57	59							580 582
586	146 147	147 147	97	99	73	73	50	50	49	49	41	43			586
590	147 147	147 149	97	99	73	75	59	59	49	49	41	_43	37	37	588
<u>594</u> 596	147 149	149 149	99	99	73	75	09	-09					37	37	592 594
598	149 140	149 151	99	101	75	75	59	61	49	51	49	42			596 598
1	4	ť	(5		8	1	0	1	2	43	4	1	6	000

ТА	BLE	OF T	wo	CIRC	UIT	SINC	LE V	VINC	DING	S FO	R DR	UM	ARM	ATUF	RES.
TORS					FRC	NT A	ND E	BACK	PITC	HES					TORS
CONDUC	Po	4 LES	Po	3 LES	PO	B LES	1 POI	0 LES	1 P0	.2 LES	1 P0	4 LES	1 POI	6 LES	CONDUC.
40. OF	F	В	F	В	F	В	F	В	F	В	F	В	F	В	No. OF
602 604	149 151	151 151	99 101	101 101	75	75	59	61	49	51	43	43			602 604
606 608	161 161	151 153	101	101	75	77	61	61					37	39	606 608
$\begin{array}{r} 610 \\ 612 \\ \end{array}$	151 153	153 153	101	103	75	77	61	61	51	51			37	39	$\begin{array}{r} 610 \\ 612 \\ \end{array}$
614 616 619	153	155	101 103	103	77	77	<i>C</i> 1	<u> </u>	51	- 51	43	45			616 618
620 622	155	155 155	103 103	103 105	77	79	61	63	51	53		40	39	39	$\begin{array}{r} 610\\ 620\\ 622 \end{array}$
$\begin{array}{c} 624 \\ 626 \end{array}$	155 157	157 157	103	105	77	79			51	53			39	39	624 626
628 630	157 157	157 159	105	105	79	79	63	63			45	45			<u>628</u> <u>630</u>
632 634 636	167 159	159 159	105	105	79	79	63	63	53	53	40	40			634 636
638 640	159 159	159 161	105 107	107 107	79	81	63	65	53	53			39	41	638 640
642 644	169 161	161	107	107	79	81	63	65			45	47	39	41	$\begin{array}{r} 642 \\ 644 \end{array}$
646 648 650	161 161	163	107	109	81	81	65	65	53	55	45	47			646 648 650
652 654	163	168 168	107	109	81	83	65	65	- 00	00			41	41	$\begin{array}{r} 650 \\ 652 \\ 654 \end{array}$
656 658	163 165	165 165	109 109	109 111	81	83	65	67	55	55	47	47	41	41	656 658
660 662	105 165	108 107	109	111	83	83	65	67	55	55	47	47			660 662
664 666 668	165 107	167	111	111	83	83	67	67							664 666 668
$\begin{array}{r} 670 \\ 672 \end{array}$	167 167	167 109	111	113	83	85	67	67	55	57	47	49	41	43	670 672
674 676	167 169	159 169	111 113	113 113	83	85			55	57	47	49	41	43	674 676
678 680 699	169	171	113	113	85	85	67	69	57						678 680
684 686	171	171 171 173	113	115	85	87	01	09	57	57	49	49	43	43	684 686
688 690	171	172 173	115	115	85	87	69	69			49	49	43	43	688 690
692 694	17# 178	173 175	115 115	115 117	87	87	69	69	57	59					692 694
698 700	173 175	175 175	115 117	117 117	87	87_	69	71	57	59	. 49	51			696 698 700
	4	ť	(3	8	3	1	0	. 1	2	1	4	1	6	







WINDING TABLES FOR TWO-CIRCUIT, DOUBLE WINDINGS FOR DRUM ARMATURES.



TA	BL	ΕO	FT	wo)-CI	RC	UIT	, D	OUI	BLE	w w	ND	INC	GS,	FO	R D	RU	MA	RM	AT	UR	ES.
rors							F	RON	IT A	ND	BA	CK	PITO	CHE	S							rors
CONDUC	P	4 OLI	ES	P	6 OL	ES	P	8 POLI	ES	P	10 POLE	ES	F	12 OLI	ES	P	14 OLE	ES	P	16 OLE	ES	CONDUCT
No. OF	F	RÉ-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	No. OF
102	05															7	Q	7				102
$104 \\ 106$	20	1 W	27	17	00	19			-	9	00	11	9	0	9							104
108	26 27	00	27 29				13 13	88	13 15							7	00	9	7	Q	7	108
110	27	0	27	19	0	19	1						0	(2)	0							110
114	29	00	29	11	00	10				11	Ø	11	3	100	9							112
116	27 29	00	29 31	19	00	21	13 15	8	15 15	11	00	13	9	00	11	7	00	9	7	Q	7	116
$118 \\ 120$	29	0	20	19	(W)	19																118
$\overline{122}$	01		01	21	Ø	21										9	Ø	9				122
124	29 31	00	81 88	19	00	21	15	8	15	11	00	13	9	00	11_				7	00	9	124
$120 \\ 128$	31 83	0	81 83	21	00	23				10		_10	11	0	11		-					120
130	81		83	21	Ø	21	15	0.0	17							9	Q	9				130
132	33	00	85	23	0	23	17	60	17	13	0	13							7	00	9	132 134
136	88 85	0	88 85	21	00	_23				13	00	15	11	0	11	9	00	11				134
138	88		85	0.9		05	17	6	17				11		10				0		0	138
$140 \\ 142$	35	00	87	$\frac{23}{23}$	Q	$\frac{20}{23}$	17	7 60 17 7 00 19					11	00	10				9	<u>w</u>	9	140
144	35 87	0	85 87							13	00	15				9	00	11				144
$\frac{146}{148}$	35	00	87	$\frac{25}{23}$	00	$\frac{25}{25}$	17	0.0	19	15	Ø	15	11	0.0	13		-		9	0	9	146
150	01		09			10	19		19						10	11	0	11				150
152	87 89	0	87 89	25	00	27				15	0	15	13	Ø	13					_		152
$154 \\ 156$	87 89	00	89 41	20	00	20	19	80	19	$15 \\ 15$	00	$\frac{15}{17}$							9	00	11	154
158				27	Ø	27	10									11	Ø	11				158
$160 \\ 162$	41	0	41	25	00	27							_13	0	13							$160 \\ 169$
164	39 41	00	41	27	00	29	19	88	£1 21	15	00	17	13	00	15	11	00	13	9	00	11	164
166	41	(0)	41	27	0	27				17	Ø	17										166
170	43	00	43	29	Ø	29																170
172	41 43	00	43 45	27	00	29	21 21	80	21 23				13	00	15	11	00	13	11	0	11	172
174	43	(1)	43	90	00	21				17	Ø	17	15	0	15						_	174
178	45		45	29	Q	29				11	00	19	10		15	13	Ø	13				178
180	43 45	00	15 17	01	6	01	21 23	88	23 23										11	Ø	11	180
182	45	0	45	$\frac{31}{29}$	00	31				17	00	19	15	0	15							182
186	- 11									19	Ø	19	10		1.0	13	Ø	13				186
188	45	00	47	31	00	33	28 28	88	23 25				15	00	17		_]	11	00	13	188
192	47	0	47	-01	00	51										13	00	15				190
194	47		40	33	Ø	33	23 0.0 25 1			19	0	19										194
$196 \\ 198$	76	00	61	31	00	33	23	65	25 25	19	00	21	15	00	17				11	00		196
200	49	0	4º 33 00 35							17	0	17	13	00	15			_	200			
	<u>4</u> 6				8			10			12			14			16					



	1	rwo	о-с	IRC	CUI	T, C	ου	BL	EW	/INI	DIN	GS,	FC	RI	DRU	JM	ARI	MA	ΓUF	RES		
ORS							F	RON	IT A	AND	BA	CK	PIT	CHE	CS							ORS
CONDUCT	P	4 OLI	ES	P	6 OLI	ES	F	8 POLI	ES	F	10 POLE	ES	P	12 OLI	ES	F	14 POLI	ES	P	16 OLE	ES	CONDUCT
No. OF	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	No. OF
202 204	49	00	£1	33	0	_33	25	R	35	19	00	21							13	0	13	202
206	- <u>1</u>	0	51	35	0	35	40			21	0	21	17	0	17	15_	0	15				206
210	51	00	63	35	0.0	37	25	9.0	27				17		10				12	0	12	210
214	68		60	35	0	35	27		27	21	0	21	11	00	10	15	0	15	10		10	212
216	65	Ø	56	37	0	37			-	21	00	23										$\begin{array}{ c c c c }\hline 216\\\hline 218\end{array}$
220 222	68 55	00	55	35	00	37	97 97	88	27 29				17	00	_19	15	00	17	13	00	15	220 222
224 226	65 57	0	55 57	37	00 @	39 37				21 23	00 0	23 23	19	Ø	19							224 226
228 230	65 57	00	57 59	39	0	39	27 29	88	22 29							15	00	,17	13	00	15	228
232	67 69	0	57	37	00	39				93	0	23	19	0	19	17	0	17				232
236	57 59	00	59 61	39	00	41	29	88	29 31	23	00	25	19	00	21				15	Ø	15	236
230	59 81	Ø	59 61	09		59								•								238
242 244	59 51	00	61 63	41 39	00	41 41	29 31	88	81 81	23	00	25	19	00	21	17	Ø	17	15_	Ø	15	242 244
$\frac{246}{248}$	63	Ø	61 63	41	00	43				25	0	25	21	0	21	17	00	19				246
$\frac{250}{252}$	61 68	00	63 65	41	0	41	31 X1	60	81 33						_				15	00	17	$\frac{250}{252}$
$\frac{254}{256}$	68 66	Ø	63	43	00	43				25 25	00	$\frac{25}{27}$	21	0	21	17	0.0	19				254
$\frac{258}{260}$	63	0.0	55	13	0.0	45	8)	0.0	33				01	00	02	1.			15		17	258
262	65	0	65	43	Ø	43	33		88	05		07	41	00	20	19	0	19	10	00	16	262
266	67	00	67	45	0	45	88	6	22	25	0	27	01		0.0				107	-	1.7	266
270	67	00	69	40	00	40	83	60	85				21	00	23	19	0	19	17	6	17	268
272	69	(W)	69	45 45	00 @	47				27	0	27	23	Ø	23							$\frac{272}{274}$
276 278	67 59	00	69 71	47	0	47	33 35	88	35 35	27	00	29				19	00	21	17	0	17	276
280 282	69 71	0	89 71	45	00	47							23	0	23		-					$\frac{280}{282}$
284 286	69 71	00	71 73	47	00	49 47	35 35	8	85 37	27	00	29 29	23	00	25	19	00	21	17_	00	19	284
288 290	71 78	0	71	49	0	49										91	0	91				288
292	71	00	76 75	47	00	49	85 87	88	817 877	00			23	00	25	21		21	17	00	19	292
296	73 75	0	78 75	49	00	51				29	00	29 31	25	0	25			-				294 296
300	78 75	49 00 49 00 75 71				49	87 87	8	67 89			5	1			21	Q	21	19	0	19	298 300
	4 6			8			10			12			14			16						

		тw	0-0	IRC	CUI	т, І	οοι	JBL	EV	VIN	DIN	IGS	, F(DR	DR	UM	AR	MA	TU	RES		
TORS							FF	RON	ΤА	ND	BAC	CK F	PITC	HE	S							TORS
CONDUC	P	4 OLI	ES	P	6 OLI	ES	P	8 OLE	ES	10 Poles			P	12 OLE	ES	P	14 POLI	ES	P	16 OLE	ES	CONDUCT
No. 0F	F	RE-	В	F	RE-	В	F	F ENTRANCY B F ENT			RE-	В	F ENTRANCY B			F ENTRANCY B			F RE- ENTRANCY B			No. OF
302	75	-	75	51	0	51				00	0.0	01	05	0	05	01		0.2				302
304	. 17	00		49	00	01_				31	Q	31	20	00	20	21	00	20				304
308 310	75	00	46	$\frac{51}{51}$	00	53	39	60	39				25	00	27				19	0	19	308
312	77 79	Ø	77	50		F9				01		01				21	00	23				312
314	73	00	79 81	51	00	53	89 39	60	89 41	31	00	31	25	00	27				19	00	21	314
318	79	(1)	7.9	53	0.0	55							97	0	07	23	0	23				318
322	81		- 81	53	0	53							-41	00								322
$\frac{324}{326}$	14	00	81	55	0	55	41	66	1	31	00	33				23	0	23	19	00	21	324
328	81 83	Q	81 83	53	00	55							27	Ø	_27_							328
332	81 83	00	83 85	55	00	57	41 41	88	41 43			_	27	00	29	23	00	25	21	0	21	332
334	88	0	83	55	0	55				33	Q	33										334
338			68	57	0	57				00	00	00_										338
$\frac{340}{342}$	85	00	87	55	00	57	41 43	00	43		-		27	00	29	23	00	_25_	21	Q	21	340
344		Ø	85 87	57	00	59				33	00	35	29	0	29	05		05				344
348	86 87	00	87 89	51	<u>w</u>	01	43 43	88	43 45	30		30				20	0	25	21	00	_23	346
$\frac{350}{352}$	87	0	87	59	00	59		_					29	0	29							350
354	09		08			01	42	0.0	45	35	0	35	20			25	Ø	25				354
$\frac{356}{358}$	- 30	_00	91	<u> </u>	00	61 59	18	60	10	35	00	37_	29	00	_31_				21_	00	_23_	356
360	80 91	Ø	89 91	61	0	61					-					25	00	27			_	360
364	89 91	00	91 93	59	00	61	45 45	88	45 47	35	00	37	29	00	31				23	Ø	23	364
$\frac{366}{368}$	91	0	03 91	61	00	63				37_	0	37	31	0	31	25	00	27				366
370	01		02	61	0	61	15	0.0											00		00	370
374	93	00	95	63	0	63	47	00	47	37	0	37	-			27	0	27	23	6	23	372
376	93 96	0	93 95	61	00	63_				37	00	39	31	0	31							376
380	93 95	00	96 97	63	00	65	47	ଞ	17		_		31	00	33				23	00	25	380
$\frac{382}{384}$	95	0	96	63	0	63		-		37	00	39	-		_	27	0	27				382
386	05		97	65	0	65	47	0.0	40	_39	Ø	39										386
390	97	00	<u> </u>	63	00	65	49	Ğ	49		-		31	00	33	27	00	29	23	00	25	388
392 394	97 99	Ø	87	65	00	67				30	(1)	20	33	0	33	-						392
396	97 99	00	99 101	-00		00	49 49	ଞ	49 51	39	00	41				27	00	29	25	0	25	396
398 400	99 101	Q	99	67 65	00	67 67			-	No.	-		33	0	33			-				398 400
	4				6			8			10			12			14			16		

		TW	0-0	CIR	CU	IT, 1	DOI	UBL	LE \	VIN	IDIN	VGS	, F	OR	DR	UM	AR	MA	TU	RES	5.	
TORS							F	RON	IT A	ND	BA	CK I	PITO	CHE	S							TORS
CONDUC	P	4 OLI	ES	P	6 OLI	ES	P	8 OLH	ES	F	10 POLI	ES	P	12 POLES			14 OLE	ES	P	16 OLE	S	CONDUC
No. OF	F	RE-	В	F	F ENTRANCY B			RE- ENTRANCY B		F	F ENTRANCY B		F ENTRANCY B		F ENTRANCY B		F	F ENTRANCY B		No. OF		
402 404	09 101	00	101 103	67	00	69	49 51	88	51 51	39	00	41	33	00	35	29	@	29	25	0	25	402 404
406 408	101	0	101 103_	67	0	67		-		41	0	41										406 408
410 412 414	101 103	00	103	67	00	69	51 51	8	51 63	41	0	41	33	00	35	29		29	25	00	27	410 412 414
416 418	108 105	0	108 105	69 69	00	71 69				41	00	43	35	0	35	29	00	31				416 418
420 422	108	00	105	71	Ø	71	51 53	68	53 53	41			05		95	- 20		01	25	00	27_	420 422
424 426 428	107	00	107	71	00	71	53	88	53	$\frac{41}{43}$	0	<u>43</u> <u>43</u>	35	00	35	29	00	51	27	Q	27	424 426 428
430 432	107	Ø	107	71	0	71	00									31	Q	31				430 432
434 436	107	00	109 111	73	00	73 73	63 55	38	65 55	<u>43</u> <u>43</u>	@ 00	43 45	35	00	37				27	0	27	434 436
438 440 442	109	0	109	73	00	75							37	0	37	31	Ŵ	31				438 440 442
444 446	109 111	00	111 113	75	Q	75	55 55	8	55 57	43 45	00 @	45 45			-	31	00	33	27	00	29	444 446
448 450	111	0	117	73	00	75							37	0	37							448 450
452 454 456	113	00	113	75	@	77	57	60	57	45	0	45	37	00	39	31	00	33	27	00	29	452 454 456
458 460	115	00	115	77 75	@	77	57 57	R	\$7	10		- T 1	37	00	39	33	Ø	33	29	@	29	458 460
$\frac{462}{464}$	115	Ø	115	77	00	79				45	00	47	39	Ø	39							462 464
466 468 470	115 117	00	117 119	79	@	77	57 59	88	59 59	47	@	47	-			33	<u></u>	33	29	Ø	29	466 468 470
472 474	217 119	0	117 119	77	00	79				47	0	47	39	Ō	39	33	00	35				472
476 478	117	00	119	79 79	00 @	81 79	59 59	æ	59 61	47	00	49	39	00	_41			0.7	29	00	31	476 478
480 482 484	119	00	121	81	00	81 81	69	8,8	61	47	0.0	40	30	0.0		33	00		-20	00	21	480 482 481
486	121 121 123	Q	123 121 123	81	00	83	61		61	49	Ø	49	41	Ø	41	35	6	35	_43	00	01	486 488
490 492	121 123	00	123 125	81	0	81	61 01	ଝ	61 63								-		31	0	31	490 492
494 496 498	123 125	0	123 125	83 81	00	83			4	49 49	00	19 51	41	0	41	35	0	35			-	494 496 498
500	123 125	00	125 127	83	83 00 85			61 0.8 63 63 08 63					41	00	43	35	00	37	31	0	31	500
	4			6				8			10			12	2	-	14		16			

		TW	0-0	IRC	CUI	т, Г	οοι	JBL	EV	VIN	DIN	IGS	, F(DR I	DRI	JM	AR	MA	TUI	RES		
SRO.							FI	RON	TA	ND	BA	CK I	PITO	CHE	S			5				ORS
CONDUCT	P	4 OLI	ES	P	6 OLI	ES	P	8 OLE	CS	P	10 OLE	S	P	12 OLE	cs	P	14 OLE	ES	P	16 OLE	CS	CONDUCT
No.OF	F	RE-	В	F	RE-	B	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	No. OF
502	125	0	125	83	0	83				4.9	00	51										502
506	127	00	127	85	Ø	85	6.9		6.9	51	Ø	51	4.1		10	05		07	01		00	506
508	127	00	129	83	00	85	63	88	65				41	00	43	30	00	31	31	00	33	510
512	127 129	Q	127	85	00	87				51	0	51	43	0	43	37	0	37				512
516	127 129	00	129 131	00			63 65	68	05 05	51	00	53				01			31	00	33	516
$518 \\ 520$	129	0	129	87 85	00	87		-					43	Q	43							518 520
522	129	0.0	131	87	0.0	89	65	R	65	51	0.0	53	13	0.0	45	37	Ø	37_	33	0	33	522
526	131		- 133	87	0	87	65	00	07	53	Ø	53	10		10	07			00			526
528	131	Ø	133	89	0	89										37	00	39				528
532	131 133	00	133 135	87	00	_89	65 07	සි	67 67	59	0	59	43	00	45				33	Ø	33	532
536	133 135	0	183 135	89	00	91				53	00	55	45	0	45	37	00	39				536
538	133	0.0	136	89	Ø	89	67	8	67										33	00	35	538
542	130		137	91	0	91	0,		00				15			39	Ø	39				542
$\frac{544}{546}$	130	0	135	89	00	91				53	00	55 55	45	Q	45							544 546
548	135	00	137 139	91	00	93	67 69	600	69 69				45	00	47	20	0	20	33	00	35	548
552	137 139	Ø	137 139	51		51										00		00				552
$554 \\ 556$	137	00	139	93	00	93	69 69	83	69 71	55	0	55	45	00	47	39	00	41	35	Ø	35	554 556
558	139		189	02		05							47		4.57							558
562	141	w l	141	93	Q	93							41	. Q	47							562
$\frac{564}{566}$	139	00	141 143	95	0	95	71	23	71	55	00	57				39	00	41	35	Ø	_35_	564
568	141 143	0	141 143	93	00	95							47	0	47	41	0	41				568
572	141 143	00	143 145	95	00	97	71 71	ଞ	71 73				47	00	49	41	00	41	35	00	37	572
574	148	0	143	95	Q	95				57	0	57										574
578	142		145	97	0	97	71	0.0	72				17		10	41	Ø.	41			07	578
580	145	00	147	95	00	97	73	ර්ග්	78				47	00	49_				35	00	37	580
584	145 147	0	145 147	97	00	99				57	00	59	49	Ø	49	41	00	43				584
588	145 147	00	147 149	01		01	78 73	80	78 75	09	00	00							37	Ø	37_	588
<u>590</u> 592	147	Ø	147	99	00	99				-			49	0	49	41	00	43		-		590
594	147	0.0	149	00	00	101	78	0.0	75	59	0	59	40		51				97	0	97	594
598	149	00	151	99	0	99	75	00	75	09	00	01	49	00	51	43	Ø	43	51		01	598
600	151	0	149					1								-						600
	4			6				8			10			12			14			16		

		тw	0-0	CIR	CU	IT, I	DOU	JBL	E V	VIN	DIN	NGS	, F	OR	DR	UM	AR	MA	TU	RES	5.	
ORS				24			F	RON	T A	ND	BA	CKI	PITO	CHE	S							rors
CONDUCT	P	4 OLI	ES	P	6 OL:	ES	P	8 OLI	ES	P	10 Poles			12 Poles			14 POLES			16 OLE	ES	CONDUC
No. OF	F	RE-	CY B F RE- ENTRANCY B			F ENTRANCY B			F	RE-	В	F	RE-	B	F	RE-	В	F	RE-	В	No. OF	
602	149		151	101	0	101	75	6	7.5	50		01	40		51				07		20	602
606	161	00	153	09	00	101	76	00	77	61	0	61	49	00	01	43	0	43	01		- 59	606
608	151 153	0	161 163	101	00	103						_	51	Ø	51							608
612	161 153	00	158 155			101	75 77	සි	-17 77							43	00	45	37	00	39	612
614	153	0	158	$103 \\ 101$	00	$103 \\ 103$				61	@ 00	$\begin{array}{c} 61 \\ 63 \end{array}$	51	0	51							$\frac{614}{616}$
618	16.8		165	1.09		105	77	-75-	77				P1		10	40		1.	20		- 00	618
620	165	00	157	103	00	103	22	676	79				- 51	00	03	43	00	40	39	<u>a</u>	39	620
624	153 167	0	155 157	105	0	105	-			61	00	63				45	0	45				624 626
628	155 157	00	157 159	103	00	105	77 79	88	79 79	00		00	51	00	53	10		10	39	Q	39	628
630	157 169	0	167 169	105	00	107							53	0	53			-				630
634	157		159	105	Ø	105	79	0	79	63	0	63	-			45	Q	45	00		41	634
638	159	00	161	107	0	107	79	60	81	03	00	69							39	00	41	638
640	169 161	0	159 161	105	00	107							53	Ø	53	45	00	47				640
644	159 161	00	161 16 3	107	00	109	79 81	8	81 81	63	00	65	53	00	55				39	00	41	644
646 648	161 163	0	101 168	107	Q	107				65	@_	65				45	00	47				$\frac{646}{648}$
650	161	0.0	163	109	0	109	81	Q	81				52	0.0	55				41	0	41	650
654	163	00	165	101	00	105	81	00	88	65	0	65	00	00	00	47	0	47	41	_00	41	654
656 658	163	0	168	109	00	111 109				65	00	67	55	Q	55							$\frac{656}{658}$
660	163 165	00	165				81 83	සී	88 83										41	Ø	41	660
662	165	Ø	165	109	00	111				65	00	67	55	Ø	55	47	Ŵ	47				$\frac{662}{664}$
666	165	-	167	111		119	88	6	88	67	Ø	67	PP		E.7	47		40	41		49	666
670	167	00	169	111	0	115	83	00	85				00	00	01	41	00	49	41	00	40	670
672	167	0	167 169	113	0	113				67	0	67		_	•							672
676	167 169	00	169 171	111	00	118	83 85	88	86 85	67	00	69	55	00	57	47_	00	49	41	00	,43	676
678	169	0	169 171	113	00	115							57	0	57							678
682	169		171	113	0	113	85	()	85	07		<u> </u>				49	Q	49	10		40	682
686	171	00	179	115	0	115	85	6.9	87	69	@	69							43	6	43	686
688	171	0	171	113	00	115							57	Ø	57	49	0	49				688
692	171 178	00	173	115	00	117	85 37	සි	87 87				57	00	59	20		10	43	Ø	43	692
$\frac{694}{696}$	178	Ô	178	115	0	115				69 69	00	69 71				49	00	51				694 696
698	178	0.0	175	117	0	117	87.	Q	87				57	0.0	50				40	0.0	AF	698
100	175		177	110		111	87	00	89				01	00	09				40	00	40	1001
4					6			8			10		-	12		-	14			16		
		тw	0-0	CIRC	CUI	Τ, Ι	DOU	JBL	E V	VIN	DIN	IGS	, F(OR	DR	UM	AR	MA	TU	RES	j	
-------------------	------------------------	-----------------	------------	-------------------	-----	--------------	-----------	-----	-----------	----------	-----	-------	------	------	----	---------	-----------------	-----	-----	-----------------	------	-------------------
TORS							F	RON	TA	ND	BAG	CK I	PITC	CHE	S							TORS
DNG		4		_	6		_	8			10			12			14			16		DNG
F CON	P	OLE	ES	P	OLE	ES	P	OLE	ES	P	OLE	S		OLE	ES	P	OLE	S	Р	OLE	S	F CON
No. 0	F	RE~ ENTRANCY	B	F	RE-	B	F	RE-	B	F	RE-	В	F	RE-	В	F	RE~ ENTRANCY	В	F	RE- ENTRANCY	В	No. 0
702	175		175	110		110	4			60			50		50	1.40		P 1	ī			702
704	177	1 CO	177	$\frac{117}{117}$	00	119				71	00	71	- 59	1.00	59	49_	00	51				704
708	175	00	177 179	110		0.1.1	87 89	83	89 89										43	00	45	708
$\frac{710}{712}$	177	Ø	177	119	00	$119 \\ 119$							59	Ø	59	51	<u>w</u>	51				710 712
714	1.97		170			101	00		90	71	Q	71									1.5	714
716	179_	00	181	119	00	121	85_	88	. W1	71	00	_/3_	_59_	00	61	51	0	51	45_	Q	45	716
720	179	Ø	179	101	0	101		-														720
724	179	00	181 183	119	00	121 121	89 91	23	91 91	71	00	73	59	00	61	51	00	53	45	0	45	724
726	181	0	181	101	00	102				73	Q	73	61	0	61							726
730	_ 183	00	188	121	Q	120							01	00	01							730
732	181 183	00	183 185	102	0	102	91 -91	88	91 98	79		79				51	00	53	45	00	47	732
736	183 185	Ø	188 185	120	00	123				73	00	75	61	Ø	61							736
738	183	00	185	103	00	195		0.0	93	<u> </u>			61	00	62	53	Ø	53	15	00	17	738
742	185	00	187	123	Q	123	93	20	93				01		00				4.)	00	- ±1	742
744	185	0	185 187	195	0	195				73	00	75				52	0	52				744
748	185 187	00	187 189	123	00	125	93 93	88	93 95	10		10	61	00	63	00	00	00	47_	Ø	47	748
750	187	0	187	125	00	127							63	0	63	53	0.0	55				$\frac{750}{752}$
754	198		461	125	Ø	125				75	Ø	75	00									754
756	189	00	191	127	0	127	95	23	<u> </u>	75	00	77	1						47	CO.	47	756
760	189 191	Ø	189 191	125	00	127							63	0	63	53	00	55				760
764	189	00	.191	127	00	129	95 95	88	96	75	00	77	63	00	65				47	00	49	762
766	191		101	127	Ø	127				77	Ø	77				55	Ø	55				766
770	103	0	193	129	0	129								1								770
772	,191 (193	00	193 195	127	00	129	95 97	8	97 97		6	17.77	63	00	65		0		47	00	49	772
776	193 195	0	193 195	129	00	131				77	00	79	65	Ø.	65	00	<u>w</u>					776
778	193	00	196	129	Q	129	97	(3)	97							EE		27	40	0	10	778
782	195	00	197	131	0	131	97	00	<u> </u>							50	00	97	49	0	49_	782
784	195	Ø	195 197	129	00	131				77	00	79	65	Ø	65							784
788	195 197	00	197 199	131	00	133	97 99	200	99 99	19_		19	65	00	67	55	00	57	49	Ø	49	788
790	197	(0)	197	131	0	131																790
794	199		199	133	0	133				79	0	79				57	0	57				792
796	197 199	00	199 201	131	00	133	99 99	80	99 101	79	00	81	65	00	67				49	00	51	796
800	800 1 (D) 1 133 00 135																					800
		4			6			8			10			12			14			16		





WINDING TABLES FOR TWO-CIRCUIT, TRIPLE WINDINGS FOR DRUM ARMATURES.



T	ABI	_E (OF T	ΓW	0-C	IRC	CUI	т, т	RIF	PLE	WI	ND	INC	GS, I	FOI	R D	RU	MA	RM	ATU	JRE	ES.
TORS							F	RON	TA	ND	BAG	CK 1	PITC	CHE	S							TORS
ONDUC	F	4	FS	F	6 01.1	FS	P	8	2.5	P	10 OL F	S	P	12 OLF	23	F	14	23	-	16	22	ONDUC
.OF C	F	RE-		F	RE+	R	F	RE-	B		RE-	B	Ē	RE-	D		RE-			RE-	B	OF C
z 102	23	ENTRANCY 000	25	15	ENTRANCI	17.	11		13	1.	ENTRANCY		I' X	ENTRANCY	8	T.	ENTRANCY		5	ENTRANCY	7	2 102
104	25	0	21				12		15	11	@	11				7	@	7	7	60	17	104
108	27		29	17 19	Ø	17 19	10		10									5		(220)		100
110	29		20	17	000	19	10	(22)	10	11		10	9	000	2							110
$114 \\ 116 \\ 110$	29	000	31	19	60	21	10	000	10	11	@	15	9	600	11							$114 \\ 116 \\ 110$
$118 \\ 120 \\ 199$	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$												$118 \\ 120 \\ 100$									
122 124 196	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													122								
120 128 130	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$												120 128 130									
132	33		35	21 23	200	21 23	11		17	10		18				9	000	9		0	0	132
$134 \\ 136 \\ 129$	85	(lee)	35	21	60	23	15		10	13	@	$\frac{15}{13}$	11		11	9	(22)		1	(22)	9	134
$130 \\ 140 \\ 140$	35	000	37	23	002	25	17	000	19				11	555	13				9	000	9	138
144 144			37	23 25	0	23 25	17	(00)	17	15	000	15				0	-					$142 \\ 144 \\ 146$
$140 \\ 148 \\ 150$	37	(00)	39	28	000	25	19	(20)	19	13	(22)	15	11	000	18	9	000	11	0		0	$146 \\ 148 \\ 150 $
150	39	000	39	25	6	27	17	000	19	4.15		1.57		چې ا	13				9	000	9	$\frac{150}{152}$
$154 \\ 156 \\ 159'$	39	00	41	26 27	553	25 27	19	000	21	15 15	000	$\frac{17}{15}$							_9	00		$\frac{154}{156}$
$150 \\ 160 \\ 160 \\ 100 $	41	000	41	- 95		07	1.9	(22)	19				19			11	00	11				158 160
$162 \\ 164 \\ 166$	41	000	43	27		29	10	000	21	17	@	17	18_	<u>65</u>	15	11	000	13	0	672		$162 \\ 164 \\ 166$
168	43		48	27 29	000	27 20	19		02		000	11							9	000	11	168
$170 \\ 172 \\ 174$	43		45	27		29	41	QU	40		-	10	12		16			10			11	$\frac{170}{172}$
176	45	000	45	29	000	31	02	000	21	17	@	19 17	15	888	15	11 13	000	13				174 176 170
180	45		47	29 31	@	29 31	40	60	20										11	-	11	178
182 184 186	47	000	47	29	000		02	(20)	25	19	Q	19	15	000	16				11	(22)	11	182 184
188	47	600	49		GD		20	000	20	17	000	19	15	_@)	11	13	0	13	11	000	13	186 188
192 194	49	600	49	31 83	888	81 33	20	60	20	10	62	01		_		19	000	19				190 192
196 198	49	000	01	81	60	83	23	000	25	19	@	19	16	972	37				11	000	13	194 196 198
200	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$												200									
	4 6							8			10			12			14			16		



T	ABL	.E (DF	rw	0-0	IRC	CUI	г, т	RIF	PLE	WI	ND	INC	S, F	-01	R D	RUI	MA	RM	ATU	JRE	ES.
rors							Fl	RON	A TI	ND	BA	CK I	PITO	CHE	S							rors
CONDUCT	P	4 OLI	ES	P	6 OLI	ES	P	8 OLE	ES	P	10 OLE	ES	P	12 POLE	ES	F	14 OLE	ES	F	16 OLI	ES	CONDUCT
No. OF	F	RE-	В	F	RE-	В	F	RE-	B	F	RE-	В	F	RE-	B	F	RE-	В	F	RE-	В	No. OF
202	49 51	Q	49 53	- 33	000		25	Q	27	91	000	91				13	@	15	13	Q	13	202
206	49 \$3	Q	61 53	35		35	25	Q	25	19	@	21						10				204
208	51 53	000	51 55	33 35	553	35 37	27	000	27				17 17	65%	17							208
212 214	51 55	@	53 56				25	œ	27	21	00	23							13	00	13	212
216 218	$\begin{array}{c c c c c c c c c c c c c c c c c c c $															216						
$\begin{array}{c ccccccccccccccccccccccccccccccccccc$															$\frac{220}{222}$							
224	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$																					
228	57		69	87 39	873	87 89	40	000	40	41		20				1.11	0	1.5	10			228
230	59	œ	69				27	(02)	29							15	8	$\frac{17}{17}$	13	(00)	15	230
234 236	57 59	000	67 61	87 39	@	89 41	29	000	_31	23	000	$\frac{25}{23}$	19	63	19 21				15	000	15	234
238	67 61	Q	59 61	89	000	89	29	œ	29							-						238
242	69 61	0	69 63	41	هما	41	31	Q	31													240
$\frac{244}{246}$	59 63	000	63 63	89 41	583	41 43	29	000	31	25 23	000	$\frac{25}{25}$	19 21	553	21	17	<u>@</u>	$\frac{17}{19}$	15	000	15	244 246
$\frac{248}{250}$	6]	0	61				31	00	33										15	00	17	$\frac{248}{250}$
252	6)	60	63	41 43	Q	41 43	91	60	01	05	60	97										252
254	65		65				- 51	000	- 21	25	Q	25										254 256
$\frac{258}{260}$	63 65	000	63 67	43	600	48 46	33	000	33				21 21	8	2) 23	17	000	<u>19</u> 19				$\frac{258}{260}$
$\frac{262}{264}$	63 67	Q	65 67	43	622	43	31	œ	33	97	000	97							15	Q	17	262
266	65 67	0	60 69	40	000	40	33	Ø	35	25	œ	27							17	@	17_	266
208	66 69	000	67 69	43 46	Q	45 47	33	000	33				2] 23	33	28 28							268
$\frac{272}{274}$	67 69	0	67		•		35	00	35	27	00	29		-		<u>19</u> 19	@	19 21				$\frac{272}{274}$
276	61	60	69	46	ê	45	22	60	35	27	000	27							17		17	276
280	71	000	71	45		47	00	QU	00	-					0.0				17	(00)	11	218
282 284	71	000	73	47	888	49	35	000	37	29	Q	29	28	669	23					000	19	282 284
286 288	09 73	œ	71 13	47 49	0	47	35	Q	35	27	@	29				19 21	000	21				286 288
290 292	11 78	@	71 75				37	Q	37													290
294 296	71 75	000	73 75	47 49	200	49 51	35	000	37	29	000	31	23 25	<u></u>	25 25				17	000	19	294
298 300	78 75	Ø	73 77	40	82	49	37	@	39			40				01	000	01	19	@	19	298
	4 6							8			10			12		21	14	21		16		300

TA	BL	E C)F T	W	D-C	IRC	ะบเา	г, т	RIP	LE	WI	NDI	NG	S, F	OF	R DI	RUN	ΛA	RM	ΑΤι	JRE	S.
TORS							F	RON	TA	ND	BAG	CK I	PITO	CHE	S							rors
CONDUC	P	4 OLE	ES	P	6 OLE	ES	P	8 OLE	S	P	10 OLE	ES	F	12 POLE	ES	P	14 POLE	ES	P	16 OLE	S	CONDUC
No. 0F	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	No. OF
302 304	73	0	75 77				37	0	37	31	60	31				21	Ø	23				302 304
306	75 77	000	75 79	49 51	Q	51 53	39	000	39	29	000	31	25 25	999	25 27							306 308
310	75 79	@	77 79	51	000	51	37	Q	39										19	@	19	310
314	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														314							
316	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														$\frac{310}{318}$							
320	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														320							
324	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$															324						
$\frac{328}{330}$	81 83	000	81 85	63 55	000	65 57	41	000	43				27 27	000	27 29	23	000	25 25_	21	000	21	$\frac{328}{330}$
334	81 85	Q	83 85				41	@	41	33	0	35										334
336 338	83 85	@	82 87	57 57	893	50 67	43	Q	43	33	000	33_										336
$\frac{340}{342}$	83 87	000	85 .87	66 67	Q	67 69	41	000	43				27 29	GED GED	29 29	23	000	25	21	000	21	$\frac{340}{342}$
$\frac{344}{346}$	86 87	Q	85 89				43	æ	45	35	(QQ)	35 35				25	@	25	21	æ	23	344 346
348 350	85 89	0	87 89	59	Geo I	86	43	Q	43													348
$\frac{352}{354}$	87 89	000	87 91	57 59	553	50 61	45	000	45	35	000	37	20 29	ଚିଚଚି	29 31							352
356 358	87 91	0	89 91				43	Q	45	35	Q	35				$\begin{array}{c} 25 \\ 25 \end{array}$		$\frac{25}{27}$	21	Q	23	$\frac{356}{358}$
$\frac{360}{362}$	89 91	@	89 93	61	(22)	61	45	Q	47										23	Q	23	360 362
$\frac{364}{366}$	89 93	000	91 93	59 61	000	61 68	45	000	45	37 35	000	37 37	29 31	000	81 81 83							$\frac{364}{366}$
368 370	91 93	Q	91 95				47	Q	47							25	Q	27				$\frac{368}{370}$
372 374	91 95	0	98 95	63	653	01 63	45	@	47	37	00	39				27	000	27	23	Q	23	$\frac{372}{374}$
376 378	98 95	000	98 97	61 63	@	63 65	47	000	49	37	@	37	31 31	83	31 88				23	000	25	376 378
380 382	93 97	Q	95 97				47	0	47													380 382
384 386	95 97	0	95 99	63 65	Geo Geo	68 65	49	0	49	39 37	000	39 39				27	000	27 29				384 386
388 390	95 99	000	97 99	63 65	888	66 67	47	000	49				31 88	873	83 88				23	000	25	388 390
<u>392</u> <u>394</u>	97 99	Q	97 101				49	Q	51	39	@	41							25	Q	25	392 394
396 398	97 101	Q	99 101	65	@	67	49	0	49	39	000	39				27	@	29				396 398
400	400 4 6							8			10	L		12		29	14	29		16		400

ТА	BL	EO	FT	W	D-C	IRC	רוט	Г , Т	RIP	LE	WI	ND	ING	S, F	OF	R DI	RUN	A A	RM	ΑΤι	JRE	S.
rors			1				FI	RON	ТА	ND	BAG	CK I	PITC	HE	S							rors
CONDUCT	P	4 OLE	ES	P	6 OLE	ES	P	8 OLE	cs	P	10 POLE	ES	P	12 OLE	ES	P	14 OLE	cs	P	16 OLE	cs	CONDUCT
No. OF	F	RE-	В	F	RE-	В	F	RE- ENTPARCY	В	F	RE- ENTRARCY	В	F	RE-	В	F	RE-	В	F	RE-	В	No. OF
402	101	000	99 103	65 67	8	67 89	51	000	51	41	60	41	33 33 .	600	83 36							402
406	99 103	Q	101 103	67	(ER)	67	49	Q	51	39	0	41							25	Q	25	406
410	101 103	Q	103	09	000	69	51	0	53							00		- 00	25	Q	27	410
412 414	101	000	103	67 69	œ	69 71	51	000	51	41	000	43	38 35	83	35 36	29	000	29 31				412
<u>416</u> 418	$ \begin{array}{c ccccccccccccccccccccccccccccccccccc$															416						
420 422	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$															420						
424 426	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$																					
428 430	$ \begin{array}{c ccccccccccccccccccccccccccccccccccc$																					
432	107		101	71 78	Q	71 78	55		55	12	(0)	45										432
436	109		111	71		79	50		00	43	Q	43	30		0.77						0.7	436
438 440	iĭi	000	111	78	G	75	53	000	55				30 37	Geo	37	31	00	31	27	000		438
442 444	109	QQ	109	78	553	73 75	55	Q	57	45	000	45				31	@	33	27	œ	29	442
446 448	109 115	@	111 113				55	@	55	43	Q	45										446
450 452	111 113	000	111 115	78 75	@	75 77	57	000	57				37 87	8	37 89							450
454	111 115	Q	118 115	75	000	75	55	Q	57	45	@	47				31	Q	33	27	Q	29	454
458	118 115	Q	113 117	71	_@D		57	Q	59	40		40				00	000	00	29	œ.	29	458
460 462	113 117	000	115	75 77	888	.77 .79	57	000	57				37	8 80	39 39			-				$\frac{460}{462}$
464 466	115 117	Q	115 119				59	Q	59	47	@	47										464
468 470	115	Q	115	79	@	77	57	0	59							33	000	33 35	29	Q	29	468
472 474	117	000	117	77	000	79	59	000	61	47	000	49	39	000	39 41				29	000	31	$\frac{472}{474}$
476 478	117	00	110				59	00	59	47	0	47										476
480 482	129	00	119	79 81	583	79 81	61	60	61							32	60	35				480
484	119	000	120	79	60	81.	50	000	61	49	@	49	89	GER		35	@	35	00	000	21	484
488	128	000	123	81		83	00	000	01	41	000	49	Ai	Gab	41				29	000	01	488
490	123	00	155	81 83	ê	81 83	01	(22)	63										31	QQ	31	490 492
494 496	125	@	125				61	QD	61	<u>49</u> <u>49</u>	00	51 49				35	@	35				494 496
498 500	122	000	123	81 83	888	,83 .85	63	000	63				1	883	41 43	35	000	37				498 500
		4			6			8			10			12			14			16		

TA	BL	E C	DF T	w	D-C	IRC		г, т	RIF	LE	WI	ND	NG	S, F	OF	R DI	RUN	AN	RM	ΑΤι	JRE	ES.
TORS							F	RON	IT A	ND	BA	CK	PITO	CHE	S							TORS
LONGNOD	P	4 POLI	ES	P	6 OLI	ES	F	8 POLE	ES	F	10 OLE	ES	P	12 OLE	S	F	14 POLI	ES	F	16 OLI	ES	CONDING
No. OF	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	NE-	В	F	RE-	В	No. OF
502 504	128 127	Ø	125 127	88 85	@	83 85	61	œ	63	51	000	51							31	@	31	502 504
506 508	125 127	œ	125 129				63	œ	65	49	Q	51			4				31	Q	33	506 508
$\frac{510}{512}$	125 129	000	127 129	88 X5	<u></u>	85 87	63	000	63				41 43	<u></u>	43 43	35 37	000 @	37 37				510 512
$\frac{514}{516}$	127 129	@	137	85 87	888	86 87	65	œ	65	51 51	000	53 51										514 516
$518 \\ 520 \\ 520$	127 131	@	129 131			97	63		65				423		43				31	œ	33	518 520
$\frac{522}{524}$	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$															524 526						
528 530	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														528 530							
$\frac{532}{534}$	131	000	138	87 89	668	89 91	65	000	67	53	000	55	43	588	45 45				33	000	33	532 534
536 538	133 135	@	133				67	œ	69	53	Ø	53				37	@	39	33	@	35	536 538
$\frac{540}{542}$	133 137	œ	135» 137	89 91	œ	89 91	67	@	67							39	000	39				540 542
$\frac{544}{546}$	135 137	000	135 139	89 91	000	91 93	69	000	69	55 53	000	55 55	45	600	45 47							544 546
548 550	135 139	@	137 139			91	67	Q	69							20		20	33	@	35	548
554 556	137 139	0	137 141	93	000	03	69	@	71	55	@	57				39	@	39 41	35	@	35	554
558 560	137 141	000	139 141	91 93	Q	93 95	69	000	69			00	45 47		47 47							558
$562 \\ 564$	139 141	00	189 143	93	000	93 95	71	QQ	71	57	000	57										$562 \\ 564$
566 568	139 143	Q	141 143				69	œ	71	55	œ	57			_	39 41	@ @	41 41	35	Ø	35	566 568
$\frac{570}{572}$	141 143	000	141 145	93 96	583	96 97	71	000	73				47	6 7 76	47 49				35	000	37_	570 572
574 576	141	Q	143	95 97	œ	96 97	71	@	71	57 57	000	59 57										574 576
578 580	145	@	147	96	000	97	73	(00)	73				47	000	49	41	Q	41	05		07	578
584 586	147	000	147	97	۵۵ ۵	99	71	000	75	59	@	59	49	ŝ	49	41	000	43	35	000	37	582 584
588 590	147		149	97 99	5573	97 99	73		73	01		00							01		01	588 590
592 594	149 147 149	000	149	97 99	Q	99 101	75	000	75	59	000	61	49	383	49	41	000	43				592 594
596 598	147	Q	149				73	@	75	59	@	59				43	œ	43	37	(00)	37	596 598
600	4 6							8			10			12			14			16		600

ТА	BL	EO	FΤ	wc)-CI	RC	UIT	, TF	RIP	LE	WIN	IDI	NG	S, F	OR	DF	RUM	1 A I	RM	ATU	RE	s.
rors							F	RON	TI A	NE	BA	CK	PIT	CHE	ES							rors
CONDUCT	P	4 OLI	ES	F	6 POL	ES	P	8 OLE	ES	F	10 POLE	ES	P	12 OLI	ES	F	14 OLI	ES	P	16 OLE	ES	CONDUCT
No. OF	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	F	RE-	В	No. OF
602 604	149 151	Q	149 153				75	Q	77	61	60	61							37	@	39	602
606	149 153	000	151 158	101	888	101 103	75	000	75	59	000	61	49 51	888	51 51	40		10				606
610	151 158	Q	151 155	101		102	77	œ	77							43	@	43				610
612 614	151 155	00	163 156	101	@	103	75	00	77	61	Q	63							37	Q	39	$\begin{array}{ c c c c c c c c c c c c c c c c c c c$
616 618	153	000	168	101	000	103	77	000	79	61	Q	61	51 51	000	61 57				39	000	39	616 618
620 622	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$															$\begin{array}{c} 620 \\ 622 \end{array}$						
624 626	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$															624						
628 630	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														628							
632	159	000	169	105	000	107		000	19			0.5	59	6	68				39	000		632
634 636	169	(00)	161	109	000	105	79	(00)	81	<u>63</u> 63	000	65 63				45	000	45	39	(00)	41	634 636
638 640	157	00	169 161				79	œ	79							45	@	47				638 640
<u>642</u> 644	159	000	159 163	106 107	553	107 109	81	000	81	65	60	65	58 53	883	53 55				•			642
646 648	159 163	Q	161 163	107	00	107	79	æ	81	63	00	65							39	Q	_41_	646
650 659	161 168	Q	161 165	109	000	109	81	0	83							45	@	47	41	0	41	650
654	161 165	000	163 165	107	8	109	81	000	81	65	000	67	63 55	000	55 55	47	(22)	41				654
658	163 165	@	168 167				83	Q	83	65	(22)	65										656
<u>660</u> 662	163 167	Q	165 167	109	883	109	81	Q	83										41	0	41	660 662
664 666	165	000	165	109	0	111	83	000	85	67 65	@ 000	67 67	86 75	83	55 57	47	000	47 49	41	000	43	664
668 670	165	60	167				83	00	83													668 670
672	167	60	167	111 113	6	111	85	60	95	67	60	60										672
676	107	000	171	111		118.	00	000	00	67	Ŵ	67			87	1.07		10	41		40	676
680	171	000	171	113	800	115	83	000	80				67	653	67	47	000	49 49	41	000	43	680 680
682 684	171	QQ	173	113	Q	113 115	85	QD	87	69	000	69							43	@	43	$\begin{array}{c} 682 \\ 684 \end{array}$
686 688	169 173	Q	171				85	Q	85	67	Q	69		-								686 688
690 692	171 173	000	171 175	113 115	000	115 117	87	000	87				67 67	000 (a)	67 69	49	00	49				690 692
694 696	171	Q	175	115	533	115	85	Q	87	<u>69</u> 69	000	71				49	@	51	43	œ	43_	694 696
698 700	178	œ	173	117	000	117	87	@	89	00		05							43	œ.	45	698 700
		4			6			8			10			12			14			16		

Т	AB	LE	OF '	тw	0-0	DIR	CUI	т, т	RI	PLE	E WI	ND	INC	GS,	FO	RE	RU	MA	RN	IAT	UR	ES.
TCRS							FI	RON	ΤА	ND	BAC	CK I	PITC	CHES	S							TORS
NDUC		4			6	10	-	8		-	10			12			14		D	16	~	NDUC
F CO1		OLE	<u>S</u>	P	OLE	S	<u>P</u>	OLE	S	1	OLE	S		OLE	S	P	OLE	S	P	OLE	S	F CO!
No. 0	F	RE-	В	F	RE-	B	F	RE-	В	F	RE-	В	F	RE- ENTRANCY	Β	F	RE- ENTRANCY	В	F	RE- ENTRANCY	В	No. 0
702	173 177	000	176	115 117	@	117 119	87	000	87	71	60	71	67' 59	83	69 69							702
706	175 177	Q	175	117	000	117	89	0	89	69	@	71				49	@	51				706
708	175 179	0	177	119	6	119	87	Q	89							51	000	01	43	œ	45	710
$\frac{712}{714}$	177	000	177	117	888	119 121	89	000	91	71	000	73	<u>59</u>	5573	69 61				45	000	45	712
716	177	60	179				89	60	89	71	Q	71										716
720	181	60	179	119 121	Q	119 121	01	60	01							51	000	51				720
724	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$										1.5		15	724								
726	188	000	183	121	GD.	123	89	000	91	11	000	73	61	600	61				45	000	45	726
730 732	153	@	181 185	121 123	ક્સ્સ	121 123	91	Q	93										45	Q	47	730
734	181 185	Q	183 .185				91	œ	91	73	@	75 73				51	00	53 53	_			734
738	183 185	000	183 187	121 123	Q	$\frac{123}{125}$	93	000	93	10			61 61	88	61 63	00	000	00				738
740	183	Q	185 187	109		202	91	Q	93								-		45	0	47	740
744 746	185 187	Q	185 189	125	6	125	93	0	95	75 73	000	75						-	47	Q	47	744
748	185	000	187 189	123 125	888	125 127	93	000	93				61 63	888	63 63	<u>53</u> 53	000	53 55		-		748
752 754	187	0	187				95	6	95	75	60	77										752
756	185		189	125 127	œ	125 127	0.0		05	75	000	75							45		47	756
760	191		191	105		107	90	(00)	90										47	(00)	47	758
762	191	000	193	120	G	129	_95	000	97	77	Q	77	03	000	63 65'	53 55	000	$\frac{55}{55}$	47	000	49	762 764
766	189 193	@	191 193	127	888	127 129	95	@	95	75	@	77							-			766
770	191 193	Q	191			-	97	œ	97													770
774	191 195	000	193 195	127 (129	Q	129	95	000	97	77	000	79	63 65	88	65 65	FE	(7)		47	000	49	774
778	193 195	Q	193 ,197	190		100	97	Q	99	11						55	90	55	49	0	49	778
780	193 197	Q	(195 (197	131	Č.	131	97	œ	97					-								780 782
784 786	195	000	-195 -199	129 131	878	131 133	99	000	99	79	000	79 79	65 65	5573	65							784
788 790	195	0	197				97	0	99							55	00	57	49	0	49	788
792 794	197	0	197	131 133	Q	131 133	99	(0)	101	79	0	81				57	000	57	10	(00)	51	792
796	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													01	796							
198 31 000 31 13 99 000 99 55 000 67 800												798 800										
		4			6			8			10	12		12	1.6		14		-	16		



the



WINDING TABLES FOR MULTIPLE-CIRCUIT, SINGLE WINDINGS FOR DRUM ARMATURES.



Г	MULT	TIPL	E-CIF	RCUI	T, SI	NGL	E WII	NDIN	GS,	FOR	DRU	JM A	RMA	TUR	ES.
ORS			14		FRO	NT A	ND B	ACK	PITCH	HES		De Ca			SRO.
4 DUCT		4	(3		3	1	0	1	2	1	.4	1	6	TOUCI
F CON	PO	LES	POI	LES	PO	LES	POI	LES	PO.	LES	PO.	LES	PO	LES	F COI
No, 0	F	B	F	B	F	B	F	B	F	B	F	B	F	B	No. O
$\frac{202}{204}$	$\begin{array}{r} 49 \\ 49 \\ \end{array}$	$\begin{array}{c c} 51 \\ 51 \end{array}$	<u>33</u> 33	<u>35</u> 35	$\begin{array}{c c} 25 \\ \hline 25 \end{array}$	$\frac{27}{27}$	<u>19</u> <u>19</u>	$\begin{array}{c} 21 \\ 21 \end{array}$	$\begin{array}{r} 15 \\ 15 \end{array}$	17 17	$\frac{13}{13}$	$\frac{15}{15}$	11	13 13	$\begin{array}{r} 202 \\ 204 \end{array}$
$\frac{206}{208}$	51 51	53 53	<u>33</u> 33	$\frac{35}{35}$	$\frac{25}{25}$	$\frac{27}{27}$	19 19	$\begin{array}{r} 21 \\ 21 \end{array}$	<u>17</u> <u>17</u>	$\frac{19}{19}$	$\frac{13}{13}$	$\frac{15}{15}$	<u>11</u> <u>11</u>	<u>13</u> 13	$\begin{array}{r} 206 \\ 208 \end{array}$
$\frac{210}{212}$	$ \begin{array}{c ccccccccccccccccccccccccccccccccccc$														$\frac{210}{212}$
$\frac{214}{216}$	53 53	55 55	35 35	<u>37</u> <u>37</u>	$\frac{25}{25}$	27 27	$\begin{array}{r} 21 \\ 21 \\ \end{array}$	23	17 17	<u>19</u> <u>19</u>	15 15	17	13 13	15 15	$\begin{array}{r} 214 \\ 216 \end{array}$
$\begin{array}{r} 218 \\ \hline 220 \\ \hline \end{array}$	53 53	55 55	35	3737	$\frac{27}{27}$	29 29	$\begin{array}{r} 21 \\ 21 \\ \end{array}$	$\begin{array}{c} 23 \\ 23 \\ \end{array}$	17 17	19 19	$\frac{15}{15}$	17	$13 \\ 13 \\ 13 \\ 10 \\ 10 \\ 10 \\ 10 \\ 10 \\ $	$\frac{15}{15}$	$\begin{array}{r} 218 \\ 220 \\ \end{array}$
222 224	$ \begin{array}{ c c c c c c c c c c c c c c c c c c c$														
$\frac{226}{228}$	55	57	37	<u>39</u> <u>39</u>	27	29 29	$\frac{21}{21}$	23	17	$\frac{19}{19}$	15 15	17	13 13	15	228
232	57	59	37	39	27	$\frac{29}{29}$	$\begin{array}{r} 21 \\ 23 \\ 03 \end{array}$	25	<u>19</u> <u>19</u>	21	15	17	13	15	232
236	57	<u>59</u> 61	39	41	<u>29</u> 29	31	23	$\frac{25}{25}$	19 19 19	$\frac{21}{21}$	$15 \\ 15 \\ 15$	17	13	15	236
$\frac{240}{242}$	<u>59</u> 59	61 61	<u>39</u> 39	<u>41</u> 41	29 29	31 31	23 •	$\frac{25}{25}$	<u>19</u> 19	$\frac{21}{21}$	17	19 19	13 15	$15 \\ 17$	$\frac{240}{242}$
$\frac{244}{246}$	59 61	$\begin{array}{r} 61 \\ 63 \end{array}$	<u>39</u> 39	$\frac{41}{41}$	29 29 29	$\frac{31}{31}$	23 23	$\frac{25}{25}$	19 19 19	21 21	17 17	$\frac{19}{19}$	$\begin{array}{r} 15 \\ 15 \\ 15 \end{array}$	$\frac{17}{17}$	$\begin{array}{r} 244 \\ 246 \end{array}$
$\frac{248}{250}$	$\begin{array}{r} 61 \\ 61 \end{array}$	63 63	41 41	$\frac{43}{43}$	$\frac{29}{31}$	$\frac{31}{33}$	$\frac{23}{23}$	$\frac{25}{25}$	<u>19</u> 19	$\frac{21}{21}$	17 17	$\frac{19}{19}$	$\frac{15}{15}$	$\frac{17}{17}$	$\begin{array}{r} 248 \\ 250 \end{array}$
$\frac{252}{254}$	61 63	63 65	41 41	43 43	31 31	33 33	$\frac{25}{25}$	$\frac{27}{27}$	19 21	$\frac{21}{23}$	17 17	<u>19</u> <u>19</u>	15 15	<u>17</u> <u>17</u>	$\frac{252}{254}$
$\frac{256}{258}$	63 63	65 65	41 41	$\frac{43}{43}$	31	33	$\frac{25}{25}$	$\frac{27}{27}$	$\begin{array}{c} 21 \\ 21 \\ \end{array}$	$\frac{23}{23}$	<u>17</u> <u>17</u>	$\frac{19}{19}$	15 15	17 17	$\frac{256}{258}$
$\frac{260}{262}$	63 65	65	43	45 45	31 31	33	25 25	27	$\frac{21}{21}$	23	$17 \\ 17 \\ 17 \\ 15$	19 19 10	$15 \\ 15 \\ 15$	17 17	260 262
264 266 268	65 65	67	43 43	45	$\frac{31}{33}$	<u> </u>	$\frac{25}{25}$	$\frac{27}{27}$	$\frac{21}{21}$	$\frac{25}{23}$	17 17 19	$19 \\ 19 \\ 91$	$\frac{15}{15}$	17	$\frac{264}{266}$
$\frac{270}{272}$	67	69 69	43	45	33	35	25 27	27	21	23	<u>19</u> 19	21 21 21	15	17	$\frac{270}{272}$
$\frac{274}{276}$	67 67	69 69	$\frac{45}{45}$	$\frac{47}{47}$	33 33	35 35	27	29 29	21 21	$\frac{23}{23}$	$\begin{array}{c} 19\\ 19\\ 19 \end{array}$	21 21	17	<u>19</u> 19	$\frac{274}{276}$
278 280	69 69	$\frac{71}{71}$	$\frac{45}{45}$	$\frac{47}{47}$	33 33	$\frac{35}{35}$	$\frac{27}{27}$	29 29	23 23	$\frac{25}{25}$	19 19	21 21	17 17	<u>19</u> 19	$\frac{278}{280}$
$\frac{282}{284}$	69 69	71 71	45 47	$\frac{47}{49}$	35 35	37 37	27 27	29 29	$\begin{array}{r} 23 \\ 23 \end{array}$	$\frac{25}{25}$	19 19	21 21	17 17	$\frac{19}{19}$	$\frac{282}{284}$
286 288	71 71 71	73	47	<u>49</u> <u>49</u>	35 35	37 37	27	29 29	23 23	25 25	<u>19</u> 19	21 21	<u>17</u> <u>17</u>	<u>19</u> <u>19</u>	286 288
290 292	71 71 71 72	73 73	47	<u>49</u> <u>49</u>	35 35	37 37	27 29	29 31	23	25 25	19 19	21 21	17	<u>19</u> <u>19</u>	290 292
294 296	73 73	75	47 49 40	<u>49</u> <u>51</u>	35 35 27	<u>37</u> <u>37</u> 20	29 29	<u>31</u> <u>31</u>	23	25 25	$\frac{19}{21}$	21 23	17	<u>19</u> <u>19</u>	294 296
300	73	75	49	51	37	39	29	$\frac{31}{31}$	23	25 25	21	23	17	$\frac{19}{19}$	300

N	IULT	IPLE	-CIR	CUIT	r, sir	NGLE	E WIN	IDIN	GS, F	OR	DRUI	M AR	MAT	URE	S.	
rors					FRC	NT A	ND E	BACK	PITC	HES.					TORS	
CONDUCI	PO	4 LES	Po	6 LES	Po	8 LES	1 PO	0 LES	1 PO	2 LES	1 PO	4 LES	1 PO	6 LES	CONDUC	
10. OF	F	В	F	В	F	В	F	В	F	В	F	В	F	В	4o. OF	
302	75	77	49	51	37	39	29	31	25	27	21	23	17	19	302	
$\frac{304}{306}$	75	77	49 49	51	37	39	$\begin{array}{c c} 29 \\ 29 \end{array}$	$\frac{31}{31}$	$\frac{25}{25}$	27	$\frac{21}{21}$	$\frac{23}{23}$	17 19	$\frac{19}{21}$	$\frac{304}{306}$	
308	75	77	51	53	37	39	29	31	25	27	21	23	19	21	308	
310	77	79	$\frac{51}{51}$	53	37	39	31	33	$\frac{25}{25}$	27	$\frac{21}{21}$	$\frac{25}{23}$	19	$\frac{21}{21}$	310	
314	77	79	51	53	39	41	31	33	25	27	21	23	19	21	314	
318	79	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														
320 322	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$															
324	79	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														
$\frac{326}{328}$	81	83	53	55	39	41	$\frac{31}{31}$	33	$\frac{27}{27}$	29	$\frac{23}{23}$	$\frac{25}{25}$	<u>19</u> 19	$\frac{21}{21}$	<u>326</u> 328	
330	81	83	53	55	41	43	31	33	27	29	23	25	19	21	330	
334	81	85	55	57	$\frac{41}{41}$	$\frac{43}{43}$	33	35 35	27	29	$\frac{23}{23}$	$\frac{25}{25}$	19	$\frac{21}{21}$	334	
336	83	85	55	57	41	43	33	35	27	29	23	25	19	21	336	
340	83	85	$\frac{55}{55}$	57	41	43	33	35	$\frac{27}{27}$	29	$\frac{23}{23}$	$\frac{25}{25}$	$\frac{21}{21}$	$\frac{23}{23}$	338	
342	85	87	55	57	41	43	33	35	27	29	23	25	21	23	342	
346	85	87	57	59	43	45	33	35	27	29	$\frac{23}{23}$	$\frac{25}{25}$	$\frac{21}{21}$	$\frac{23}{23}$	346	
348	85	87	57	59 59	43	45	33	35	27	29	23	25	21	23	348	
352	87	89	57	59	43	45	35	37	29	31	25	25	21	23	352	
354	87	89 80	57	59 61	43	45	35	87	29	31	25	27	21	23	354	
358	89	91	59	61	43	45	35	37	29	$\frac{31}{31}$	25	27	$\frac{21}{21}$	$\frac{23}{23}$	358	
360	89	<u>91</u> 91	<u>59</u>	61	43	45	35	37	29	31	25	27	21	23	360	
364	89	91	59	61	45	47	35	37	29	31	25	27	21	23	364	
366	<u>91</u> 91	<u>93</u> 93	<u>59</u> 61	<u>61</u> 63	45	47	35	37	29	31	25	27	21	23	366	
370	91	93	61	63	45	47	35	37	29	31	25	27	23	25	370	
$\frac{372}{374}$	<u>91</u> 93	<u>93</u> 95	61	<u>63</u>	$\frac{45}{45}$	47	37	39	29	31	$\frac{25}{25}$	27	23	$\frac{25}{25}$	372	
376	93	95	61	63	45	47	37	39	31	33	25	27	23	25	376	
$\frac{378}{380}$	93	<u>95</u> 95	61	63 65	47	49	37	39	31	33	25	27	23	25	378	
382	95	97	63	65	47	49	37	39	31	33	27	29	23	25	382	
$\frac{384}{386}$	95 95	97 97	63	$\frac{65}{65}$	47	49	37	39	31	33	27	29	23	25	384	
388	95	97	63	65	47	49	37	39	31	33	27	29	23	25	388	
390	97	99	63	65	47	49	37	<u>39</u> 41	$\frac{31}{31}$	33	27	29	$\frac{23}{23}$	<u>25</u> 25	390	
394	97	99	65	67	49	51	39	41	31	33	27	29	23	25	394	
398	97	101	65	67	49	51	39	41	31	33	27	<u>29</u> 29	23	$\frac{25}{25}$	396 398	
400	99	101	65	67	49	51	39	41	33	35	27	29	23	25	400	

IV	MULTIPLE-CIRCUIT, SINGLE WINDINGS, FOR DRUM ARMATURES. FRONT AND BACK PITCHES #														5.
ORS		663	-		FRC	NT A	ND E	ACK	PITCI	HES					rors
CONDUCT	POI	4 LES	POI	B LES	8 Poi	3 LES	1 POI	0 LES	1 Poi	2 LES	1 Poi	4 LES	1 POI	6 LES	- CONDUC
No. DF	F	В	F	В	F	B	F	В	F	В	F	В	F	В	No. 01
402	<u>99</u> 99	101	65 67	$\frac{67}{69}$	<u>49</u> 49	51 51	<u>39</u> <u>39</u>	$\frac{41}{41}$	33 33	35 35	27	29 29	$\frac{25}{25}$	$\frac{27}{27}$	402
406	101	103	67	<u>69</u> 69	49	51	39	41	33	35	27	29 31	$\frac{25}{25}$	$\frac{27}{27}$	406
400	101	103	67	69	51	53	39	41	33	35	29	31	25	27	410
412 414	$\begin{array}{c c c c c c c c c c c c c c c c c c c $														
416	$ \begin{array}{c ccccccccccccccccccccccccccccccccccc$														
420	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														
422	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														
$\frac{426}{428}$	$\frac{105}{105}$	$\begin{array}{r}107\\107\end{array}$	<u>69</u> 71	$\frac{71}{73}$	53 53	55 55	41 41	$\frac{43}{43}$	$\frac{35}{35}$	$\frac{37}{37}$	<u>29</u> 29	$\frac{31}{31}$	$\frac{25}{25}$	$\frac{27}{27}$	$\frac{426}{428}$
430	107	109	71	73	53	55	41	43	35	37	29	31	25	27	430
434_	107	109	71	73	53	55	43	45	35	37	29	31	27	29	434
436 438	107	109	71 71	73	53	<u> </u>	$\frac{43}{43}$	$\frac{45}{45}$	35 35	37 37	$\frac{31}{31}$	33	$\frac{27}{27}$	$\frac{29}{29}$	436
440	109	111	73	75	53 55	55	43	45 45	35	37	31	33	27	29 29	440
444	109	111	73	75	55	57	43	45	35	37	31	33	27	$\frac{29}{29}$	444
<u>446</u> 448	111	$113 \\ 113$	73	75	55 55	57	$\frac{43}{43}$	$\frac{45}{45}$	37	39	$\frac{31}{31}$	33	27	29	440
$\frac{450}{452}$	111	113	73	75	55 55	57	43	45	37	<u>39</u> 39	31	<u>33</u> 33	$\frac{27}{27}$	29 29	$\frac{450}{452}$
454	113	115	75	77	55	57	45	47	37	39	31	33	27	29	454
458	113	115	75	77	57	59	45	47	37	39	31	33	27	29	458
$\frac{460}{462}$	113 115	$115 \\ 117$	75	77	57	59 59	$\frac{45}{45}$	47	37	· 39 39	$\frac{31}{31}$	<u>33</u> 33	$\frac{27}{27}$	$\frac{29}{29}$	$\begin{array}{r} 460 \\ 462 \end{array}$
464	115	117	77	79	57	59	45	47	37	39	33	35	27	29	464
468	115	117	77	79	57	59	45	47	37	39	33	35	29	$\frac{31}{31}$	468
$\frac{470}{472}$	$\begin{array}{c} 117 \\ 117 \end{array}$	<u>119</u> 119	77	79 79	<u>57</u> 57	<u> </u>	$\frac{45}{47}$	$\frac{47}{49}$	<u>39</u> 39	41	33	$\frac{35}{35}$	$\frac{29}{29}$	$\frac{31}{31}$	$\frac{470}{472}$
474	117	119	77	79 81	59	61	47	49	39	41	33	35	29	31	474
478	119	121	79	81	59	61	47	49	39	41	33	35	29	31	478
$\frac{480}{482}$	119	121	79	81 81	<u>59</u> 59	61 61	47	<u>49</u> 49	39	$\begin{array}{c} 41 \\ 41 \end{array}$	33	$\frac{35}{35}$	29	$\frac{31}{31}$	$\frac{480}{482}$
484	119	121	79	81	59 59	61	47	49	39	41	33	35 35	29	31	484
488	121	123	81	83	59	61	47	49	39	41	33	35	29	31	488
490	121	$123 \\ 123$	81	83	61	63	47	49 51	39	41 41	33	35 37	29 29	31	490 492
<u>494</u> 496	$\begin{array}{r} 123 \\ 123 \end{array}$	$\begin{array}{c c} 125 \\ 125 \end{array}$	81	83	$\begin{array}{r} 61 \\ 61 \end{array}$	63 63	49	51	41	43	35	37	$\frac{29}{29}$	31 31	494
498 500	123 123	125 125	81	83 85	61 61	63 63	49	51	41 41	43	35	37	31	33	498

I	MULT	ripli	E-CIF	RCUI	T, SI	NGL	EWI	NDIN	IGS,	FOR	DRU	MAF	RMAT	URE	s.
TORS					FRO	ONT A	AND I	BACK	PITC	HES					TORS
DUC	4	4		6		8	1	0	1	2	1	4	1	6	IDUC
F CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	F CON
No. OI	F	В	F	B	F	В	F	В	F	В	F	B	F	B	No. 0
502	125	127	83	85	<u>61</u> 61	63 63	49	51 51	41	43	35	37	31	33	502
506	125	127	83	85	63	65	49	51	41	43	35	37	31	33	506
508	$\frac{125}{127}$	$127 \\ 129$	83	85	<u>63</u>	65	$\frac{49}{49}$	<u>51</u> 51	41	43	35	37	$\frac{31}{31}$	33	$508 \\ 510$
512	127	129	85	87	63	65	51	53	41	43	35	37	31	33	512
514	$\begin{array}{ c c c c c c c c c c c c c c c c c c c$														
518	129 131 85 87 63 65 51 53 43 45 35 37 31 33 129 131 85 87 63 65 51 53 43 45 35 37 31 33 129 131 85 87 63 65 51 53 43 45 37 39 31 33 129 131 85 87 65 67 51 53 43 45 37 39 31 33 129 131 85 87 65 67 51 53 43 45 37 39 31 33														
520	129 131 85 87 63 65 51 53 43 45 35 37 31 33 129 131 85 87 63 65 51 53 43 45 35 37 31 33 129 131 85 87 63 65 51 53 43 45 37 39 31 33 129 131 85 87 65 67 51 53 43 45 37 39 31 33 129 131 87 89 65 67 51 53 43 45 37 39 31 33 129 131 87 89 65 67 51 53 43 45 37 39 31 33														
522	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														
526	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														
528	131	133	87	89	65 65	67	51	53	43	45	$\frac{37}{37}$	$\frac{39}{39}$	31	33	528
532	131	133	87	89	65	67	53	55	43	45	37	39	33	35	532
534	133	135	87	89	65	67	53	55	43	45	37	39	33	35	534
538	133	135	89	<u>91</u> 91	67	69	53	$\frac{55}{55}$	$\frac{43}{43}$	$\frac{43}{45}$	37	$\frac{39}{39}$	33	$\frac{30}{35}$	538
540	133	135	89	91	67	69	53	55	43	45	37	39	33	35	_540
542	$\frac{135}{135}$	$\frac{137}{137}$	89	91	67	<u>69</u> <u>69</u>	53	55	45	47	37	39	33	35	542
546	135	137	89	91	67	69	53	55	45	47	37	39	33	35	546
548	135	137	91	93	67	69	53	55	45	47	39	41	33	35	548
552	137	139	91	93	67	69	55	57	45	47	39	41	33	35	552
554	137	139	91	93	69	71	55	57	45	47	39	41	33	35	554
<u> </u>	$\frac{137}{139}$	139	91	93	69	71	55	57	45	47	39	41	33	35	<u> </u>
560	139	141	93	95	69	71	_55	57	45	47	39	41	33	35	560
562	139	141	93	95	69	71	55	57	45	47	39	41	35	37	562
566	141	143	93	95	69	71	55	57	40	49	39	41	35	37	566
568	141	143	93	95	69	71	55	57	47	49	39	41	35	37	568
572	141	$143 \\ 143$	95 95	95	71	$\frac{73}{73}$	<u> </u>	59	47	49	39	41	$\frac{35}{35}$	37	$570 \\ 572$
574	143	145	95	97	71	73	57	59	47	49	39	41	35	37	574
576	$143 \\ 143$	$145 \\ 145$	<u>95</u> 95	97	$\frac{71}{71}$	73	57	<u>59</u>	47	49	41	$\frac{43}{43}$	35	$\frac{37}{37}$	576
580	143	145	95	97	71	73	57	59	47	49	41	43	35	37	580
582	145	147	95	97	71	73	57	59	47	49	41	43	35	37	582
586	145	147	97	99	73	75	57	59	47	49	41	43	35	37	586
588	145	147	97	99	73	75	57	59	47	49	41	43	35	37	588
590	147	149	97	99	73	75	57	59 61	49	51	41	43	35	37	590
594	147	149	97	99	73	75	59	61	49	51	41	43	37	39	594
596	147	149	99	101	73	75	59	61	49	51	41	43	37	39	596
600	149	151	99	101	73	75	59	61	49	51	41 41	43	37	39	600
				1.	11-1-1-1-1-1-1-1-1-1-1-1-1-1-1-1-1-1-1	10									

IN	NULT	TIPLE	E-CIF	RCUI	T, SII	NGLE	a wi	NDIN	GS, I	FOR	DRU	MAR	MAT	URE	s.
rors	ΰ.Ξ',				FRO	NT A	ND E	BACK	PITCI	HES					rors
DUC	4	4	(3	8	3	1	0	1	2	1	4	1	6	DUCI
CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO.	LES	CON
40. OF	F	В	F	В	F	В	F	В	F	В	F	В	F	В	40. OF
602	149	151	99	101	75	77	59	61	49	51	41	43	37	39	602
604	$149 \\ 151$	151	99	101	75	77	59	61	49	51	43	45	37	39	604
608	151	153	101	103	75	77	59	61	49	51	43	45	37	39	608
$\frac{610}{619}$	151	153	101	103	75	77	<u>59</u> 61	61	49	51	43	45	37	39	<u>610</u> 612
614	153	155	101	103	75	77	61	63	51	53	43	45	37	39	614
616	153	155	101	103	75	77	61	63	51	53	43	45	37	39	616
618	153	155	101	103	77	79	61	63	51	53	43	45	37	39	618
620	155	$155 \\ 157$	103	$-\frac{105}{105}$	77	79	61	63	51	53	43	45	37	$\frac{39}{39}$	620
624	155	157	103	105	77	79	61	63	51	53	43	45	37	39	624
626	155	157	103	105	77	79	61	63	51	53	43	45	39	41	626
630	$150 \\ 157$	157	103 103	105	77	79	61	63	$\frac{51}{51}$	53	43	45	39	41	628
632	157	159	105	107	77	79	63	65	51	53	45	47	39	41	632
634	157	159	105	107	79	81	63	65	51	53	45	47	.39	41	634
636	157	159	105	107	79	81	63	65	51	53	45	47	39	41	636
640	159	161	$105 \\ 105$	107	79	81	63	65	<u>03</u> 53	55	40	47	39	41	638
642	159	161	105	107	79	81	63	65	53	55	45	47	39	41	642
644	159	161	107	109	79	81	63	65	53	55	45	47	39	41	644
$\frac{646}{648}$	161	163	107	109	79	81	63	65	53	55	45	47	39	41	646
650	161	163	107	109	81	83	63	65	53	55	45	47	39	$\frac{41}{41}$	650
652	161	163	107	109	81	83	65	67	53	55	45	47	39	41	652
654	163	165	107	109	81	83	65	67	53	55	45	47	39	41	654
$\frac{000}{658}$	163	$165 \\ 165$	109	111	81	83	65	67	$\frac{-03}{53}$	55	45	47	<u> </u>	41 43	656
660	163	165	109	I11	81	83	65	67	53	55	47	49	41	43	660
662	165	167	109	111	81	83	65	67	55	57	47	49	41	43	662
664	165	167	109		81	83	65	67	55	57	47	49	41	43	664
668	165	167	111	113	83	85	65	67	55	57	47	49	41	43	668
670	167	169	111	113	83	85	65	67	55	57	47	49	41	43	670
672	167	169	111	113	83	85	67	69	55	57	47	49	41	43	672
676	167	169 169	111	113	83	85	67	69	<u> </u>	57	47	49	41	43	674
678	169	171	111	113	83	85	67	69	55	57	47	49	41	43	678
680	169	171	113	115	83	85	67	69	55	57	47	49	41	43	680
684	169	171	113	115	85	87	67	69	55	57	47	49	41	43	682
686	171	173	113	115	85	87	67	69	57	59	47	49	41	43	686
688	171	173	113	115	85	87	67	69	57	59	49	51	41	43	688
690	171	173	113	115	85	87	67	69	57	59	_49	51	43	45	690
694	173	175	115	117	85	87	69	71	57	59	49	51	43	45	692
696	173	175	115	117	85	87	69	71	57	59	49	51	43	45	696
698	173	175	_115	117	87	89	69	71	57	59	49	51	43	45	698
100	1/3	175	115	117	87	89	69	71	57	59	49	51	43	45	700



IV	IULT	IPLE	C-CIR	CUIT	r, sin	IGLE	WIN	IDIN	GS, F	ORI	DRUI	MAR	MAT	URE	s.
ORS		1.5		Sec.	FR	ONT	AND	BACK	PITO	CHES					TORS
LONG		4		6	8	8	1	0	_ 1	2	1	4	1	6	Lonar
F CON	PO	LES	POI	LES	POI	LES	POI	LES	PO	LES	PO	LES	PO	LES	F COP
No. 0	F	В	F	В	F	B	F	В	F	В	F	B	F	В	No. 0
$\frac{702}{704}$	175 175	177 177	115 117	117 119	87 87	89 89	<u>69</u> 69	71 71	57 57	59 59	49 49	51 51	43 43	$\frac{45}{45}$	$\frac{702}{704}$
706 708	$\frac{175}{175}$	$\frac{177}{177}$	117 117	119 119	87 87	89 89	69 69	$\frac{71}{71}$	57 57	59 59	49 49	$\frac{51}{51}$	43 43	$\frac{45}{45}$	706 708
710 712	$\frac{177}{177}$	$\frac{179}{179}$	117 117	119 119	87 87	89 89	69 71	71 73	59 59	$\frac{61}{61}$	49 49	$\frac{51}{51}$	43 43	45 45	710 712
714	177	179	117	119 121	89	91	71	73	59 59	61 61	49	51 53	43	45	714
718	179	181	119	121	89	91	71	73	59	61 61	51	53	43	45	718
722	179	181	119	121	89	91 01	71	73	59		51	53	45	40	722
726	181	183	119	121	89	91	71	73	59	61	51	53	45	47	726
730	181	183	121	123	91	93	71	73	59	61	51	<u>53</u>	45	47	728
732	<u>181</u> <u>183</u>	$\frac{183}{185}$	$\frac{121}{121}$	$\frac{123}{123}$	<u>91</u> 91	93 93	73	75 75	<u>59</u> 61	61 63	51 51	53 53	$\frac{45}{45}$	$\frac{47}{47}$	$\frac{732}{734}$
736	$\frac{183}{183}$	$\frac{185}{185}$	$\begin{array}{r}121\\121\end{array}$	$\frac{123}{123}$	91 91	93 93	73 73	$\frac{75}{75}$	$\frac{61}{61}$	63 63	$\frac{51}{51}$	53 53	45 45	47 47	736 738
$\frac{740}{742}$	$\frac{183}{185}$	185 187	$\begin{array}{r}123\\123\end{array}$	$\frac{125}{125}$	91 91	93 93	73 73	75 75	$\begin{array}{r} 61 \\ 61 \end{array}$	<u>63</u> 63	$\frac{51}{51}$	$\frac{53}{53}$	$\frac{45}{45}$	$\frac{47}{47}$	$\frac{740}{742}$
$\frac{744}{746}$	$\frac{185}{185}$	$\frac{187}{187}$	$\frac{123}{123}$	$\frac{125}{125}$	<u>91</u> 93	93 95	73 73	75 75	$\begin{array}{r} 61 \\ 61 \end{array}$	<u>63</u> 63	<u>53</u> 53	55 55.	$\begin{array}{r} 45 \\ 45 \end{array}$	47 47	$\frac{744}{746}$
748 750	<u>185</u> 187	$\frac{187}{189}$	$\begin{array}{c} 123 \\ 123 \end{array}$	$\frac{125}{125}$	93 93	95 95	73 73	75 75	$\begin{array}{c} 61 \\ 61 \end{array}$	63 63	53 53	<u>55</u> 55	$\frac{45}{45}$	47 47	$\frac{748}{750}$
$\frac{752}{754}$	187 187	189 189	$\frac{125}{125}$	$\frac{127}{127}$	93 93	95 95	75 75	77	61 61	63 63	53 53	55 55	45	47	752
756 758	187 189	<u>189</u> 191	$\frac{125}{125}$	$\frac{127}{127}$	93 93	95 95	· 75 75	77	<u>61</u> 63	63 65	53	55	47	49	756
760	189 189	191 191	$\frac{125}{125}$	$\frac{127}{127}$	93 95	95 97	75	77	<u>63</u>	65 65	53	55	47	49	760
764	<u>189</u> 191	191 193	127 127	129 129	95 95	97 97	75	77	63	65	53	55	47	49	764
768	<u>191</u> 191	193 193	127 127	129 129	95 95	97	75	77	63 63	65	53	55	47	49	768
772	<u>191</u> 193	<u>193</u> 195	127 127	129	95 95	97	77	79	63	65	55	57	47	49	772
776	193	195 195	129	131	95	97	77	79	63	<u>65</u>	55	57	47	49	776
780	193	195	129	131	97	99	77	79	63	65	55	57	41 47	49	780
784	195	197	129	131	97	99	77	79	65	67	55	57	47	49	784
788	195	197	131	133	97	99	77	<u>79</u> 79	65 65	67	<u>55</u>	57	<u>49</u> <u>49</u>	<u>51</u> 51	786
792	197	199	131	133	97	99	79	<u>19</u> 81	65	67	<u>55</u>	57 57	49 49	51 51	790 792
794	197	199	131	133	99	101	79 79	81 81	65 65	67 67	55	<u>57</u> 57	<u>49</u> <u>49</u>	$\frac{51}{51}$	794 796
800	<u>199</u> 199	$\begin{array}{r} 201 \\ 201 \end{array}$	$\begin{array}{r} 131 \\ 133 \end{array}$	$\frac{133}{135}$	99	101	79 79	<u>81</u>	65	67	55	57	49	51	798

r	NULT	TIPLE	E-CIF	RCUI	T SIN	IGLE	WIN	DIN	GS, F	ORI	DRUI	MAR	MAT	URE	5.
TORS					FRO	ONT A	ND I	BACK	PITC	CHES					rors
DUC.		4	(3		8	1	0	1	2	1	4	1	6	DOC
CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	CON
No. 01	F	В	F	В	F	В	F	В	F	В	F	В	F	В	No. 01
802	199	201	133	135	99	101	79	81	65	67	57	59 59	49	51	802
804	201	201	133	135	99	101	79	81	67	69	57	59	49	51	806
808	201	203	133	135	99	101	79	81	67	69	57	59	49	51	808
810	201	203	133	135 127	$101 \\ 101$	103	79 91	81	67	69	57	59	49	51	810
814	201	205	135	137	101	103	81	83	67	69	57	59	49	51	814
816	203	205	135	137	101	103	81	83	67	69	57	59	49	51	816
818	203	205	135	137	101	103	81	83	67	69	57	59	51	53	818
820	$\frac{203}{205}$	205	135	137 137	$101 \\ 101$	103 103	81	83	67	69	57	59	51	<u> </u>	820
824	205	207	137	139	101	103	81	83	67	69	57	59	51	53	824
826	205	207	137	139	103	105	81	83	67	69	57	59	51	53	826
828	205	207	137	139	103	105	81	83	67	69	59	61	51	53	828
830	207	209	137	139	103	105	81	85	69	71	59	61	51	53	830
834	207	209	137	139	103	105	83	85	69	71	59	61	51	53	834
836	207	209	139	141	103	105	83	85	69	71	59	61	51	53	836
838	209	211	139	141	103	105	83	85	69	71	59	61	51	53	838
842	209	211 211	139	141	103 105	$105 \\ 107$	83	85	69	71	59	61	51	53	840
844	209	211	139	141	105	107	83	85	69	71	59	61	51	53	844
846	211	213	139	141	105	107	83	85	69	71	59	61	51	53	846
848	$\frac{211}{911}$	213	141	143	105	107	83	85	69	71	59	61	51	53	848
852	211	213	141	143	105	107	85	87	69	71	59	61	53	55	852
854	213	215	141	143	105	107	85	87	71	73	59	61	53	55	854
856	213	215	141	143	105	107	85	87	71	73	61	63	53	55	856
868	<u>213</u> 913	$\frac{210}{915}$	141	143	107	109	85	87	71	73	61	63	53	55	868
862	215	217	143	145	107	109	85	87	71	73	61	63	53	55	862
864	215	217	143	145	107	109	85	87	71	73	61	63	53	55	864
866	215	217	143	145	107	109	85	87	71	73	61	63	53	55	866
870	215	$\frac{217}{219}$	143	145	107	109	85	87	$\frac{71}{71}$	73	61	63	53	55	808
872	217	219	145	147	107	109	87	89	71	73	61	63	53	55	872
874	217	219	145	147	109	111	87	89	71	73	61	_63	53	55	874
876	217	219	145	147	109	111	87	89	71	73	61	63	53	55	876
880	219	$\frac{221}{221}$	145	147 147	109	111	87	89	73	$\frac{75}{75}$	61	63	53	<u>55</u>	878
882	219	221	145	147	109	111	87	89	73	75	61	63	55	57	882
884	219	221	147	149	109	111	87	89	73	75	63	65	55	_ 57	884
886	221	223	147	149	109	111	87	89	73	75	63	65	55	57	886
890	221	223	147	149	111	111	87	89	73	75	63	65	55	57	890
892	221	223	147	149	111	113	89	91	73	75	63	65	55	57	892
894	223	225	147	149	111	113	89	91	73	75	63	65	55	57	894
896	223	225	149	151	111	113	89	91	73	75	63	65	55	57	896
_900	223	225	149	151	111	113	89	91	73	75	63	65	55	57	900

N	IULT	IPLE	C-CIR	CUIT	r, sin	NGLE	WIN	IDIN	GS, F	OR	DRUI	MAR	MAT	URE	S.
LORS					FRC	NT A	ND I	BACK	PITC	HES					TORS
DNC		4		6		8	1	0	1	2	1	.4	1	6	DUC
F CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PC	LES	PO	LES	F CON
Non O	F	В	F	B	F	B	F	B	F	B	F	B	F	B	No. 0
902	225 225	227 227	149 149	151	111	113	<u>89</u> 89	91	75	77	63	65	55	57	902
906	225	227	149	151	113	115	89	91	75	77	63	65	55	57	906
908	225	227	151	153	113	115	89	91	75	77	63	65	55	57	908
910	227	229	151	153	113	115	91	91	75	77	63	67	55	57	910
914	227	229	151	153	113	115	91	93	75	77	65	67	57	59	914
916	227	229	151	153	113	115	91	93	75	77	65	67	57	59	916
918	229	231	151	153	113	115	91	93	75	77	65	67	57	59	918
920	229	231	153	$100 \\ 155$	115	115	91	93	75	77	65	67	57	59	920
924	229	231	153	155	115	117	91	93	75	77	65	67	57	59	924
926	231	233	153	155	115	117	91	93	77	79	65	67	57	59	926
928	231	233	153	155	115	117	91	93	77	79	65	67	57	59	928
932	231	233	155	157	115	117	91	95	77	79	65	67	57	59	930
934	233	235	155	157	115	117	93	95	77	79	65	67	57	59	934
936	233	235	155	157	115	117	93	95	77	79	65	67	57	59	936
938	233	235	155	157	117	119	93	95	77	79	65	67	57	59	938
940	235	230	155	157	117	119	93	95	77	79	67	69	57	59	940
944	235	237	157	159	117	119	93	95	77	79	67	69	57	59	944
946	235	237	157	159	117	119	93	95	77	79	67	69	59	61	946
948	235	237	157	159	117	119	93	95	77	79	67	69	59	61	948
952	237	239	157	159	117	119	95	95	79	81	67	69	59	61	950
954	237	239	157	159	119	121	95	97	79	81	67	69	59	61	954
956	237	239	159	161	119	121	95	97	79	81	67	69	59	·61	956
958	239	241	159	161	119	121	95	97	79	81	67	69	59	61	958
962	239	241	159	161	119	121	95	97	79	81	67	60	59	61	960
964	239	241	159	161	119	121	95	97	79	81	67	69	59	61	964
966	241	243	159	161	119	121	95	97	79	81	67	69	59	61	966
968	241	243	161	163	119	121	95	97	79	81	69	71	59	61	968
972	241	243	161	163	121	123 123	95	99	79	81	69	71	59	61	970
974	243	245	161	163	121	123	97	99	81	83	69	71	59	61	974
976	243	245	161	163	121	123	97	99	81	83	69	71	59	61	976
978	243	245	161	165	121	123	97	99	81	83	69	71	61	63	978
982	245	247	163	165	$121 \\ 121$	123	97	99	81	83	69	71	61	63	980
984	245	247	163	165	121	123	97	99	81	83	69	71	61	63	984
986	245	247	163	165	123	125	97	99	81	83	69	71	61	63	986
988	245	241	163	165	123	125	97	99	81	83	69	71	61	63	988
992	247	249	165	167	123	125	99	101	81	83	69	71	61	63	9992
994	247	249	165	167	123	125	99	101	81	83	69	71	61	63	994
996	247	249	165	167	123	125	99	101	81	83	71	73	61	63	996
1000	249	251	165	167	123	125	99	101	83	85	71	73	61	63	998
2000	LIU	AUT	100	101	120	120	09	101	03	60	11	13	101	03	1000

I	IULT	IPLE	CIR	CUIT	, SIN	IGLE	WIN	DIN	GS, F	ORI	DRUN	AR	MAT	URE	5.
ORS					FRC	NT A	ND H	BACK	PITC	HES					rors
DUCI	4	ł	6	3	8	3	1	0	1	2	1	4	1	6	DUCT
CON	PO	LES	PO	LES	PO	LES	Po	LES	PO	LES	PO	LES	PO	LES	CON
40. OF	F	В	F	В	F	В	F	В	F	В	F	В	F	В	No. 0F
1002	249	251	165	167	125	127	99	101	83	85	71	73	61	63	1002
1004 1006	$\frac{249}{251}$	$\frac{251}{253}$	$167 \\ 167$	$\frac{169}{169}$	$\frac{125}{125}$	$\frac{127}{127}$	99	$101 \\ 101$	83	85	71	73	61	63	1004
1008	251	253	167	169	125	127	99	101	83	85	71	73	61	63	1008
1010	$\frac{251}{951}$	253	167	169	125 195	127	99	101 103	83	85	71	73	63	65	1010 1012
1012 1014	253	255	167	169	125	127	101	103	83	85	71	73	63	65	1012
1016	253	255	169	171	125	127	101	103	83	85	71	73	63	65	1016
1018	253	255	169 169	171	127	$\frac{129}{129}$	101	103 103	83	85	$\frac{71}{71}$	73	63	65	1018
1020	255	257	109	171	127	129	101	103	85	87	71	73	63	65	1020
1024	255	257	169	171	127	129	101	103	85	87	73	75	63	65	1024
1026 1028	255	257	169	171	127 197	129	101	103	85	87	73	75	63	65	1026
1020	257	259	171	173	127	129	101	103	85	87	73	75	63	65	1020
1032	_257	259	171	173	127	129	103	105	85	87	73	75	63	_65_	1032
1034	257	259	171	173	129	131	103	105	85	87	73	75	63	65	1034
1036	257	$\frac{239}{261}$	171	$\frac{173}{173}$	129 129	131 131	103 103	105	85	87	73	75	63	65	1036
1040	259	261	173	175	129	131	103	105	85	87	73	75	63_	65	1040
1042	259	261	173	175	129	131	103	105	85	87	73	75	65	67	1042
1044	269	261	173	175	129 129	131	103	105	80	87	73	75	65	67	1044
1048	261	263	173	175	129	131	103	105	87	89	73	75	65	67	1048
1050	261	263	173	175	131	133	103	105	87	89	73	75	65	67	1050
1052	261	263	$\frac{175}{175}$	177	131	133	105	107	87	89	75	77	65	67	1052
1054	263	265	175	177	131	133	$103 \\ 105$	107	87	89	75	77	65	67	1054
1058	263	265	175	177	_131	_133	105	107	87	89	75	77	65	67	1058
1060	263	265	175	177	131	133	105	107	87	89	75	77	65	67	1060
1064	265	267	177	179	131	133	$105 \\ 105$	107	87	89	75	77	65	67	1064
1066	265	267	177	179	133	135	105	107	87	89	75	77	65	67	1066
1068	265	267	177	179	133	135	105	_107	87	89	75	77	65	67	1068
1070	$\frac{207}{267}$	$\frac{269}{269}$	177	$179 \\ 179$	133	135	105	107	89	91	75	77	65	67	1070
1074	267	269	177	179	133	135	107	109	89	91	75	77	67	69	1074
1076	267	269	179	181	133	135	107	109	89	91	75	77	67	69	1076
1078	269	$\frac{271}{271}$	179	181	133	135	107	109	89	91	75	77	67	69	1078
1082	269	271	179	181	135	137	107	109	89	91	77	79	67	69	1080
1084	269	271	179	181	135	137	107	109	89	91	77	79	67	69	1084
1086	271	273	179	$181 \\ 183$	135 135	137	107	109	89	91	77	79	67	69	1086
1090	271	273	181	183	135	137	107	109	89	91	77	79	67	69	1088
1092	271	273	181	183	135	137	109	111	89	. 91	77	79	67	69	1092
1094	273	275	181	183	135	137	109	111	91	93	77	79	67	69	1094
1098	273	275	181	183	$135 \\ 137$	137	109	111	91	93	77	79	67	69	1096
1100	273	275	183	185	137	139	109	111	91	93	77	79	67	69	1100



N	IULT	IPLE	-CIR	сил	, SIN	IGLE	WIN	DIN	GS, F	OR	DRUN	M AR	MAT	URES	5.
rors				-	FR	ONT	AND	BACK	PITO	CHES					rors
DUCI		4		6		8	1	0	1	2	1	4	1	6	DUCI
CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	CON
No. 0F	F	B	F	В	F	В	F	В	F	В	F	В	F	В	40. OF
1102	275	277	183	185	137	139	109	111	91	93	77	79	67	69	1102
1104	275	277	183	185	137	139	109	111	91	93	77	79	67	69	1104
1106	215	277	183	185	137	139	109	111	91	93	70	<u>79</u> 81	69	71	1106 1108
1110	277	279	183	185	137	139	109	111	$-\frac{31}{91}$	93	79	81	69	71	1110
1112	277	279	185	187	137	139	_111	113	91	93	79	81	69	71	1112
1114	277	279	185	187	139	141	111	113	91	93	79	81	69	71	1114
1116	277	279	185	187	139	141	111	113	91	93	79	81	69	71	1116
1120	279	281	185	187	139	141	111	113	93	95	79	81	69	$\frac{71}{71}$	1120
1122	279	281	185	187	139	141	111	113	93	95	79	81	69	71	1120
1124	279	281	187	189	139	141	111	113	93	95	79	81	69	71	1124
1126	281	283	187	189	139	141	111	113	93	95	79	81	69	71	1126
1128	281	283	187	189	1 139	141	111	113	93	95	79	81	69	71	1128
1132	281	283	187	189	141	143	113	115	93	95	79	81	69	71	1130
1134	283	285	187	189	141	143	113	115	93	95	79	81	69	71	1134
1136	283	285	189	191	141	143	113	115	93	95	81	83	69	71	1136
1138	283	285	189	191	141	143	113	115	93	95	81	83	71	73	1138
1140	283	280	189	191	141	143	$-\frac{113}{112}$	115	93	95	81	83	71	73	1140
1144	285	287	189	191	141	143	113	115	95	97	81	83	71	73	1142
1146	285	287	189	191	143	145	113	115	95	97	81	83	71	73	1146
1148	285	287	191	193	143	145	113	115	95	97	81	83	71	73	1148
1150	287	289	191	193	143	145	_113	115	95	97	81	83	71	73	1150
1102 1154	287	289	$191 \\ 191$	193	143	140	115	117	95	97	81	83	71	73	1152 1154
1156	287	289	191	193	143	145	115	117	95	97	81	83	71	73	1154
1158	289	291	191	193	143	145	115	117	95	97	81	83	71	73	1158
1160	289	291	193	195	143	145	115	117	95	97	81	83	71	73	1160
1162	289	291	193	195	145	147	115	117	95	97	81	83	71	73	1162
1166	209	291	195	195	145	147	115	117	95	97	83	85	71	73	1164
1168	291	293	193	195	145	147	115	117	97	99	83	85	71	73	1168
1170	291	293	193	195	145	147	115	117	97	99	83	85	73	75	1170
1172	291	293	195	197	145	147	117	_119	97	99	83	85	73	75	1172
1174 1176	293	295	195	197	145	147	117	119	97	99	83	* 85	73	75	1174
1178	293	295	195	197	145	147	117	119	97	99	83	85	73	75	1176 1178
1180	293	295	195	197	147	149	117	119	97	99	83	85	73	75	1180
1182	295	297	195	197	147	149	117	119	97	99.	83	85	73	75	1182
1184	295	297	197	199	147	149	117	119	_ 97	99	83	85	73	75	1184
1180	295	297	197	199	147	149	117	119	97	99	83	85	73	75	1186
1190	297	299	197	199	147	149	117	119	91	101	83	85	73	75	1188
1192	297	299	197	199	147	149	119	121	99	101	85	87	73	75	1192
1194	297	299	197	199	149	151	119	121	99	101	85	87	73	75	1194
1196	297	299	199	201	149	151	119	121	_ 99	101	85	87	73	75	1196
1200	299	301	199	201	149	151	119	121	99	101	85	87	73	75	1198
LAUU	200	001	100	201	143	101	113	121	99	101	85	81	13	10	1200

.

Above choice of Pitches will prove most satisfactory, although as stated in text, the absolute magnitude of average pitch may be varied within reasonable limits.

1

IV	IULT	IPLE	-CIR	CUIT	r, sin	IGLE	WIN	DIN	GS, F	ORI	DRUI	MAR	MAT	URE	s.
SHO.				E.T.	FR	TNC	AND	BACK	PITO	CHES			2.24		ORS
NDUCT	Do	4		3		8	1	0	1	2	1	4	1	6	TOUGN
F CO	PO	LES	PO	LES	PO.	LES	P0.	LES	PO	LES	PO	LES	PO	LES	F CO
N 0.0	F	B	F	B	F	B	F	B	F	B	F	B	F	B	No. 0
$\frac{1202}{1204}$	$\frac{299}{299}$	301	<u>199</u> 199	$\begin{array}{c c} 201 \\ \hline 201 \end{array}$	149	$\frac{151}{151}$	<u>119</u> 119	$\begin{array}{r} 121 \\ 121 \end{array}$	<u>99</u> 99	$\begin{array}{c c} 101 \\ 101 \end{array}$	85	87	75	77	$\begin{array}{r} 1202 \\ 1204 \end{array}$
$1206 \\ 1208$	301	303	<u>199</u> 201	201	149	151	119 119	121 121	99 99	101	85 85	87	75	77	$1206 \\ 1208$
1210	301	303	201	203	151	153	119	121	99	101	85	87	75	77	1210
1212	303	305	201	203	151	153	121	123	101	101	85	87	75	77	1212
$\frac{1216}{1218}$	303	305 305	$\begin{array}{r} 201 \\ \hline 201 \end{array}$	$\frac{203}{203}$	$151 \\ 151$	153 153	$\begin{array}{r} 121 \\ 121 \end{array}$	$\begin{array}{r} 123 \\ 123 \end{array}$	$\begin{array}{r} 101 \\ 101 \end{array}$	$103 \\ 103$	85	87 87	75	77	$\begin{array}{r} 1216 \\ 1218 \end{array}$
$\frac{1220}{1222}$	<u>303</u> 305	<u>305</u> <u>307</u>	203 203	$\begin{array}{r} 205 \\ \hline 205 \end{array}$	$\begin{array}{r} 151 \\ 151 \end{array}$	$\frac{153}{153}$	$\begin{array}{r} 121 \\ 121 \end{array}$	$\begin{array}{r} 123 \\ 123 \end{array}$	$\begin{array}{r} 101 \\ 101 \end{array}$	$103 \\ 103$	87	89 89	75	77	$\begin{array}{r} 1220 \\ 1222 \end{array}$
$\frac{1224}{1226}$	$\begin{array}{r} 305 \\ 305 \end{array}$	307 307	$\begin{array}{ c c c }\hline 203\\\hline 203\end{array}$	$\begin{array}{r} 205 \\ 205 \end{array}$	151 153	$\begin{array}{r} 153 \\ 155 \end{array}$	$\begin{array}{r} 121 \\ 121 \end{array}$	$\begin{array}{r} 123 \\ 123 \end{array}$	$\begin{array}{r} 101 \\ 101 \end{array}$	$\begin{array}{r}103\\103\end{array}$	87	<u>89</u> 89	75	77	$\frac{1224}{1226}$
$\frac{1228}{1230}$	305 307	307 309	203 203	$\frac{205}{205}$	153 153	$155 \\ 155$	121 121	123 123	101 101	103	87	89 89	75	77	1228
$\frac{1232}{1234}$	307	309	205	207	153	155	123	125	101	103	87	89	75	77	1232
1236	307	309	205	207	153	155	123 123	125 125 195	101	103 103 105	87	89	77	79	1236
1238 1240 1040	309	311	205	207	153	$\frac{155}{155}$	$\frac{123}{123}$	$125 \\ 125$	103	105 105	87	89 89	77	79 79	$\frac{1238}{1240}$
$\frac{1242}{1244}$	309	311 311	$\frac{205}{207}$	207 209	$\frac{155}{155}$	$\frac{157}{157}$	$\frac{123}{123}$	$\frac{125}{125}$	$\frac{103}{103}$	$105 \\ 105$	87	<u>89</u> 89	77	79 79	$\begin{array}{r} 1242 \\ 1244 \end{array}$
$\frac{1246}{1248}$	$\frac{311}{311}$	$\frac{313}{313}$	207	$\frac{209}{209}$	$\frac{155}{155}$	$\frac{157}{157}$	$\begin{array}{r} 123 \\ 123 \end{array}$	$\frac{125}{125}$	$\begin{array}{r}103\\103\end{array}$	$\begin{array}{r} 105 \\ 105 \end{array}$	87	89 91	77	79 79	$\begin{array}{r} 1246 \\ 1248 \end{array}$
$\frac{1250}{1252}$	$\frac{311}{311}$	$\frac{313}{313}$	$\frac{207}{207}$	$\frac{209}{209}$	$\frac{155}{155}$	$\frac{157}{157}$	$\frac{123}{125}$	$\frac{125}{127}$	$\begin{array}{r} 103 \\ 103 \end{array}$	$\frac{105}{105}$	<u>89</u> 89	91 91	77	<u>79</u> 79	$\begin{array}{r}1250\\1252\end{array}$
$\frac{1254}{1256}$	313 313	$\frac{315}{315}$	$\frac{207}{209}$	$\frac{209}{211}$	$\frac{155}{155}$	157 157	$\frac{125}{125}$	$\frac{127}{127}$	103 103	$105 \\ 105$	89 89	91 91	77	79 79	1254 1256
$\frac{1258}{1260}$	313 313	315 315	209	211 211	157 157	159 159	125	$\frac{127}{127}$	103	105	89	91 91	77	79	$1258 \\ 1260$
1262 1264	315	317	209	211	157 157	159	125	127	105	107	89	91	77	79	1262
1266	315	317	209	211 211 212	157	159	$120 \\ 125 \\ 195$	$\frac{127}{127}$	105	107 107	89	91	79	81	1204 1266
1270	317	319	211	213	157	159	125	$\frac{121}{127}$	105	107	89	91	79	81	1208
1274 1274	317 317	$\frac{319}{319}$	211 211	$\frac{213}{213}$	$\frac{157}{159}$	$\frac{159}{161}$	$\frac{127}{127}$	$129 \\ 120 \\ 120 $	$\frac{105}{105}$	$107 \\ 107$	89	<u>91</u> 91	79	81 81	$\frac{1272}{1274}$
$\frac{1276}{1278}$	$\frac{317}{319}$	319 321	$\frac{211}{211}$	$\frac{213}{213}$	$\frac{159}{159}$	$\frac{161}{161}$	$\frac{127}{127}$	$\frac{129}{129}$	$\frac{105}{105}$	$\frac{107}{107}$	$\frac{91}{91}$	<u>93</u> 93	79 79	<u>81</u> 81	$\frac{1276}{1278}$
$\frac{1280}{1282}$	$\frac{319}{319}$	$\frac{321}{321}$	$\frac{213}{213}$	$\frac{215}{215}$	$\frac{159}{159}$	$\underline{161}$	$\begin{array}{r} 127 \\ 127 \end{array}$	$\frac{129}{129}$	$\frac{105}{105}$	$\frac{107}{107}$	91 91	<u>93</u> 93	79 79	81 81	$\begin{array}{r} 1280 \\ 1282 \end{array}$
$\frac{1284}{1286}$	$\frac{319}{321}$	$\frac{321}{323}$	$\frac{213}{213}$	$\frac{215}{215}$	$\frac{159}{159}$	$\frac{161}{161}$	$\frac{127}{127}$	$\frac{129}{129}$	$\frac{105}{107}$	$\frac{107}{109}$	91 91	93 93	79 79	81 81	$\frac{1284}{1286}$
$\frac{1288}{1290}$	$\frac{321}{321}$	323 323	$\begin{array}{c} 213 \\ 213 \end{array}$	$\frac{215}{215}$	159 161	$\frac{161}{163}$	$\frac{127}{127}$	129 129	$\frac{107}{107}$	109 109	91 91	93 93	79 79	81 81	1288 1290
1292 1294	321 323	323 325	$\frac{215}{215}$	217 217	161	$\frac{163}{163}$	129	131 131	107	109	91	93	79	81	1292
1296 1298	323	325	215	217	161	163	129	131	107 107	109	91	93	79	81	1294
1300	323	325	215	217	161	163	129	131	107	$109 \\ 109$	91	93	81	83	1298

N	ULT	IPLE	E-CIR	CUIT	r, sii	NGLE	e win	IDIN	GS, F	OR	DRUI	MAR	MAT	URE	s.
TORS					FRC	DNT A	ND E	ACK	PITC	HES					TORS
DAG	4	4	(3		8	1	0	1	2	1	4	1	6	DUCT
CON	PO	LES	PO	LES	PO	LES	PO	LES	, PO	LES	PO	LES	PO	LES	CON
No. 0F	F	В	F	В	F	В	F	В	F	В	F	В	F	В	No. 0F
1302	325	327	215	217	161	163	129	131	107	109	91	93	81	83	1302
1304	325	327	$\frac{217}{217}$	219	$161 \\ 163$	165	129 129	131	107	109	93	95	81	83	1304
1308	325	327	217	219	163	165	129	131	107	109	93	95	81	83	1308
1310	327	329	217	219	163	165	129	131	109	111	93	95	81	83	1310
1312	327	329	217	219	163	165	131	133	109	111	93	95	81	83	1312
1314	327	329	217	219	163	165	131	133	109	111	93	95	81	83	1314
1318	329	331	219	221	163	165	131	133	109	111	93	95	81	83	1318
1320	329	331	219	221	163	165	131	133	109	111	93	95	81	83	1320
1322	329	331	219	221	165	167	131	133	109	111	93	95	81	83	1322
$\frac{1324}{1326}$	329	333	$\frac{219}{219}$	221	165	167	$\frac{131}{131}$	133	109		93	95	81	83	$1324 \\ 1396$
1328	331	333	221	223	165	167	131	133	109	111	93	95	81	83	1320 1328
1330	331	333	221	223	165	167	131	133	109	111	93	95	83	85	1330
1332	331	333	221	223	165	167	133	135	109	111	95	97	83	85	1332
1334	333	335	221	223	165	167	133	135	111	113	95	97	83	85	1334
1338	333	335	221	223	167	169	133	135		113	95	97	83	85	1330
1340	333	335	223	225	167	169	133	135	111	113	95	97	83	85	1340
1342	335	337	223	225	167	169	133	135	111	113	95	97	83	85	1342
1344	335	337	223	225	167	169	133	135	111	113	95	97	83	85	1344
$\frac{1340}{1348}$	335	337	223	225	167	169	133	135		113	95	97	83	85	1346
1350	337	339	223	225	167	169	133	$135 \\ 135$	111	113 113	95	97	83	85	1348 1350
1352	337	339	225	227	167	169	135	137	111	113	95	97	83	85	1352
1354	337	339	225	227	169	171	135	137	111	113	95	97	83	85	1354
1356	337	339	225	227	169	171	135	137	111	113	95	97	83	85	1356
1360	339	341	$\frac{225}{225}$	221	169	171	135 135	137	113	110	95	97	83	85	1358 1360
1362	339	341	225	227	169	171	135	137	113	115	97	99	85	87	1362
1364	339	341	227	229	169	171	135	137	113	115	97	99	85	87	1364
1366	341	343	227	229	169	171	135	137	113	115	97	99	85	87	1366
1300	341	343	227	229	171	171	135	137	113	115	97	99	85	87	1368 1970
1372	341	343	227	229	171	173	137	139	113	115	97	99	85	87	1372
1374	_343	345	227	229	171	173	137	139	113	115	97	99	85	87	1374
1376	343	345	229	231	171	173	137	139	113	115	97	99	85	87	1376
1378	343	345	229	231	$171 \\ 171$	173	137	139	113	115	97	99	85	87	1378
1382	345	347	229	231	$\frac{171}{171}$	173	137	139 139	113	110	97	99	85	87	1380 1382
1384	345	347	229	231	171	173	137	139	115	117	97	99	85	87	1384
1386	345	347	229	231	173	175	137	139	115	117	9.7	99	85	87	1386
1388	345	347	231	233	173	175	137	139	115	117	99	101	85	87	1388
1390	347	349	231	233	173	175	137	139	115	117	99	101	85	87	1390
1394	347	349	231	233	173	175	139	141	115	117	99	101	87	89	1394
1396	347	349	231	233	173	175	139	141	115	117	99	101	87	89	1396
1398	349	351	231	233	173	175	139	141	115	117	99	101	87	89	1398
1400	041	001	400	200	115	1.(5	139				00		87	80	14(30)

1

IV	IULT	IPLE	E-CIR	CUIT	r, sin	IGLE	WIN	DIN	GS, F	ORI	DRUN	MAR	MAT	URE	s.
ORS					FRC	NT A	ND E	BACK	PITC	HES					rors
CONDUCT	PO	4 LES	POI	3 LES	PO	8 LES	1 Poi	0 LES	1 Poi	2 LES	1 Po	4 LES	1 P0	6 LES	CONDUCT
No. 0F	F	В	F	В	F	В	F	Β.	F	В	F	В	F	B	No. 0F
$\frac{1402}{1404}$	349 349	$\begin{array}{r} 351 \\ 351 \end{array}$	233 233	$\frac{235}{235}$	$\begin{array}{r} 175 \\ 175 \end{array}$	$\begin{array}{c c} 177 \\ 177 \end{array}$	139 139	141 141	$\frac{115}{115}$	117 117	99 99	101 101	87 87	89 89	$\begin{array}{r} 1402 \\ 1404 \end{array}$
$\frac{1406}{1408}$	$\frac{351}{351}$	353 353	233 233	235 235	$\frac{175}{175}$	$\begin{array}{r} 177 \\ 177 \end{array}$	$\begin{array}{r} 139 \\ 139 \end{array}$	$\frac{141}{141}$	<u>117</u> <u>117</u>	119 119	99 99	$\begin{array}{r} 101 \\ 101 \end{array}$	87	<u>89</u> 89	1406 1408
$\frac{1410}{1412}$	351 351	353 353	233 235	235	$\begin{array}{r} 175 \\ 175 \end{array}$	177	139	141 143	117	$119 \\ 119 \\ 119$	<u>99</u> 99	$101 \\ 101$	87	<u>89</u> 89	<u>1410</u> <u>1412</u>
1414 1416 1410	353 353	355 355	235 235	237	$175 \\ 175 \\ 175 \\ 177 $	$\frac{177}{177}$	$141 \\ 141 \\ 141$	143 143 143	117 117 117	<u>119</u> <u>119</u>	<u>99</u> <u>101</u>	$101 \\ 103 \\ 102$	87 87	<u>89</u> 89	1414 1416 1410
$1418 \\ 1420 \\ 1492 \\ $	353	<u>355</u> 357	$\frac{250}{235}$	$\frac{237}{237}$	177 177 177	179 179 179	$\begin{array}{r} 141 \\ 141 \\ 141 \end{array}$	$\begin{array}{r} 143 \\ 143 \\ 143 \end{array}$	117 117 117	119 119 119	$101 \\ 101 \\ 101$	103 103	87 87	<u>89</u> 89	1418 1420 1420
1424 1424 1426	355 355	$\frac{357}{357}$	$\frac{237}{237}$	239	177	179 179 179	$141 \\ 141 \\ 141$	$143 \\ 143 \\ 143$	117	$119 \\ 119 \\ 119$	$101 \\ 101 \\ 101$	$103 \\ 103 \\ 103$	87 89	89 91	1424 1424 1426
$\frac{1428}{1430}$	355 357	357 359	$\frac{237}{237}$	$\begin{array}{r} 239 \\ 239 \end{array}$	177 177	179 179	1 <u>41</u> 141	$\frac{143}{143}$	$\begin{array}{c} 117 \\ 119 \end{array}$	119 121	101 101	$\frac{103}{103}$	89 89	91 91	$\begin{array}{r}1428\\1430\end{array}$
$\frac{1432}{1434}$	357 357	359 359	237 237	239 239	$\begin{array}{r}177\\179\end{array}$	179 181	143 143	$\begin{array}{r}145\\145\end{array}$	119 119	$\begin{array}{r}121\\121\end{array}$	101 101	103 103	89 89	91 91	$\begin{array}{r} 1432 \\ 1434 \end{array}$
$\frac{1436}{1438}$	357	359 361	239 239	$\begin{array}{r} 241 \\ 241 \\ \end{array}$	179 179	181 181	143 143	145 145	$119 \\ 119$	121 121	101 101	$\begin{array}{r}103\\103\end{array}$	89 89	91 91	1436 1438
$\frac{1440}{1442}$	359 359 250	$\frac{361}{361}$	239 239 239	$\begin{array}{r} 241 \\ 241 \\ 241 \\ 241 \end{array}$	$179 \\ 179 \\ 179 \\ 170 \\ 100 $	$181 \\ 181 \\ 191 $	$\begin{array}{r} 143 \\ 143 \\ 143 \end{array}$	$145 \\ 145 $	119 119 119	121 121 121	101 101 102	103 103 105	89	<u>91</u> 91	1440 1442
1444 1446 1448	361	363 363	$\begin{array}{r} 239 \\ \hline 239 \\ \hline 241 \end{array}$	241 241 243	$179 \\ 179 \\ 179$	181	143 143	$145 \\ 145 $	$119 \\ 119 \\ 119$	121 121 191	103 103 103	$105 \\ 105 $	89 89	91 91	1444 1446 1448
$\frac{1450}{1452}$	$\frac{361}{361}$	363 363	$\frac{241}{241}$	$\frac{243}{243}$	181 181	183 183	$\begin{array}{r} 110\\ 143\\ 145\end{array}$	$\begin{array}{r}145\\147\end{array}$	$\begin{array}{r}119\\119\\\end{array}$	$\frac{121}{121}$	103 103	$\frac{105}{105}$	89 89	91 91	$\begin{array}{r} 1450 \\ 1452 \end{array}$
$\frac{1454}{1456}$	363 363	365 365	$\begin{array}{r} 241 \\ 241 \end{array}$	$\frac{243}{243}$	181 181	183 183	$\frac{145}{145}$	147 147	$\begin{array}{r} 121 \\ 121 \end{array}$	$\frac{123}{123}$	103 103	$\frac{105}{105}$	89 89	91 91	$\begin{array}{r} 1454 \\ 1456 \end{array}$
$\frac{1458}{1460}$	363 363	365 365	$\begin{array}{r} 241 \\ 243 \\ \end{array}$	$\begin{array}{r} 243 \\ 245 \\ \end{array}$	181	183 183	$\frac{145}{145}$	147 147	$\begin{array}{r} 121 \\ 121 \end{array}$	$\begin{array}{r} 123 \\ 123 \\ \end{array}$	103 103	$\frac{105}{105}$	<u>91</u> 91	93 93	$\begin{array}{r} 1458 \\ 1460 \end{array}$
$1462 \\ 1464 \\ 1466 \\ $	365 365	$\frac{367}{367}$	243 243 943	$\begin{array}{r} 245 \\ 245 \\ 945 \end{array}$	181 181 192	183 183	$145 \\ 145 $	$\frac{147}{147}$	$121 \\ 121 \\ 191$	123 123 102	103 103 102	$105 \\ 105 \\ 105$	$\begin{array}{r} 91 \\ 91 \\ 01 \end{array}$	93 93 02	1462 1464
$1468 \\ 1470$	365 367	367 369	243 243 243	$\frac{245}{245}$	183 183	185 185 185	$145 \\ 145 \\ 145$	147 147 147	$121 \\ 121 \\ 121$	123 123 123	103 103 103	$105 \\ 105 \\ 105$	91 91	93 93	1400 1468 1470
$\frac{1472}{1474}$	367 367	369 369	$\frac{245}{245}$	$\frac{247}{247}$	183 183	185 185	$\begin{array}{r} 147 \\ 147 \\ 147 \end{array}$	$\begin{array}{r} 149 \\ 149 \end{array}$	121 121	$\frac{123}{123}$	$105 \\ 105$	$107 \\ 107$	91 91	93 93	$\frac{1472}{1474}$
$\frac{1476}{1478}$	$\frac{367}{369}$	369 371	$\frac{245}{245}$	$\frac{247}{247}$	183 183	185 185	$\begin{array}{r}147\\147\end{array}$	$\begin{array}{r}149\\149\end{array}$	$\begin{array}{r}121\\123\end{array}$	$\begin{array}{c} 123 \\ 125 \end{array}$	$\begin{array}{r}105\\105\end{array}$	$\begin{array}{r}107\\107\end{array}$	91 91	93 93	$\frac{1476}{1478}$
$\frac{1480}{1482}$	369 369	371 371	$\frac{245}{245}$	$\frac{247}{247}$	183	185 187	147	149 149	$123 \\ 123 \\ 100$	$\frac{125}{125}$	$105 \\ 105$	$\frac{107}{107}$	91 91	93 93	1480 1482
$\begin{array}{r} 1484 \\ 1486 \\ 1.188 \end{array}$	369 371 371	$\frac{371}{373}$	$\frac{247}{247}$	249 249 949	185 185 195	187	147 147 147	$149 \\ 149 \\ 149 \\ 140 $	123 123 192	$125 \\ 125 \\ 195 $	$105 \\ 105 \\ 105$	107 107 107	91 91 01	93 93	1484 1486 1486
$1490 \\ 1492$	371 371	373	$\frac{247}{247}$	$\frac{249}{249}$	185	187 187 187	147	149 149 151	$\begin{array}{r}123\\123\\123\end{array}$	$125 \\ 125 \\ 125$	$105 \\ 105 \\ 105$	107 107 107	93 93	95 95	1488 1490 1492
$\frac{1494}{1496}$	373 373	375 375	$\frac{247}{249}$	$\frac{249}{251}$	185 185	187 187	149 149	151 151	123 123	$\frac{125}{125}$	$105 \\ 105$	107 107	93 93	95 95	$1494 \\ 1496$
$\frac{1498}{1500}$	373 373	$\frac{375}{375}$	$\frac{249}{249}$	$\frac{251}{251}$	187 187	189 189	149 149	$\frac{151}{151}$	$\begin{array}{r}123\\123\end{array}$	$\frac{125}{125}$	$\begin{array}{c} 105 \\ 107 \end{array}$	$\frac{107}{109}$	93 93	95 95	1498 1500



M	ULT	IPLE	-CIR	сил	, SIN	IGLE	WIN	DIN	GS, F	OR	DRUN	A AR	MAT	URES	5.
ORS					FRC	NT A	ND E	BACK	PITC	HES					rors
DUCT		4	(6	8	8	1	0	1	2	1	4	1	6	DUC
CON	PO	LES	PO	LES	PO	LES	POI	LES	PO	LES	PO	LES	POI	LĘS	CON
No. OF	F	B	F	В	F	В	F	B	F	В	F	В	F	В	No.OF
1502	375	377	249	251	187	189	149	151	125	127	107	109	93	95	1502
1504	375	377	249	251	187	189	149	151	125	127	107	109	93	95	1504
1508	375	377	249	253	187	189	$149 \\ 149$	151	125	127	107	109	93	95	1508 1508
1510	377	379	251	253	187	189	149	151	125	127	107	109	93	95	1510
1512	377	379	251	253	187	189	151	153	125	127	107	109	93	95	1512
1514	377	379	251	253	189	191	151	153	125	127	107	109	93	95	1514
1518	379	381	251	253	189	191	151	153	125	127	107	109	93	95	1518
1520	379	381	253	255	189	191	151	153	125	127	107	109	93	95	1520
1522	379	381	253	255	189	191	151	153	125	127	107	109	95	97	1522
1524	379	381	253	255	189	191	151	153	125	127	107 107	109	95	97	1524 1596
1528	381	383	253	255	189	191	151	153	127	129	109	111	95	97	1528
1530	381	383	253	255	191	193	151	153	127	129	109	111	95	97	1530
1532	381	383	255	257	191	193	153	155	127	129	109	111	95	97	1532
1534	383	385	255	257	191	193	153	155	127	129	109	111	95	97	1534
1538	383	385	255	257	191	193	153 153	155	$\frac{127}{197}$	129	109	111	95	97	1538
1540	383	385	255	257	191	193	153	155	127	129	109	111	95	97	1540
1542	385	387	255	257	191	193	153	155	127	129	109	111	. 95	97	1542
1544	385	387	257	259	191	193	153	155	127	129	109	111	95	97	1544
1548	385	387	257	259	193	195	153	155	127	129	109	111	95	97	1546
1550	387	389	257	259	193	195	153	155	129	131	109	111	95	97	1540
1552	387	389	257	259	193	195	155	157	129	131	109	111	95	97	1552
1554	387	389	257	259	193	1.95	155	157	129	131	109	111	97	99	1554
1558	387	389	259	261	193	195	155	157	129	131	111	113	97	99	1556
1560	389	391	259	261	193	195	155	157	129	131	111	113	97	99	1560
1562	389	391	259	261	195	197	155	157	129	131	111	113	97	99	1562
1564	389	391	259	261	195	197	155	157	129	131	111	113	97	99	1564
1566	891	393	259	261	195	197	155	157	129	131	111	113	97	99	1566
1570	891	393	201	263	195	197	155	157	129	131	111	113	97	99	1570
1572	391	393	261	263	195	197	157	159	129	131	111	113	97	99	1572
1574	393	395	261	263	195	197	157	159	131	133	111	113	97	99	1574
1576	393	395	261	263	195	197	157	159	131	133	111	113	97	99	1576
1580	393	395	261	263	197	199	157	159	131	133	111	113	97	99	1578
1582	395	397	263	265	197	199	157	159 159	131 131	133	111	113	97	99	1582
1584	395	397	263	265	197	199	157	159	131	133	113	115	97	99	1584
1586	395	397	263	265	197	199	157	159	131	133	113	115	99	101	1586
1588	395	397	263	265	197	199	157	159	131	133	113	115	99	101	1588
1592	397	399	265	267	197	199	159	161	131	133	113	115	99	101	1590
.1594	397	399	265	267	199	201	159	161	131	133	113	115	99	101	1594
1596	397	399	265	267	199	201	159	161	131	133	113	115	99	101	1596
1598	399	401	265	267	199	201	159	161	133	135	113	115	99	101	1598
1000	000	1 101	400	401	1 199	201	100	101	100	130	113	_110	.99	101	1000

¥

WINDING TABLES FOR MULTIPLE-CIRCUIT, DOUBLE WINDINGS FOR DRUM ARMATURES.



1	MUL	TIPL	E-CI	RCU	IT, I	DOU	BLE	WIN	DINC	CS, F	ORI	DRUI	MAF	RMAT	TURE	ES.
X	ORS				FF	RONT	AND	BAC	K PI	TCHE	ES					ORS
RANC	DUCT	4	4		6		8	1	0	1	2	1	4	1	6	DUCT
ENT	CONI	PO	LES	PO	LES	PO	LES	POI	LES	PO	LES	PO	LES	PO	LES	CON
RE	40.0F	F	В	F	В	F	В	F	В	F	В	F	В	F	·B	40.0F
0	202	49	53	31	35	23	27	19	23	15	19	13	17	11	15	202
00	204	49	53	$\frac{31}{33}$	35	23	27	19	23	15	19	13	17	11	15	204
00	208	49	53	33	37	23	27	$\frac{15}{19}$	$\frac{23}{23}$	15	19	$\frac{13}{13}$	17	11	15	208
0	210	51	55	33	37	25	29	19	23	15	19	13	17	11	15	210
00	212	51	55	33	37	25	29	19	23	15	19	13	17	11	15	212
00	214	51	55	33	37	25	29	19	23	15	19	13	17	11	15	214
D.	218	53	57_	_ 35	39	25	29	19	23	17	21	13	17	11	15	218
00	220	53	_57	35	39	25	29	19	23	17	21	13	17	11	15	220
00	222	53	57	35	39	$\frac{25}{25}$	29	$\frac{21}{91}$	$\frac{25}{25}$	17	$\frac{21}{21}$	13	17		15	222
0	226	55	59	35	39	27	31	21	25	17	21	15	19	13	17	226
00	228	55	59	35	39	27	31	21	25	17	21	15	19	13	17	228
0	230	55	59	37	41	27	31	21	25	17	21	15	19	13	17	230
Q	232	57	61	37	41	$\frac{21}{27}$	31	$\frac{21}{21}$	$\frac{20}{25}$	17	21	15	19	13	17	234
00	236	57	61	37	41	27	31	21	25	17	21	15	19	13	17	236
0	238	57	61	37	41	27	31	21	25	17	21	15	19	13	17	238
00	240	57	61	37	41	27	31	$\frac{21}{92}$	25	17	21	15	19	13	17	240
00	$\frac{244}{244}$	59	63	39	43	29	33	$\frac{23}{23}$	27	$\frac{19}{19}$	23	15	19	13	17	244
Q	246	59	63	39	43	29	33	23	27	19	23	15	19	13	17	246
00	248	59	63	39	43	29	33	23	27	19	23	15	19	13	17	248
<u></u>	$\frac{250}{252}$	61	<u>65</u>	39	43	29	33	23	27	19	23	15	19	13	17	250
Ø	254	61	65	41	45	29	33	23	27	19	23	17	$\frac{15}{21}$	13	17	254
00	256	61	65	41	_ 45 _	29	33	23	27	19	23	17	21	13	17	256
@	258	63	67	41	45	31	35	23	27	19	23	17	21	15	19	258
0	$\frac{200}{262}$	63	67	$\frac{41}{41}$	45	31	35	25	21	19	23	17	$\frac{21}{21}$	15	19	260
00	264	63	67	41	45	31	35	25	29	19	23	17	21	15	19	264
0	266	65	69	43	47	31	35	25	29	21	25	17	21	15	19	266
60	268	65	69	43	41	31	30	25	29	21	25	17	21	15	19	268
00	272	65	69	43	47	31	35	25	29	21	25	17	21	15	19	272
0	274	67	71	43	47	33	37	25	29	21	25	17	21	15	19	274
00	276	67	71	43	47	33	37	25	29	21	25	17	21	15	19	276
00	278	67	71	45	49	33	37	25	29	21	25	17	21	15	19	278
Ø	282	69	73	45	49	33	37	27	$\frac{23}{31}$	$\frac{21}{21}$	25	19	$\frac{21}{23}$	15	19	280
00	284	69	73	45	49	33	37	27	31	21	25	19	23	15	19	284
0	286	69	73	45	49	33	37	27	31	21	25	19	23	15	19	286
0	290	71	75	47	49 51	35	39	27	31	21	25	19	23	15	19	288
00	292	71	75	47	51	35	39	27	31	23	27	19	23	17	21	292
0	294	71	75	47	51	35	39	27	31	23	27	19	23	17	21	294
00	296	71	75	47	51	35	39	27	31	23	27	19	23	17	21	296
00	300	73	77	47	51	35	39	27	31	23	27	19	23	17	21	300



ſ	MUL	TIPL	E-CI	RCU	IT, E	OUE	BLE	WINI	DINC	i, FO	R DI	RUM	ARM	ΙΑΤ	JRES	5.
X	ORS				F	RONT	r AN	D BA	CK PI	ITCH	ES					SHO.
ENTRANC	CONDUCT	POI	4 LES	Po	6 LES	Pot	3 LES	1 Poi	0 LES	1 P0.	2 LES	1 Poi	4 LES	1 P0	6 LES	CONDUCT
ΒĘ	No. OF	F	В	F	В	F	B	F	В	F	В	F	В	F	В	No. OF
0	302	73	77	49	53	35	39	29	33	23	27	19	23	17	21	302
6	304	73	77	49	53	35	39	29	33	23	27	19	23	17	21	304
00	308	75	79	49	53	37	41	29	33	23	27	19	23	17	21	308
0	310	75	79	49	53	37	41	29	33	23	27	21	25	17	21	310
00	312	75	<u>79</u> 81	<u>49</u> 51	<u> </u>	37	41	29	33	25	29	$\frac{21}{21}$	25	17	21	314
00	316	77	81	51	55	37	41	29	33	25	29	21	25	17	21	316
0	318	77	81 *	51	55	37	41	29	33	25	29	21	25	17	21	318
00	$\frac{320}{399}$	77	81	51	55	37	$\frac{41}{43}$	29	33	25	29	$\frac{21}{21}$	25	19	21	320
00	324	79	83	51	55	39	43	31	35	25	29	21	25	19	23	324
Ø	326	79	83	53	57	39	43	31	35	25	29	21	25	19	23	326
00	328	<u>79</u> 81	83	53	$\frac{57}{57}$	39	43	31	35	25	29	$\frac{21}{21}$	$\frac{25}{25}$	19	23	328
00	332	81	85	53	57	39	43	31	35	25	29	21	25	19	23	332
Ø	334	81	85	53	57	39	43	31	35	25	29	21	25	19	23	334
00	336	81	85	53	57	39	43	31	35	25	29	$\frac{21}{92}$	25	19	23	336
00	340	83	87	55	59	41	40	<u>31</u> <u>31</u>	35	21	31	23	27	19	23	340
0	342	83	87	55	59	41	45	33	37	27	31	23	27	19	23	342
00	344	83	87	55	59	41	45	33	37	27	31	23	27	19	23	344
60	346	85	89	55	59	_41	45	33	37	27	31	23	27	19 19	23	$\frac{346}{348}$
0	350	85	89	57	61	41	45	33	37	27	31	23	27	19	23	350
00	352	85	89	57	61	41	45	33	37	27	31	23	27	19	23	352
Q	354	87	91	_57	61	43	47	83	37	27	31	23	27	21	25	354
00	358	87	91	57	61	43	47	00	37	21	31	$\frac{23}{23}$	27	21	25	358
00	360	87	91	57	61	43	47	33	37	27	31	23	27	21	25	360
Ø	362	89	93	59	63	43	47	35	39	29	33	23	27	21	25	362
00	364	89	93	59	63	43	47	35	39	29	33	23	27	$\frac{21}{91}$	25	364
00	368	89	93	59	63	43	47	35	39	29	33	25	29	21	25	368
0	370	91	95	59	63	45	49	35	39	29	33	25	29	21	25	370
00	372	. 91	95	59	63	45	49	35	39	29	33	25	29	21	25	372
00	376	91	95	$\frac{-61}{-61}$	65	40	49	35	39	29	33	25	29	21	25	376
Ø	378	93	97	61	65	45	49	35	39	29	33	25	29	21	25	378
00	380	93	97	61	65_	45	49	35	39	29	33	25	29	21	25	380
@ 00	382	$-\frac{93}{93}$	97	61 61	65	45	49	37	41	29	33	25	29	$\frac{21}{91}$	25	$\frac{382}{384}$
0	386	95	99	63	67	47	51	37	41	31	35	25	29	23	27	386
00	388	95	99	63	67	47	51	37	41	31	35	25	29	23	27	388
Q	390	95	99	63	67	47	51	37	41	31	35	25	29	23	27	390
0	394	95	101	68	67	47	51	37	41	- 31	35	25	29	23	27	392
00	396	97	101	63	67	47	51	37	41	31	35	27	31	23	27	396
0	398	97	101	65	69	47	51	37	41	31	35	27	31	23	27	398
00	400	91	101	65	69	47	51	37	41	31	35	27	31	23	27	400

	MULTIPLE-CIRCUIT, DOUBLE WINDINGS, FOR DRUM ARMATURES.															
7	ORS			4	FF	RONT	AND	BAC	K PI	TCHE	ES			645		ORS
RANG	DUCT	4	'±	(6		8		10		12		14		16	
ENT	CON	POI	POLES		POLES		POLES		POLES		POLES		POLES		POLES	
8	No. 0F	F	В	F	В	F	В	F	В	F	В	F	В	F	В	No. 0F
Ø	402	99	103	65	69	49	53	39	43	31	35	27	31	23	27	402
00	404 406	99	$\frac{103}{103}$	<u>65</u>	<u>69</u>	49	53	39	$\frac{43^{\circ}}{43}$	31	35	27	31	23	27	404 406
00	408	99	103	65	69	49	53	39	43	31	35	27	31	23	27	408
00	410	$\frac{101}{101}$	$105 \\ 105$	67	$\frac{71}{71}$	49	53	39	$\frac{43}{43}$	33	37	27	31	23	27	410
Ø	414	101	105	67	71	49	53	39	43	33	37	27	31	23	27	414
00	416	101	105	67	71	49	53	39	43	33	37	27	31	23	27	416
00	410	$\frac{103}{103}$	107	67	71	$51 \\ 51$	55	39	43	33	37	27	31	$\frac{25}{25}$	29	410
@	422	103	107	69	73	51	55	41	45	33	37	29	33	25	29	422
<u> </u>	$\frac{424}{426}$	$103 \\ 105$	107	69	73	51 - 51	55	$\frac{41}{41}$	$\frac{45}{45}$	33	37	29	33	$\frac{25}{25}$	29	$\frac{424}{426}$
00	428	105	109	69	73	51	55	41	45	33	37	29	33	25	29	428
0	$430 \\ 432$	$105 \\ 105$	$109 \\ 109$	<u>69</u>	73	51	55	41	45	33	37	29	33	25	29	430
Ø	434	107	111	71	75	53	57	41	45	35	39	29	33	25	29	434
00	436	107	111	71	75	53	57	41	45	35	39	29	33	25	29	436
00	$\frac{438}{440}$	107	111	71	75	53	57	41	45	35	39	29	33	25	29	438
Q	442_	109	113	71	75	_53	57	43	47	35	39	29	33	25	29	442
00	444	109	113	71	75	53	57	43	47	35	39	29	33	25	29	444
00	440	109	113	73	77	53	57	43	47	35	39	29	33	25	29	448
Ø	450	111	115	73	77	55	59	43	47	35	39	31	35	27	31	450
<u> </u>	454	111	115	73	77	55	<u>59</u> 59	43	47	35	39	31	35 35	27	31	452
00_	456	111	115	73	77	55	59	43	47	35	39	31	35	27	31	456
0	458	113	117	75	79	55	59	43	47	37	41	31	35	27	31	458
00 @	$\frac{460}{462}$	$\frac{113}{113}$	$\frac{117}{117}$	75	79	<u> </u>	<u> </u>	$\frac{43}{45}$	47	37	41	$\frac{31}{31}$	35	27	$\frac{31}{31}$	460
00	464	113	117	75	79	55	59	45	49	37	41	31	35	27	31	464
00	$\frac{466}{468}$	$\frac{115}{115}$	$\frac{119}{119}$	$\frac{75}{75}$	$\frac{79}{79}$	57 57	<u>61</u> 61	45	$\frac{49}{49}$	37	41	$\frac{31}{31}$	$\frac{35}{35}$	27	31	466
Ø	470	115	119	77	81	57	61	45	49	37	41	31	35	27	31	470
00	472	115	119	77	81	57	61	45	49	37	41	31	35	27	31	472
00	476	$\frac{117}{117}$	$\frac{121}{121}$	77	81	57	61	45	$\frac{49}{49}$	37	41	31	$\frac{30}{35}$	27	31	474
Ø	478	117	121	77	81	57	61	45	49	37	41	33	37	27	31	478
00	480	117	$\frac{121}{193}$	77	81	57	61	45	49	37	41	33	37	27	31	480
00	484	119	123	79	83	59	63	47	51	39	43	33	37	29	33	484
Ø	486	119	123	79	83	59	63	47	51	39	43	33	37	29	33	486
00 ©	488	$119 \\ 121$	$\frac{123}{125}$	79	83	59	63	47	51	39	43	33	37	29	33	488
00	492	121	125	79	83	59	63	47	51	39	43	33	37	29	33	492
0	494	121	125	81	85	59	63	47	51	39	43	33	37	29	33	494
@	498	121	125	81	85	<u> </u>	65	47	$\frac{51}{51}$	39	43	33	37	29	33	496
00	500	123	127	81	85	61	65	47	51	39	43	33	37	29	33	500

1	MULTIPLE-CIRCUIT, DOUBLE WINDINGS, FOR DRUM ARMATURES.															
X	ORS	FRONT AND BACK PITCHES														ORS
RANC	DUCT	4 6 POLES POLES		3	8	3	10		12		1	4	16		DUCT	
ENT	CON			POLES		POLES		POLES		POLES		POLES		POLES		CON
RE	No. OF	F	В	F	В	F	В	F	В	F	В	F	В	F	В	No. OF
Ø	502	123	127	81	85	61	65	49	53	39	43	33	37	29	33	502
00	504	123	127	81	85	61	65	49	53	39	43	33	37	29	33	504
00	508	125	$129 \\ 129$	83	87	61	65	49	53	41	45	35	39	29	33	508
Ø	510	125	129	83	87	61	65	49	53	41	45	35	39	29	33	510
00	512	125	129	83	87	61	65	49	53	41	45	35	39	29	33	512
Ø	514	127	131	83	87	63	67	49	53	41	45	35	39	31	35	514
00	516	127	131	83	87	63	67	49	53	41	45	35	39	$\frac{31}{21}$	35	516
00	520	127	131	85	89	63	67	49	53	41	45	35	39	31	35	520
Q	522	129	133	85	89	63	67	51	55	41	45	35	39	31	35	522
00	524	129	133	85	89	63	67	51	55	41	45	35	39	31	35	524
Q	526	129	133	85	89	63	67	51	55	41	45	35	39	31	35	526
00	520	129	133	80	01	65	69	51	55	41	40	35	30	31	35	530
00	532	131	135	87	91	65	69	51	55	43	47	35	39	31	35	532
Ø	534	131	135	87	91	65	69	51	55	43	47	37	41	31	35	534
00	536	131	135	87	91	65	69	51	55	43	47	37	41		35	536
Ø	538	133	137	87	91	65	69	51	55	43	47	37	41	31	35	538
00	540	133	137	87	91	65	69	52	<u>57</u>	43	47	31	41	31	35	549
00	544	133	137	89	93	65	69	53	57	43	47	37	41	31	35	544
Ø	546	135	139	89	93	67	71	53	57	43	47	37	41	33	37	546
00	548	135	139	89	93	67	71	53	57	43	47	37	41	33	37	548
Ø	550	135	139	89	93	67	71	53	57	43	47	37	41	33	37	550
00	554	130	141	01	93	67	71	53	57	40	41	31	41	33	37	554
00	556	137	141	91	95	67	71	53	57	45	49	37	41	33	37	556
0	558	137	141	91	95	67	71	53	57	45	49	37	41	33	37	558
00	560	137	141	91	95_	_67	71	53	57	_45_	49	37	41	33	37	_560
Ø	562	139	143	91	95	69	73	55	59	45	49	39	43	33	37	562
00	564	139	143	91	95	69	73	55	59	45	49	39	43	33	37	566
00	568	139	$143 \\ 143$	93	97	69	73	55	59	45	49	39	43	33	37	568
Ø	570	141	145	93	97	69	73	55	59	45	49	39	43	33	37	570
00	572	141	145	_ 93	97	69	73	55	59	45	49	39	43	33	37	572
Ø	574	141	145	93	97	69	73	55	59	45	49	39	43	33	37	574
00	576	141	145	93	97	69	73	55	59	45	49	39	43	33		579
00	580	143	147	95	- 99	71	75	55	59	47	51	$\frac{39}{39}$	43	35	39	580
Ø	582	143	147	95	99	71	75	57	61	47	51	39	43	35	39	582
00	584	143	147	95	99	71	75	57	61	47	51	39	43	35	39	584
Ø	586	145	149	95	99	71	_75_	57	61	47	_51	39	43	35	39	586
00	588	145	149	95	99	71	75	57	61	47	51	39	43	35	39	588
00	599	140	149	97	101	71	75	57	61	41	51	41	40	35	39	599
Ø	594	147	151	97	101	73	77	57	61	47	51	41	45	35	39	594
00	596	147	151	97	101	73	77	57	61	47	51	41	45	35	39	596
Ø	598	147	151	97	101	73	77	57	61	47	_51	41	45	35	39	598
00	600	147	151	97	101	73	77	57	61	47	51	41	45	35	39	600

	MULTIPLE-CIRCUIT, DOUBLE WINDINGS, FOR DRUM ARMATURES.															
2	ORS				FF	RONT	AND	BAC	K PI	TCHE	ES				1	TORS
RANC	DUCT	4 6		6	8	8	10		12		1	4	16		DUCI	
CON		POLES		POLES		POLES		POLES		POLES		POLES		POLES		CON
R	No.OF	F	В	F	В	F	В	F	В	F	В	F	В	F	В	No. OF
Q	_602	149	153	99	103	73	77	59	63	49	53	41	45	35	39	602
00	604	149	153	99	103	73	77	59	63	49	53	41	45	35	39	604
00	608	$149 \\ 149$	153 153	99	103	73	77	59	63	49	53	41	45	35	39	608
Ø	610	151	155	99	103	75	79	59	63	49	53	41	45	_37		610
00	612	151	155	99	103	75	79	59	63	49	53	. 41	45	37	41	612
00	616	151	155	101	105	75	79	59	63	49	<u> </u>	41	45	37	41	614
Q	618	153	157	101	105	75	79	59	63	49	53	43	47	37	41	618
00	620	153	157	101	105	75	79	59	63	49	53	43	47	37	41	620
0	622	153	157	101	105	75	79	61	65	49	53	43	47	37	41	622
00	626	155	157 159	101	105	77	81	61	65	<u>49</u> 51	55	43	47	37	41	626
00	628	155	159	103	107	77	81	61	65	51	55	43	47	37	41	628
Ø	630	155	159	103	107	77	81	61	65	51	55	43	47	37	41	630
00	632	155	159	103	107	77	81	61	65	51	55	43	47	37	41	632
00	636	157	161	103	107	77	81	61	65	51	55	43	47	37	41	636
Q	638	157	161	$105 \\ 105$	109	77	81	61	65	51	55	43	47	37	41	638
00	640	157	161	105	109	77	81	61	65	51	55	43	47	37	41	640
Q	642	159	163	105	109	79	83	63	67	51	55	43	47	39	43	642
00	644	159	163	105	109	79	83	$\frac{63}{62}$	67	51	55	43	47	39	43	644
00	648	$159 \\ 159$	$103 \\ 163$	105	109	79	83	63	67	51	55	40	49	39	43	648
Ø	650	161	165	107	111	79	83	63	67	53	57	45	49	39	43	650
00	652	161	165	107	111	79	83	63	67	53	57	45	49	39	43	652
00	654	161	165	107	111	79	83	63	67	53	57	45	49	39	43	654
00	658	161	167	107	111	<u>79</u> 81	83	63	67	53	57	45	49	39	43	656
00	660	163	167	107	111	81	85	63	67	53	57	45	49	39	43	660
00	662	163	167	109	113	81	85	65	69	53	57	45	49	39	43	662
00	664	163	167	109	113	81	85	65	69	53	57	45	49	39	43	664
Ø	666	$165 \\ 165$	169	109	113	81	85	65	69	53	57	45	49	39	43	666
00	670	165	169	109	113	81	85	65	69	53	57	45	49	39	43	670
.00	672	165	169	109	113	81	85	65	69	53	57	45	49	39	43	672
Ø	674	167	171	111	115	83	_ 87	_65	69	55	_59_	47	51	41	45	674
00	676	167	171	111	115	83	87	65	69	55	59	47	51	41	45	676
0.0	680	167	171	111	115	83	87	65	<u>69</u> 69	55	59	47	51	41	45	678
00	682	169	173	111	115	83	87	67	71	55	59	47	51	41	45	682
00	684	169	173	111	115	83	87	67	71	55	59	47	51	41	45	684
0	686	169	173	113	117	83	87	67	71	55	59	47	51	41	45	686
00	688	169	173	113	117	83	87	67	71	55	59	47		41	45	688
00	192	171	175	113	117	85	89	67	71	55	59	47	51	41	40	690
Q	694	171	175	113	117	85	89	67	71	55	59	47	51	41	45	694
00	696	171	175	113	117	85	89	67	71	55	59	47	51	41	45	696
(0)	698	173	177	115	119	85	- 89	67	71	57	61	47	51	41	45	698
00	100	110	111	110	113	00	03	01	11	01	101	41	10	41	40	100



	MULTIPLE-CIRCUIT, DOUBLE WINDINGS, FOR DRUM ARMATURES.															
>	rors				FI	RONT	ANI	D BAG	CK PI	тсні	ES			111		ORS
RANC	RANC		4		6		8		_ 10		12		14		16	
ENT	F CON	POLES		POLES		POLES		POLES		POLES		POLES		POLES		F CON
R	No.0	F	В	F	В	F	В	F	В	F	В	F	В	F	B	No.0
0	702	173	177	115	119	85	89	<u>69</u>	73	57	61	49	53 53	41	45	702
0	706	175	179	115	119	87	91	69	73	_57	61	49	53	43	47	706
00	708	175	179	115	119	87	91	69	73	57	61	49	53	43	47	708
0	710	175 175	179	117	121	87	91	69	73	57	61	49	53	43	47	710
Q	714	177	181	117	121 121	87	91	69	73	57	61	49	53	43	47	714
00	716	177	181	117	121	87	91	69	73	57	61	49	53	43	47	716
Ø	718	177	181	117	121	87	91	69	73	57	61	49	53	43	47	718
00	720	177	181	117	121	87	91	69	73	57	61	49	53	43	47	720
00	724	179	183	119	123	89	93	71	75	59	63	49	53	43	47	724
Ø	726	179	183	119	123	89	93	71	75	59	63	49	53	43	47	726
00	728	179	183	119	123	89	93	71	75	59	63	49	53	43	47	728
0	730	181	185	119	123	89	93	71	75	59	63	51	55	43	47	730
00	734	181	185	119	125	89	93	71	75	59	63	51	55	43	47	732
00	736	181	185	121	125	89	93	71	75	59	63	51	55	43	47	736
Ø	738	183	_187_	121	125	91	95	71	75	59	_63	_ 51	55	45	49	738
00	740	183	187	121	125	91	95	71	75	59	63	51	55	45	49	740
00	742	183	187	121	125	91	95	73	77	59	63	51	55	45	49	742
Ø	746	185	189	121	127	91	95	73	77	61	65	51	55	$\frac{45}{45}$	49	746
00	748	185	189	123	127	91	95	73	77	61	65	51	55	45	49	748
Ø	750	185	_189	123	127	91	95	73	77	61	65	51	55_	45	49	750
00	752	185	189	123	127	91	95	73	77	61	65	51	55	45	49	752
00	756	$\frac{107}{187}$	191	$\frac{123}{123}$	127	93	97	73	77	61	<u> </u>	$\frac{-51}{51}$	$\frac{55}{55}$	45	49	756
Ø	758	187	191	125	129	93	97	73	77	61	65	53	57	45	49	758
00	760	187	191	125	129	93	97	73	77	61	65	53	57	45	49	760
Ø	762	189	193	125	129	93	97	75	79	61	65	53	57	45	49	762
00	766	189	193	$125 \\ 125$	129	93	97	75	79	61	65	<u> </u>	57	45	49	764
00	768	189	193	125	129	93	97	75	79	61	65	53	57	45	49	768
Ø	770	191	195	127	131	95	99	75	79	63	67	53	57	47	51	770
00	772	191	195	127	131	95	99	75	79	63	67	53_	57	47	51	772
00	776	191	195	127	131	95	99	75	79	63	67	53	<u> </u>	47	51	776
Q	778	193	197	127	131	95	99	75	79	63	67	53	57	47	51	778
00	780	193	197	127	131	95	99	75	79	63	67	53	57	47	51	780
0	782	193	197	129	133	95	99	77	81	63	67	53	57	47	51	782
00	786	193	197	129	133	95	99	77	81	63	67	55	50	47	51	784
00	788	195	199	129	133	97	101	77	81	63	67	55	59	47	51	788
Ø	790	195	199	129	133	97	101	77	81	63	67	55	59	47	51	790
00	792	195	199	129	133	97	101	77	81	63	67	55	59	47	51	792
0	794	197	201	131	135	97	101	77	81	65	69	55	59	47	51	794
0	798	197	201	131	135	97	101	77	81	65	69	55	59	47	51	796
00	800	197	201	131	135	97	101	77	81	65	69	55	59	47	51	800
ſ	MUL	TIPL	E-CI	RCU	IT, E	OUE	BLE	WINI	DINC	S, F	ORE	DRUN	A AR	MAT	URE	ES.
----------	--------	---	-------------------	------------	-------------------	--------------	--------------	------	------	------	-----------------	--------	------	------------	-----------------	--------
×	ORS	FRONT AND BACK PITCHES46810121416POLESPOLESPOLESPOLESPOLESPOLES														
RANC	DUCT	4	4		6	8	3	1	0	1	2	1	4	1	6	Lond
ENTP	CONI	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	CON
RE	10. OF	F	В	F	В	F	В	F	В	F	В	F	В	F	В	40, OF
0	802	199	203	131	135	99	103	79	83	65	69	55	59	49	53	802
00	804	199 203 131 135 99 103 79 83 65 69 55 59 49 53 802 199 203 131 135 99 103 79 83 65 69 55 59 49 53 802 199 203 131 135 99 103 79 83 65 69 55 59 49 53 802 199 203 133 137 99 103 79 83 65 69 55 59 49 53 802													804	
00	808	199 203 133 137 99 103 79 83 65 69 55 59 49 53 80 199 203 133 137 99 103 79 83 65 69 55 59 49 53 80 199 203 133 137 99 103 79 83 65 69 55 59 49 53 80													808	
Q	810_	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														810
00	812	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														812
00	814	$\begin{array}{cccccccccccccccccccccccccccccccccccc$														816
Ø	818	203	207	135	139	101	105	79	83	67	71	57	61	49	53	818
00	820	203	207	135	139	101	105	79	83	67	71	57	61	49	53	820
0	822	203	$\frac{207}{207}$	135	139	101	$105 \\ 105$	81	85	67	$\frac{71}{71}$	57	61	49	53	822
Ø	826	$\frac{205}{205}$	209	135	139	101	105	81	85	67	71	57	61	49	$\frac{53}{53}$	826
00	828	_205	209	135	139	101	105	81	85	67	71	57_	61	49	53	828
0	830	205	209	137	141	101	105	81	85	67	71	57	61	49	53	830
00	834	205	209	137	141	$101 \\ 103$	105	81	85	67	71	57	61	49	55	832
00	836	207	211	137	141	103	107	81	85	67	71	57	61	51	55	836
Q	838	207	211	137	141	103	107	81	85	67	71	57	61	51	55	838
00	840	207	211	137	141	103	107	81	85	67	71	57	61	51	55	840
<u>@</u>	842	209	$\frac{213}{913}$	139	$\frac{143}{143}$	103	107	83	87	69	73	59	63	51	55	842
Q	846	209	213	139	143	103	107	83	87	69	73	59	63	51	55	846
00	848	209_	213	139	143_	103	107	83	87	69	73	_ 59 _	63	.51	55	848
©_	850	211	215		143	105	109	83	87	69	73	59	63	51	55	850
00	854	211	215 915	139	143	105	109	83	87	69	73	59	63	51	55	852
00	856	211	215	141	145	105	109	83	87	69	73	59	63	51	55	856
Ø	858	213	217	141	145	105	109	83	87	69	73	59	63	51	55	858
00	860	213	217	141	145	105	109	83		69	73	59	63	51	55	860
00	864	213	217	141	140	100	109	80	89	60	73	59	63	51.	_55	802
Ø	866	$\frac{215}{215}$	219	141	147	107	111	85	89	71	75	59	63	53	57	866
00	868	215	219	143	147	107	111	85	89	71	75	_59	63	53	57	868
Ø	870	$\frac{215}{215}$	219	143	147	107	111	85	89	71	75	61	65	53	57	870
00	872	$\frac{215}{917}$	$\frac{219}{221}$	143 143	147	107	111	85	89	71	75	61	65	<u></u> 53	57	872
00	876	217	221	143	147	107	111	85	89	71	75	61	65	53	57	876
Ø.	878	217	221	145	149	107	111	85	89	71	75	61	65	53	57	878
00	880	217	221	145	149	107	111	85	89	71	75_	61	65	53	57	880
00	884	219	223	145	149	109	113	87	91	71	75	61	65	53	57	884
0	_886_	219	223	145	149	109	113	87	91	71	75	61	65	53	57	886
00	888	219	223	145	149	109	113	87_	91		_75_	61	65	_53_	57	888
Q	_890	221	225	147	151	109	113	87	91	73	77	61	65	53	57	890
00	892	221	225	147	151	109	113	87	91	73	77	61	65	53	57	892
00	896	221	225	147	151	109	113	87	91	73	77	61	65	53	57	896
Ø	898	223	227	147	151	111	115	87	91	73	77	63	67	55	59	898
00	900	223	227	147	151	111	115	87	91	73	77	63	67	55	59	900

Above choice of Pitches will prove most satisfactory, although, as stated in text, the absolute

magnitude of average pitch may be varied within reasonable limits.

I	MUL	TIPL	E-CI	RCU	IT, E	OUE	BLE '	WINI	DINC	is, f	ORI	DRUN	M AR	MAT	URE	ES.
>	ORS	FRONT AND BACK PITCHES46810121416POLESPOLESPOLESPOLESPOLESPOLESPOLES														
RANC	DUCT	-	4		3	8	3	1	0	1	2	1	4	1	6	DUCT
ENT	F CON	PO	LES	PO	LES	PO.	LES	PO	LES	PO	LES	PO	LES	PO	LES	F CON
ě.	No. 0	F B F B <td>Ño, 0</td>											Ño, 0			
00	902	223	227	149	153	111	115	89	93	73	77	63	67	55	59	902
Ø	906	225	229	149	153	111	115	89	93	73	77	63	67	55	59	906
00	908	225	229	149	153	111	115	89	93	73	77	63	67	55	59	908
00	910	225	229	149	153	111	115	89	93	73	77	63	67	55	59	910
Ø	914	227	231	151	155	113	117	89	93	75	79	63	67	55	59	914
00	916	227	231	151	155	113	117	89	93	75	79	63	67	55	59	916
00	918	227	$\frac{231}{231}$	151	155	113	117	89	93	75	79	63	67	55	59	918
0	922	229	233	151	155	113	117	91	95	75	79	63	67	55	59	922
00	924	229	233	151	155	113	117	91	95	75	79	63	67	55	59	924
00	928	229	233	153	157	113	117	91	95	75	79	65	69	55	59	928
Ø	930	231	235	153	157	115	119	91	95	75	79	65	69	57	61	930
00	932	231	235	153	157	115	119	91	95	75	79	65	69	57	61	932
00	936	231	235	153	157	115	119	91	95	75	79	65	69	57	61	936
Ø	938	233	237	155	159	115	119	91	95	77	81	65	69	57	61	938
00	940	233	237	155	159	115	119	91	95	77	81	65	69	57	61	940
00	942	233	237	$155 \\ 155$	159	$115 \\ 115$	119	93	97	77	81	65	69	57	61	944
0	946	235	239	155	159	117	121	93	97	77	81	65	69	57	61	946
00	948	235	239	155	159	117	121	93	97	77	81	65	69	57	61	948
00	952	235	239	157	161	117	121	93	97	77	81	65	69	57	61	952
Ø	954	237	241	157	161	117	121	93	97	77	81_	67	71	57	61	954
00	956	237	241	157	161	117	121	93	97	77	81	67	71	57	61	956
00	960	237	241	157	161	117	121	93	97	77	81	67	71	57	61	960
Ø	962	239	243	159	163	119	123	95_	99	79	83	67	71	59	63	962
00	964	239	243	159	163	119	123	95	99	79	83	67	71	59_	63	964
00	968	239	243	159	163	119	$123 \\ 123$	95	99	79	83	67	71	59	63	968
Q	970	241	245	159	163	119	123	95	99	79	83	67_	71	59	63	.970
00	972	241	245	159	163	119	123	95	99	79	83	67	71	59	63	972
00	976	241	245	161	165	119	123 123	95	99	79	83	67	71	59	63	974
Ø	978	243	247	161	165	121	125	95	99	79	83	67	71	59	63	978_
00	980	243	247	161	165	121	125	95	99	79	83	67	71	59	63	980
00	984	243	247	161	165	121	125	97	101	79	83	69	73	59	63	982
Ø	986	245	249	163	167	121	125	97	101	81	85	69	73	59	63	986
00	988	245	249	163	167	121	125	97	101	81	85	69	73	59	63	988
00	992	245	249	163	167	121	125	97	101	81	85	69	73	59	63	990
0	994	247	251	163	167	123	127	97	101	81	85	69	73	_61	65	994
00	996	247	251	163	167	123	127	97	101	81	85	<u>69</u>	73	61	65	996
00	1000	247	251	165	169	123	127	97	101	81	85	69	73	61	65	1000

P	MULT	FIPL	E-CI	RCU	IT, D	OUE	LE V	VINE	DING	S, F	ORE	RUN	A AR	МАТ	URE	s.
>	rors	FRONT AND BACK PITCHES46810121416PolesPolesPolesPolesPolesPoles														
ANC	DUCI		4		6		8	1	0	1	.2	1	4	1	.6	DUCT
ENTE	CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	CON
В	No. OF	F B S G G														No. OF
Ø	1002	F B F													1002	
00	1004	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														1004
00	1008	$\begin{array}{ c c c c c c c c c c c c c c c c c c c$														1006
Ø	1010	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														1010
00	1012	$\begin{array}{ c c c c c c c c c c c c c c c c c c c$														1012
0	1014	251 255 167 171 125 129 99 103 83 87 71 75 61 65 1014 251 255 167 171 125 129 99 103 83 87 71 75 61 65 1014 251 255 167 171 125 129 99 103 83 87 71 75 61 65 1016														1014
00	1018	251 255 167 171 125 129 99 103 83 87 71 75 61 65 1016 253 257 167 171 125 129 99 103 83 87 71 75 61 65 1016 253 257 167 171 125 129 99 103 83 87 71 75 61 65 1018 050 257 167 171 125 129 99 103 83 87 71 75 61 65 1018														1016
00	1020	$\begin{array}{ c c c c c c c c c c c c c c c c c c c$														
Ø	1022	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														
00	1024 1096	253	$\frac{257}{250}$	169	173	125	129	$101 \\ 101$	105	83	87	71	75	61	65	1024
00	1020	255	259	169	173	$\frac{127}{127}$	131 131	101	105 105	83	87	71	75	63	67	1020
0	1030	255	259	169	173	127	131	101	105	83	87	71	75	63	67	1020
00	1032	255	259	169	173	127	131	101	105	83	87	71	75	63	67	1032
Ø	1034	257	261	171	175	127	131	101	105	85	89	71	75	63	67	1034
00	1036	257	261	171	175	127	131	$101 \\ 101$	$105 \\ 105$	85	89	71	75	63	67	1036
00	1040	257	261	171	175	127	131	101	105	85	89	10	77	63	67	1038
0	1042	259	263	171	175	129	133	103	107	85	89	73	77	63	67	1042
00	1044	259	263	171	175	129	133	103	107	85	89	73	77	63	67	1044
0	1046	259	$\frac{263}{263}$	173	177	129	133	103	107	85	89	73	77	63	67	1046
00	1040	209	265	173	177	129	133	103	107	85	89	73	77	63	67	1048
00	1050	261	265	173	177	129	133	103	107	85	89	73	77	63	67	1050
Q	1054	261	265	173	177	129	133	103	107	85	89	73	77	63	67	1054
00	1056	261	265	173	177	129	133	103	107	85	89	73	77	63	67	1056
CO CO	1058	263	267	175	179	131	135	103	107	87	91	73	77	65	69	1058
00	1060	$\frac{263}{263}$	$\frac{207}{267}$	$170 \\ 175$	179	131	135	105	107	87	91	73	77	65	69	1060
00	1064	263	267	175	179	131	135	105	109	87	91	73	77	65	69	1064
Ø	1066	265	269	175	179_	131	_135_	105	109	87	91	75	79	65	69	1066
00	1068	265	269	175	179	131	135	105	109	87	91	75	79	65	69	1068
00	1070	200	269	177	181	131	135	105	109	87	91	75	79	65	69	1070
Q	1074	267	271	177	181	131	$\frac{135}{137}$	105	109	87	91	75	79	65	69	1072
00	1076	267	271	177	181	133	137	105	109	87	91	75	79	65	69	1076
Ø	1078	267	271	177	181	133	137	105	109	87	91	75	79	65	69	1078
00	1080	267	271	177	181	133	137	105	109	87	$\frac{91}{02}$	75	79	65	69	1080
00	1084	269	273	179	183	133	137	107	111	89	93	75	79	65	69	1082
Ø	1086	269	273	179	183	133	137	107	111	89	93	75	79	65	69	1086
00	1088	269	273	179	183_	_133	137	107	111	89	93	75	_ 79	65	69	1088
0	1090	271	275	179	183	135	139	107	111	89	93	_75	79	67	71	1090
00	1092	271	275	179	183	135	139	107	111	89	93	75	79	67	71	1092
00	1096	271	275	181	185	135	139	107	111	89	93	77	81	67	71	1094
0	1098	273	277	181	185	135	139	107	111	89	93	77	81	67	71	1098
00	1100	273	277	181	185	135	139	107	111	89	93	77	81	67	71	1100

Above choice of Pitches will prove most satisfactory, although, as stated in text, the absolute

magnitude of average pitch may be varied within reasonable limits.

	MUL	TIPL	E-C	IRCL	лт, і	DOU	BLE	WIN	DING	GS, F	OR	DRU	MAF	RMAT	U RI	ES.
	ORS	FRONT AND BACK PITCHES46810121416POLESPOLESPOLESPOLESPOLESPOLESPOLES														rors
NTRANCY	CONDUCT	Po	4 LES	Po	3 LES	POI	3 LES	1 P0	0 LES	1 PO	2 LES	1 Po	4 LES	1 PO	6 LES	CONDUCT
RE-E	No. OF	F	В	F	B	F	В	F	В	F	В	F	В	F	В	No.OF
0	1102	273	277	181	185	135	139	109	113	89	93	77	81	67	71	1102
00	1104	273	277	181	185	135	139 141	109	113	<u>89</u> 91	93	77	81	67	71	1104
00	1108	275	279	183	187	137	141	109	113	91	95	77	81	67	71	1108
Ø	1110	275	279	183	187	137	141	_109_	113	91	95	77	81	67	71	1110
00	1112	275	279	183	187	137	141	109	113	91	95	77	81	67	71	1112
0	1114	277	281	183	187	137	141	109	113	91	95	77	81	67	71	1114
Q	1118	277	281	185	189	137	141	109	113	91	95	77	81	67	71	1118
00	1120	277	281	185	189	137	141	109	113	91	95	77_	81	67	71	1120
Q	1122	279	283	185	189	139	143	111	115	91	95	79	83	69	73	1122
00	1124	279	283	185	189	139	$143 \\ 143$	111	115	91	95	79	83	69	73	1124
00	1128	279	283	185	189	139	143	111	115	91_	95	79	83	69	73	1128
Ø	1130	281	285	187	191	139	143	111	115	93	97	79	83	69	73	1130
00	1132	281	285	187	191	139	143	111	115	93	97	79	83	69	73	1132
00	1134	281	285	187	191	139	14.3	111	115	93	97	79	83	69	73	1134
0	1130	283	287	187	191	141	145	111	115	93	97	79	83	69	73	1138
00	1140	283	287	187	191	141	145	111	115	93	97	79	83	69	73	1140
Ø	1142	283	287	189	193	141	145	113	117	93	97	79	83	69	73	1142
00	1144	283	287	189	193	141	145	113	117	93	97	79	83	69	73	1144
00	1140	285	289	189	193	141	$\frac{140}{145}$	$113 \\ 113$	117	93	97	79	83	69	73	1148
Ø	1150	285	289	189	193	141	145	113	117	93	97	81	85	69	73	1150
00	1152	285	289	189	193	141	145	113	117	93	97	81	85	69	73	1152
Ø	1154	287	291	191	195	143	147	113	117	95	99	81	85	71	75_	1154
00	1156	287	291	191	195	143	147	113	117	95	99	81	85	71	75	1150
00	1160	287	291	191	195	143	147	113	117	95	99	81	85	71	75	1160
Ø	1162	289	293	191	195	143	147	115	119	95	99	81	85	71	75	1162
00	1164	289	293	191	195	143	147	115	119	95	99	81	85_	71	75	1164
Q	1166	289	293	193	197	143	147	115	119	95	99	81	85	71	75	1166
00	1108	200	290	193	197	140	147	115	119	95	99	81	85	71	75	1170
00	1172	291	295	193	197	145	149	115	119	95	99	81	85	71	75	1172
Ø	1174	291	295	193	197	145	149	115	119	95	99	81	85	71	75	1174
00	1176	291	295	193	197	145	149	115	119	95	99	81	85	71	75	1176
	1178	293	297	195	199_	145	14.	115	119	97	101	83	87	71	75	1178
Q	1182	293	297	195	199	145	149	117	121	97	101	83	87	71	75	1182
00	1184	293	297	195	199	145	149	117	121	97	101	83	87	71	75	1184
Ø	1186	295	299	195	199	147	151	117	121	97	101	83	87	73	77	1186
00	1188	295	299	195	199	147	151	117	121	97	101	83	87	73	77	1188
00	1190	295	299	197	201	147	151	117	121	97	101	82	87	73	77	1190
Ø	1194	297	301	197	201	147	151	117	121	97	101	83	87	73	77	1194
00	1196	297	301	197	201	147	151	117	121	97	101	83	87	73	77	1196
0	1198	297	301	197	201	147	151	117	121	97	101	83	87	73	77	1198
00	1200	201	106	197	201	141	101	117	121	91	1 101	03	01	10	1 11	1200

N	NULI	IPL	E-CI	RCU	IT, D	OUB	LE W	VIND	ING	s, fc	RD	RUM	AR	MAT	JRES	3.
• >	ORS	FRONT AND BACK PITCHES 4 6 8 10 12 14 16 POLES POLES POLES POLES POLES POLES														ORS
FNTRANC	CONDUCT	PO	4 LES	Po	6 les	POI	3 LES	1 POI	0 LES	1 P0	2 LES	PO	LES	1 Po	6 LES	CONDUCT
Ш Ш Ш	No.OF	F	В	F	В	F	В	F	B	F	В	F	B	F	В	No.OF
0	1202	F B F												1202		
00	1204	299 303 199 203 149 153 119 123 99 103 83 87 73 77 19 299 303 199 203 149 153 119 123 99 103 83 87 73 77 19 299 303 199 203 149 153 119 123 99 103 83 87 73 77 19 299 303 199 203 149 153 119 123 99 103 85 89 73 77 19 209 303 199 203 149 153 119 123 99 103 85 89 73 77 19 209 303 199 203 140 152 19 103 85 89 73 77 19													1204	
00	1200 1208	4 299 303 199 203 149 153 119 123 99 103 83 87 73 77 12 3 299 303 199 203 149 153 119 123 99 103 83 87 73 77 12 3 299 303 199 203 149 153 119 123 99 103 85 89 73 77 12 3 299 303 199 203 149 153 119 123 99 103 85 89 73 77 12 3 299 303 199 203 149 153 119 123 99 103 85 89 73 77 12 0 301 305 199 203 149 153 119 123 99 103 85 89 73													1208	
Q	1210	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													1210	
00	1212	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														1212
Q	1214	301 305 199 203 149 153 119 123 99 103 85 89 73 77 121 301 305 201 205 149 153 119 123 99 103 85 89 73 77 121 301 305 201 205 149 153 119 123 99 103 85 89 73 77 121 301 305 201 205 149 153 119 123 99 103 85 89 73 77 121 301 305 201 205 149 153 119 123 99 103 85 89 73 77 121													1214	
00	1216	301 305 201 205 149 153 119 123 99 103 85 89 73 77 121 301 305 201 205 149 153 119 123 99 103 85 89 73 77 121 303 307 201 205 151 155 119 123 99 103 85 89 73 77 121 303 307 201 205 151 155 119 123 99 103 85 89 75 79 121														1216
00	1218	301 305 201 205 149 153 119 123 99 103 85 89 73 77 123 303 307 201 205 151 155 119 123 99 103 85 89 73 77 123 303 307 201 205 151 155 119 123 99 103 85 89 75 79 123 303 307 201 205 151 155 119 123 99 103 85 89 75 79 123 303 307 201 205 151 155 119 123 99 103 85 89 75 79 123														1218
Ø	1222	303 307 201 205 151 155 119 123 99 103 85 89 75 79 121 303 307 201 205 151 155 119 123 99 103 85 89 75 79 122 303 307 201 205 151 155 119 123 99 103 85 89 75 79 122 303 307 201 205 151 155 121 125 99 103 85 89 75 79 122 303 307 201 205 151 155 121 125 99 103 85 89 75 79 122														1220
00	1224	303	307	201	205	_151	155	121	125	99	103	85	89	_75	79	1224
0_	1226	305	309	203	207	151	155	121_	125	101	105	85	89	75	7.9	1226
00	1228	305	309	203	207	151	155	101	125	101	105	85	89	75	79	1228
.00	1230	305	309	203	207	<u>101</u> 151	155	121	120	101	105	85	89	75	79	1230
0	1234	307	311	203	207	153	157	121	125	101	105	87	91	75	79	1234
00	1236	307	311	203	207	153	157	121	125	101	105	87	91	75	79	1236
Q	1238	307	311	205	209	153	157	121	125	101	105	87	91	75	79	1238
00	1240	307	311	205	209	153	157	121	125	101	105	87	91	75	79	1240
0	1242	309	313	205	209	153	157	123	127	101	105	87	91	75	79	1242
00	1244	309	313	205	209	153	157	120	121	101	105	87	91	75	79	1244
00	1248	309	313	205	209	153	157	123	127	101	105	87	91	75	79	1248
Q	1250	311	315	207	211	155	_159_	123	127	103	107	87	91	77	81	1250
00	1252	311	315	207	211	155	159	123	127	103	107	87	91	77	81	1252
<u></u>	1254	211	315	207	211	155	159	123	127	103	107	87	91	77	81	1254
00	$\frac{1250}{1958}$	313	$\frac{310}{317}$	207	$\frac{211}{211}$	$100 \\ 155$	159	123	127	103	107	87	91	77	81	1250
00	1260	313	317	207	211	155	159	123	127	103	107	87	91	77	81	1260
Q	1262	313	317	209	213	155	159	125	129	103	107	89	93	77	81	1262
00	1264	313	317	209	213	155	159	125	129	103	107	89	93	77	81	1264
Q	1266	$\frac{315}{215}$	319	209	213	157	161	125	129	103	107	89	93	77	81	1266
00	1208 1270	$\frac{-515}{-315}$	$\frac{319}{319}$	209	$\frac{215}{213}$	157	161	120	129	103	107	89	93	177	81	1208
00	1272	315	319	209	213	157	161	125	129	103	107	89	93	77	81	1272
Ø	1274	317	321	211	215	157	161	125	129	105	109	89	93	77	81	1274
00	1276	317	321	211	215	157	161	125	129	_105_	109	89	93	77	81	1276
Q	1278	317	321	211	215	157	161	125	129	105	109	89	93	77	81	1278
00	1280	317	321	911	215 915	157	162	125	129	105	109	89	93	70	81	1280
00	1284	319	323	211	215	159	163	127	131	105	109	89	93	79	83	1284
Ø	1286	319	323	213	217	159	163	127	131	105	109	89	93	79	83	1286
00	1288	319	323	213	217	159	163	127	131	105	109	89	93	79	83	1288
Ø	1290	321	325	213	217	159	163	127	131	105	109	91	95	79	83	1290
00	1292	321	325	$\frac{213}{913}$	217	159	163	127	131	105	109	91	95	79	83	1292
00	1294	321	325	213	217	159	163	127	131	105	109	91	95	79	83	1294
0	1298	323	327	215	219	161	165	127	131	107	111	91	95	79	83	1298
00	1300	323	327	215	219	161	165	127	131	107	111	91	95	79	83	1300

Above choice of Pitches will prove most satisfactory, although, as stated in text, the absolute

magnitude of average pitch may be varied within reasonable limits.

Г	NULT	FIPL	E-CI	RCU	IT, D	OUB	LEV	VINE	DING	S, F(DR D	RUM	ARI	MAT	URE	S.
>	ORS	FRONT AND BACK PITCHES46810121416PolesPolesPolesPolesPolesPolesPoles														ORS
RANC	DUCT		4 6 8 10 12 14 16 POLES POLES POLES POLES POLES POLES POLES													
ENT	CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	CON
RE	No. OF	F	B	F	B	F	В	F	B	F	B	F	В	F	B	No. OF
0	1302	323	327	_215	219	161	165	129	133	107	111	91	95	79	83	1302
00	1304	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$												83	1304	
00	1306	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$												79	83	1306
0	1310	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													1308	
00	1312	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														1312
Q	1314	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														1314
00	1316	$ \begin{smallmatrix} 1 & 1 & 2 & 2 & 1 & 2 & 2 & 1 & 1 & 1 & 1 & 1 & 3 & 3 & 3 & 3 & 1 \\ 5 & 3 & 2 & 7 & 3 & 3 & 1 & 2 & 1 & 1 & 3 & 1 & 1 & 3 & 3 & 3 & 3 & 1 \\ 5 & 3 & 2 & 7 & 3 & 3 & 1 & 2 & 1 & 1 & 3 & 1 & 1 & 3 & 3 & 3 & 3 & 3 \\ 5 & 3 & 3 & 2 & 7 & 3 & 3 & 1 & 2 & 1 & 1 & 3 & 1 & 1 & 3 & 3 & 3 & 3 & 1 \\ 5 & 3 & 3 & 1 & 1 & 1 & 3 & 3 & 1 & 1 & 1 & 3 & 3 & 3 & 1 & 3 \\ 5 & 3 & 3 & 1 & 1 & 1 & 3 & 3 & 1 & 1 & 1 & 3 & 3 & 3 & 1 & 3 & 3 & 1 \\ 5 & 5 & 1 & 5 & 1 & 5 & 5 & 1 & 5 & 1 & 5 & 5 & 1 & 5 \\ 5 & 3 & 3 & 1 & 1 & 1 & 3 & 3 & 1 & 1 & 1 & 3 & 3 & 3 & 1 & 1 & 1 & 3 & 3 & 3 & 1 \\ 5 & 5 & 5 & 1 & 5 & 5 & 1 & 5 & 5 & 1 & 5 \\ 5 & 5$														1316
00	1318	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														1318
0	1322	329	333	219	223	163	167	131	135	109	113	93	97	81	85	1320
00	1324	329	333	219	223	163	167	131	135	109	113	93	97	81	85	1324
0	1326	329	333	219	223	163	167	131	135	109	113	93	97	81	85	1326
00	1328	329	333	219	223	163	167	131	135	109	113	93	97	81	85	1328
00	1332	331	335	219	223	165	169	131	135	109	113	93	97	81	85	1330
Ø	1334	331	335	221	225	165	169	131	135	109	113	93	97	81	85	1334
00	1336	331	335	221	225	165	169	131	135	109	113	93	97	81	85	1336
Ø	1338	333	337	221	225	165	169	131	135	109	113	93	97	81	85	1338
00	1340	333	337	221	225	165	169	131	135	109	113	93	97	81	85_	1340
00	1342	333	337	991	225	165	169	133	137	109	113	93	97	81	80	1342
Ø	1346	335	339	223	227	167	171	133	137	111	115	95	99	83	87	1346
00	1348	335	339	223	227	167	171	133	137	111_	_115_	95	99	83	87	1348
Ø	1350	335	339	223	227	167	171	133	137	111	115	95_	99	83	87	1350
00	1352	335	339	223	227	167	171	133	137	111	115	95	99	83	87	1352
00	1304	337	341	223	227	167	171	133	137	111	115	95	99	83	87	1354
Ø	1358	337	341	225	229	167	171	133	137	111	115	95	99	83	87	1300
00	1360	337	341	225	229	167	171	133	137	111	115	95	99	83	87	1360
0	1362	339	343	225	229	169	173	135	139	111	115	95	99	83	87	1362
00	1364	339	343	225	229	169	173	135	139	111	_115_	95	_99	83	87	1364
00	1368	339	343	225	229	169	173	135	139	111	115	95	99	83	87	1366
Ø	1370	341	345	227	231	169	173	135	139	113	117	95	90	83	87	1308
00	1372	341	345	227	231	169	173	135	139	113	117	95	99	83	87	1372
Ø	_1374	341	345	227	231	169	173	135	139	113	117	97	101	83	87	1374
00	1376	341	345	227	231	169	173	135	139	113	117	97	101	83	87	1376
00	1378	343	347	227	231	171	175	135	139	113	117	97	101	85	89	1378
Q	1382	343	347	229	233	171	175	137	141	113	117	97	101	85	89	1382
00	1384	343	347	229	233	171	175	137	141	113	117	97	101	85	89	1384
Ø	1386	345	349	229	233	171	175	137	141	113	117	97	_101	85	89	1386
00	1388	345	349	229	233	171	175	137	141	113	117	97	101	85	89	1388
0	1390	345	349	229	233	171	175	137	141	113	117	97	101	85	89	1390
0	1394	347	351	229	233	171	175	137	141	113	117	97	101	85	89	1392
00	1396	347	351	231	235	173	177	137	141	115	119	97	101	85	89	1396
Ø	1398	3473512312351731771371411151199710185891394347351231235173177137141115119971018589139434735123123517317713714111511997101858913963473512312351731771371411151199710185891398												1398		
00	1400	347	351	231	235	173	177	137	141	115	119	97	101	85	89	1400

Above choice of Pitches will prove most satisfactory, although, as stated in text, the absolute

magnitude of average pitch may be varied within reasonable limits,

	MUL	TIPL	E-CI	RCU	IT, E	OUE	BLE	WIN	DINC	GS, F	ORI	DRUI	MAR	MAT	URE	ES.
>	ORS	FRONT AND BACK PITCHES46810121416POLESPOLESPOLESPOLESPOLESPOLESPOLES														rors
ANC	Lond	4 6 8 10 12 14 16 POLES POLES POLES POLES POLES POLES														DNG
ENTE	CON	PO	LES	PO	LES	Po	LES	PO	LES	PO	LES	PO	LES	PO	LES	CON
ц Ц	No. OF	F	В	F	B	F	В	F	B	F	B	F	В	F	В	No. OF
0	1402	349	353	231	235	173	177	139	143	115	119	99	103	85	89	1402
00	1404	349	353	231	230	173	177	139	143	115	119	99	103	80	89	1404
00	1408	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$												1408		
Q	1410	$\begin{array}{ c c c c c c c c c c c c c c c c c c c$													1410	
00	1412	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													1412	
00	1414	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													1414	
0	1418	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													1418	
00	1420	353	357	235	239	175	179	139	143	117	121	99	103	87	91	1420
Q	1422	353	357	235	239	175	179	141	145	117	121	99	103	87	91	1422
00	1424	353	357	235	239	175	179	141	145	117	121 191	99	103	87	91	1424
00	1420	355	359	235	239	177	181	141	140	117	121 121	99	103	87	91	1420
Ø	1430	355	359	237	241	177	181	141	145	117	121	101	105	87	91	1430
. 00	1432	355	359	237	241	177	181	141	145	117	121	101	105	87	91	1432
Ø	1434	357	361	237	241	177	181	141	145	117	121	101	105	87	91	1434
00	1436	357	$\frac{361}{261}$	237	241	177	181	141	145	$\frac{117}{117}$	121 191	101	105 105	87	91	1436
00	1400	357	361	237	241	177	181	141	145	117	121	101	105	87	91	1430
Q	1442	359	363	239	243	179	183	143	147	119	123	101	105	89	93	1442
00	1444	359	363	239	243	179	183	143	147	119	123	101	105	89	93	1444
0	1446	359	363	239	243	179	183_	143	147	119	123	101	105	89	93	1446
00	1448	309	365	239	-243 943	179	183	143	141	119	120	101	100	89	95	1440
00	1452	361	365	239	243	179	183	143	147	119	$\frac{123}{123}$	101	105	89	93	1452
0	1454	361	365	241	245	179	183	143	147	119	123	101	105	89	93	1454
00	1456	361	365	241	245	179	183	143	147	119	123	101	105	89	93	1456
0	1458	363	367	241	245	181	185	143	147	119	123	103	107	89	93	1458
00	1460 1462	363	367	241	$\frac{240}{245}$	181	185	143	147	119	123	103	107	89	93	1460 1469
00	1464	363	367	241	245	181	185	145	149	119	123	103	107	89	93	1464
Ø	1466	365	369	243	247	181	185	145	149	121	125	103	107	. 89	93	1466
00	1468	365	369	243	_247	181	185	145	149	121	125	103	107	89	93	1468
	1470	365	369	243	247	181	185	145	149	121	125	103	107	89	93	1470
Ø	1474	367	371	243	247	183	187	145	149	121 121	$120 \\ 125$	103	107	<u>89</u> 91	95	1412
00	1476	367	371	243	247	183	187	145	149	121	125	103	107	91	95	1476
Ø	1478	367	371	245	249	183	187	145	149	121	_125_	103	107	91	95	1478
00	1480	$\frac{367}{260}$	371	245	249	183	187	145	149	121	125	103	107	91	95	1480
00	1482	369	373	245	249	183	187	147	$\frac{151}{151}$	121 191	125	103	$\frac{107}{107}$	91	95	1482
Q	1486	369	373	245	249	183	187	147	151	121	125	105	109	91	95	1486
00	1488	369	373	245	249	183	187	147	151	121	125	105	109	91	95	1488
0	1490	371	375	247	251	185	189	147	151	123	127	105	109	91	95	1490
00	1492	371	375	247	251	185	189	147	151	123	127	105	109	91	95	1492
00	1496	371	375	247	251	185	189	147	151	123	127	105	109	91	95	1494
Q	1498	373	377	247	251	185	189	147	151	123	127	105	109	91	95	1498
00	1500	373	377	217	251	185	189	147	151	123	127	105	109	91	95	1500



	MUL	TIPL	E-C	IRCL	лт, і		BLE	WIN	DING	GS, F	ORI	DRU	MAF	RMAT	TUR	ES.
×	rors	FRONT AND BACK PITCHES46810121416PolesPolesPolesPolesPolesPolesPoles														LORS
RANC	DNG	4 6 8 10 12 14 16 POLES POLES POLES POLES POLES POLES													DUCI	
ENT	CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	CON
RE	No.0F	F	В	F	В	F	В	F	В	F	B	F	В	F	В	No. OF
0	1502	373	377	249	253	185	189	149	153	123	127	105	109	91	95	1502
@	1504 1506	375	379	$\begin{array}{r} 249 \\ 249 \end{array}$	$\frac{253}{253}$	185	189	$149 \\ 149$	153 153	123 123	$\frac{127}{127}$	105°	109	91	95	1504 1506
00	1508	375	379	249	253	187	191	149	153	123	127	105	109	93	97	1508
0	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													93	97	1510
0	1512 1514	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													1512	
00	1516	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													1514	
0	1518	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													1518	
00	1520	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													1520	
00	1524	379	383	251	255	189	193	151	155	125	129	107	111	93	97	1522 1524
Ø	1526	379	383	253	257	189	193	151	_155	125	129	107	111	93	97	1526
00	1528	379	383	253	257	189	193	151	155	125	129	107	111	93	97	1528
00	1530	381	385	253	257	189	193	151	155	125	129	107	111	93	97	1530
Ø	1534	381	385	253	257	189	193	151	155	$125 \\ 125$	129	107	111	93	97	1534
00	1536	381	385	253	257	189	193	151	155	125	129	107	_111	93	97	1536
Q	1538	383	387	255	259	191	195	151	155	127	131	107	111	95	99	1538
00	1540	383	387	255	259	191	195	151	155	127	131	107	111	95	99	1540
00	1544	383	387	255	259	191	195	153	157	$\frac{127}{127}$	131	109	$\frac{113}{113}$	95	99	1542
Ø	1546	385	389	255	259	191	195	153	157	127	131	109	113	95	99	1546
00	1548	385	389	255	259	191	195	153	157	127	131	109	113	95	99	1548
00	1552	385	389	257	261	191	195	153	157	127	131	109	113	95	99	1550
0	1554	387	391	257	261	191	197	153	157	127	$\frac{151}{131}$	109	110	95	99	1554
00	1556	387	391	257	261	193	197	153	157	127	131	109	113	95	99	1556
0	1558	387	391	257	261	193	197	153	157	127	131	109	113	95	99	1558
00	1569	387	391	257	261	193	197	153	157	127	131	109	113	95	99	1560
00	1564	389	393	259	263	193	197	155	159	129	133	109	113	95	99	1564
Ø	1566	389	393	259	263	193	197	155	159	129	133	109	113	95	99	1566
00	1568	389	393	259	_263	193	197	155	159	129	133	109	113	95	99	1568
00	1570	391	395	209	263	195	199	155	159	129	133	111	115	97	101	1570
0	1574	391	395	261	265	195	199	155	159	129	133	111	115	97	101	1572 1574
00	1576	391	395	261	265	195	199	155	159	129	133	111	115	97	101	1576
0	1578	393	397	261	265	195	199	155	159	129	133	111	115	97	101	1578
00	1589	393	397	261	265	195	199	155	159	129	133	111	115	97	101	1580
00	1584	393	397	261	265	195	199	157	161	129	133	111	115	97	101	1584
Ø	1586	395	399	263	267	197	201	157	161	131	135	111	115	97	101	1586
00	1588	395	399	263	267	197	201	157	161	131	135	111	115	97	101	1588
00	1590	395	399	263	267	197	201	157	161	131	135	111	115	97	101	1590
Ø	1594	397	401	263	267	197	201	157	161	131	135	111	115	97	101	1592
00	1596	397	401	263	267	197	201	157	161	131	135	111	115	97	101	1596
0	1598	397	401	265	269	197	201	157	161	131	135	113	117	97	101	1598
00	1000	391	401	265	269	197	201	157	161	131	135	113	117	97	101	1600

WINDING TABLES FOR MULTIPLE-CIRCUIT, TRIPLE WINDINGS FOR DRUM ARMATURES.



-	MUL	MULTIPLE-CIRCUIT, TRIPLE WINDINGS, FOR DRUM ARMATURES. FRONT AND BACK PITCHES We be a be														
~	ORS	FRONT AND BACK PITCHES FRONT AND BACK PITCHES 4 6 8 10 12 14 16														rors
ANC	DUCT	4 6 8 10 12 14 16													DUCI	
ENTE	CONI	PO	LES	PO	LES	POI	LES	PO	LES	PO	LES	POI	LES	PO	LES	CON
RE	40.0F	POLESPOLESPOLESPOLESPOLESPOLESPFBFBFBFBFBF												F	B	No. 01
Q	202	47	53	31	37	23	29	17	23	13	19	11	17	9	15	202
000	$\frac{204}{206}$	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													204	
Q	208	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													208	
000	210	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														210
	$\frac{212}{214}$	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														214
000	216	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														216
00	218	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$														218 220
000	$\frac{220}{222}$	53	59	33	39	25	31	19	25	15	21	13	19	11	17	222
œ	224	53	59	35	41	25	31	19	25	15	21	13	19	11	17	224
000	226	53	<u> </u>	35	41	$\frac{25}{25}$	31	19	$\frac{25}{25}$	15	21	13	19	11	17	$\frac{226}{228}$
œ	230	55	61	35	41	25	31	19	25	17	23	13	19	11	17	230
Q	232	55	61	35	41	25	31	21	27	17	23	13	19	11	17	232
000	234	55	61	30	41	27	33	21	27	17	23	13	19	11	17	234
œ	238	57	63	37	43	27	33	21	27	17	23	13	19	11	17	238
000	240	57	63	37	43	27	33	21	27	17	23	15	21	11	17	240
Q	$\frac{242}{244}$	57	63	37	$\frac{43}{43}$	27	33	$\frac{21}{21}$	27	$\frac{1}{17}$	23	15	21	13	19	242
000	246	59	65	37	43	27	33	21	27	17	23	15_	21	13	19	246
600	248_	59	65	39	45	27	33	21	27	17	23	15	$\frac{21}{91}$	13	19	248
000	$\frac{250}{252}$	59	65	39	45	29	35	$\frac{21}{23}$	29	17	23	15	$\frac{21}{21}$	13	19	252
Q	254	61	67	39	45	29	35	23	29	19	25	15	21	13	19	254
000	256	61	67	39	45	29	35	23	29	19	$\frac{25}{25}$	15	$\frac{21}{21}$	13	19	256
Q	260	61	67	41	47	29	35	23	29	19	25	15	21	13	19	260
Q	262	63	69	41	47	29	35	23	29	19	25	15	21	13	19	262
000	264	63	69	41	47	29	35	23	29	19	25	15	21	13	19	264
Ŵ	268	63	69	41	47	31	37	23	29	19	25	17	23	13	19	268
000	270	65	71	41	47	31	37	23	29	19	25	17	23	13	19	270
	272	65	71	43	49	31	37	$\frac{25}{25}$	31	19	25	$\frac{17}{17}$	$\frac{23}{23}$	13	21	272
000	276	65	71	43	49	31	37	25	31	19	25	17	23	15	21	276
00	278	67	73	43	49	31	37	25	31	21	27	17	23	15	21	278
000	280	67	73	43	49	$\frac{31}{33}$	37	25	31131131131131131131113111111	$\frac{21}{21}$	21	17	$\frac{23}{23}$	15	$\frac{21}{21}$	280
œ	284	67	73	45	51	33	39	25_	31	21	27	17	23	15	21	284
00	286	69	75	45	51	33	39	25	31	21	27	17	23	15	21	286
Q	288	69	75	45	51	33	39	25	31	21	27	17	$\frac{23}{23}$	15	21	290
Q	292	69	75	45	_51	33	39	27	33	21	27	17	23	15	21	292
000	294	71	77	45	51	33	39	27	33	21	27	17	23	15	21	294
00	296	71	77	47	53	35	41	27	33	21	27	19	$\frac{25}{25}$	15	21	296
000	300	71	77	47	53	35	41	27	33	21	27	19	25	15	21	300



	MUL	TIPL	E-C	IRCL	ЛΤ, 1	RIP	LE V	VIND	ING	S, F(DR D	RUM		MAT	URE	s.
X	ORS	FRONT AND BACK PITCHES 4 6 8 10 12 14 16 POLES POLES POLES POLES POLES POLES														ORS
ENTRANC	CONDUCT	PO	4 LES	(PO	3 LES	Po	8 LES	1 P0	0 LES	1 P0	2 LES	1 Po	4 LES	1 Poi	6 LES	CONDUCT
RE	No. OF	F	В	F	В	F	В	F	В	F	В	F	В	F	B	No.OF
Q	302	73	79	47	53	_35	41	27	33	23	29	19	25	15	21	302
œ	304	73	79	47	53	35	41	27	33	23	29	19	25	15	21	304
600	306	73	79	47	55	35	41	27	33	23	29	19	25	17	23	306
Q	310	73 79 47 53 35 41 27 33 23 29 19 25 17 23 30 73 79 49 55 35 41 27 33 23 29 19 25 17 23 30 73 79 49 55 35 41 27 33 23 29 19 25 17 23 30 75 81 49 55 35 41 27 33 23 29 19 25 17 23 30 75 81 49 55 35 41 27 33 23 29 19 25 17 23 31													310	
000	312	15 15 15 15 11 11 12 15 16 17 17 18 17 17 17 17 17 17 17 17 17 17 17 17 17 17 18 17 18 17 17 18 11 17 18 18 17 18 11 17 18 18 17 18 11 17 18 11 17 18 11 17 18 11 17 18 11 17 18 11<													312	
00	314	75	81	49	55	37	43	29	35	23	29	19	25	17	23	314
000	316	75	81	49	55	37	43	29	35	23	29	19	25	17	23	316
Q	320	77	83	51	57	37	43	29	35	$\frac{20}{23}$	29	19	25	17	23	$\frac{-316}{320}$
œ	322	77	83	51	57	37	43	29	35	23	29	19	25	17	23	322
000	324	77	83	51	57	37	43	29	35	23	29	21	27	_17	23	324
600	326	79	85	51	57	37	43	29	35	25	31	21	27	17	23	326
000	330	79	85	51 - 51	57	39	43	29	35	25	31	-21	21	17	23	328
Q	332	79	85	53	59	39	45	31	37	25	31	21	27	17	23	332
Q	334	81	87	53	59	39	45	31	37	25	31	21	27	17	23	334
000	336	81	87	53	59	39	45	31	37	25	31	21	27	17	23	336
	338	<u>81</u> 91	87	53	59	39	40	31	37	25	31	$\frac{21}{91}$	27	19	25	338
000	342	83	89	53	59	39	45	31	37	25	31	<u>21</u> 91	21	19	20	349
Q	344	83	89	55	61	39	45	31	37	25	31	21	27	19	25	344
Q	346	83	89	55	61	41	47	31	37	25	31	21	27	19	25	346
000	348	83	<u>89</u> 91	55	61	41	47	31	37	25	31	$\frac{21}{91}$	27	19	25	$\frac{348}{250}$
Q	352	85	91	55	61	41	47	33	39	27	33	21	21	19	25	352
000	354	85	91	55	61	41	47	33	39	27	33	23	29	19	25	354
@	356	85	91_	57	63	41	47	33	39	27	33	23	29	19	_25	356
000	358	87	93	57	63	41	47	33	39	27	33	23	29	19	25	358
600	362	87	93	57	63	41	47	33	39	27	33	23	29	19	25	360
Ŵ	364	87	93	57	63	43	49	33	39	27	33	23	29	19	25	364
000	366	89	95	57	63	43	49	33	39	27	33	23	29	19	25	366
600	368	89	95	59	65	43	49	33	39	27	33	23	29	19	25	368
000	370	89	95	59	65	43	49	33	39	27	33	23	29	21	27	370
Q	374	91	97	59	65	43	49	35	41	29	35	20	29	91	21	374
Q	376	91	97	59	65	43	49	35	41	29	35	23	29	21	27	376
000	378	91	97	59	65	45	51	35	41	29	35	23	29	21	27	378
000	380	91	97	61	67	45	51	35	41	29	35	25	31	21	27	380
000	384	93	99	61	67	40	51	35	41	29	35	- 25	31	21	27	382
Q	386	93	99	61	67	45	51	35	41	29	35	25	31	21	27	386
æ	388	93	99	61	67	45	51	35	41	29	35	25	31	21	27	388
000	390	95	101	61	67	45	51	35	41	_29	35	25	31	21	27	390
60	392	95	101	63	69	45	51	37	43	29	35	25	31	21	27	392
000	396	95	101	63	69	47	53	37	43	29	35	25	31	21	27	394
Q	398	97	103	63	69	47	53	37	43	31	37	$-\frac{25}{25}$	31	21	27	398
QQ	400	97	103	63	69	47	53	37	43	31	37	25	31	21	27	400

.

1	MUL	TIPL	E-CI	RCU	T TI	RIP	LEW	/IND	INGS	S, FC	RD	RUM	ARM	ΛΑΤΙ	JRES	5.
X	rors	FRONT AND BACK PITCHES 4 6 8 10 12 14 16 POLES POLES POLES POLES POLES POLES														TORS
ENTRANC	CONDUCT	46810121416POLESPOLESPOLESPOLESPOLESPOLESPOLES													CONDUC	
RE	No. OF	POLES POLES POLES POLES POLES POLES POLES F B F B F B F B F B													No.0F	
000	402	F B F												402		
Q	406	$\begin{array}{ c c c c c c c c c c c c c c c c c c c$												406		
000	408	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													408	
Q	412	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													412	
000	$\frac{414}{416}$	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													414	
Q	418	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													418	
000	$\frac{420}{422}$	$101 \\ 103$	$107 \\ 109$	67	73	49	<u>55</u>	39	45	$\frac{31}{33}$	37	27	33	$\frac{23}{23}$	29	420
Q	424	103	109	67	73	49	55	39	45	33	39	27	_33	23	29	424
000	426	103	$109 \\ 109$	67	73	51	57	39	45	33	39	27	33	23	29	426
Q	430	105	111	69	75	51	57	39	45	33	39	27	33	23	29	430
000.	432	105	111	69	75	51	57	41 .	47	33	39	27	33	23	29	432
<u>(00)</u>	436	$105 \\ 105$	$\frac{111}{111}$	69	75	$\frac{51}{51}$	57	41 41	47	33	39	29	35	$\frac{25}{25}$	31	434
000	438	107	113	69	75	_51_	57	41	47	33	39	29	35	25	31	438
	440	$107 \\ 107$	113	71	77	51	57	41	47	33	39	29	35	25	31	440
000	444	107	113	71	77	53	59	41	47	33	39	29	35	25	31	444
Q	446	109	115	71	77	53	59	41	_ 47	35	41	29	35	25	31	446
000	$\frac{448}{450}$	$109 \\ 109$	$\frac{115}{115}$	$\frac{71}{71}$	77	53	<u>59</u>	41	47	35	$\frac{41}{41}$	29	$\frac{35}{35}$	$\frac{25}{25}$	$\frac{31}{31}$	448
QD	452	109	115	73	79	53	59	43	49	35	41	29	35	25	31	452
000	454	111	117	73	79	53	59	43	49	35	41	29	35	25	31	454
000	458	111	117	73	79	55	61	$\frac{43}{43}$	49	35	41	29	35	25	$\frac{31}{31}$	458
Q	460	111	117	73	79	55	61	43	49	35	41	29	35	25	31	460
000	464	113	119	73	<u>79</u> 81	55	61	43	49	35	41	29	35	25	31	462
00	466	113	119	75	81	55	61	43	49	35	41	_31	37	27	33	466
000	$\frac{468}{470}$	113	119	75	81	55	61	43	49	35	41	31	37	27	33	468
60	$\frac{470}{472}$	$115 \\ 115$	$\frac{121}{121}$	75	81	55	61	45	49 51	37	43	$\frac{31}{31}$	37	$\frac{27}{27}$	33	470
000	474	115	121	75	81	57	63	45	51	37	43	31	37	27	33	474
00	$\frac{476}{478}$	$115 \\ 117$	$\frac{121}{123}$	77	83	57	$\frac{-63}{-63}$	45	51	37	43	31	37	27	33	476
000	480	117	123	77	83	57	63	45	51	37	43	31	37	27	33	480
00	482	117	123	77	83	57	63	45	51	37	43	31	37	27	33	482
000	486	117	125	77	83	57	63	45	51	37	43	31	37	27	33	484
Q	488	119	125	79	85	_57	63	45	51	37	43	31	37	27	33	488
000	490	119	$\frac{125}{195}$	79	85	59	65	45	51		43	31	37	27	33	490
Q	494	121	120	79	85	59	65	47	53	39	45	33	39	27	33	492
Q	496	121	127	79	85	59	65	47	53	39	45	33	39	27	33	496
Q	498 500	$\frac{121}{121}$	$\frac{127}{127}$	81	87	59 59	$\frac{60}{65}$	47	53 53	39	$\frac{45}{45}$	33	39	29	35	498

	MUL	TIPL	E-CI	RCU	IT, 1	RIP	LEW	IND	INGS	6, FC	RD	RUM	ARN	ΛΑΤΙ	JRES	5.
×	ORS	FRONT AND BACK PITCHES46810121416POLESPOLESPOLESPOLESPOLESPOLES														rors
RANC	DUCI	4 6 8 10 12 14 16 POLES POLES POLES POLES POLES POLES													DUC	
ENT	CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	CON
38	No. 0F	F	В	F	В	F	В	F	В	F	В	F	В	F	В	No. OF
Q	502	123	129	81	87	59	65	47	53	39	45	33	39	29	35	502
000	506	$ \begin{array}{ c c c c c c c c c c c c c c c c c c c$													506	
- CO	508	$\begin{array}{ c c c c c c c c c c c c c c c c c c c$													508	
000	510	3 123 129 81 87 61 67 47 53 39 45 33 39 29 35 0 125 131 81 87 61 67 47 53 39 45 33 39 29 35 2 125 131 83 89 61 67 49 55 39 45 33 39 29 35													510	
œ	512	$\begin{array}{ c c c c c c c c c c c c c c c c c c c$													512	
(22)	514	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													514	
000	518	$\begin{array}{c ccccccccccccccccccccccccccccccccccc$													518	
Q	520	127	133	83	89	61	67	49	55	41	47	35	41	29	35	520
000	522	127	133	83	89	63	69	49	55	41	47	35	41	29	35	522
Q	524	127	133	85	91	63	69	49	55	41	47	35	41	29	35	524
(22)	526	129	135	85	91	63	69	49	55	41	47	35	41	29	35	526
600	530	129	135	85	91	63	69	49	55	41	47	35	41	31	37	530
Q	532	129	135	85	91	63	69	•51	57	41	47	35	41	31	37	532
000	534	131	137	85	91	63	69	51	57	41	47	35	41	31	37	534
Q	536	131	137	87	93	63	69	51	57	41	47	35	41	31	37	536
(22)	538	131	137	87	93	65	71	51	57	41	47	35	41	31	37	538
000	549	131	137	87	95	65	$\frac{1}{71}$	51	57	41	47	30	41	31	37	549
@	544	133	139	87	93	65	71	51	57	43	49	35	41	$\frac{31}{31}$	37	544
000	546	133	139	87	93	65	71	51	57	43	49	35	41	31	37	546
0	_548	133	139	89	95	65	71	51	57	43	49	37	43	31	37	548
(00)	550	135	141	89	95	65	71	51	57	43	49	37	43	31_{-1}	37	550
000	554	135	141	89	95	67	73	53	- 59	43	49	37	43	31	37	554
@	556	135	141	89	95	67	73	53	59	43	49	37	43	31	37	556
000	558	137	143	89	95	67	73	53	59	43	49	37	43	31	37	558
@	_560	137	143		97	67	73	53	59	43	49	37	43	31	37	560
(22)	562	137	143	91	97	67	73	53	59	43	49	37	43	33	39	562
000	566	139	145	91	97	67	73	53	59	43	49	37	43	33	39	566
Q	568	139	145	91	97	67	73	53	59	45	51	37	43	33	39	568
000	570	139	145	91	97	69	75	53	59	45	51	37	43	33	39	570
00	572	_139	145	93	99	69	75	55	61	45	51	37	43	33	39	572
(22)	574	141	147	93	99	69	75	55	61	45	51	37	43	33	39	574
000	578	141	147	93	99	69	75	55	61	45	51	39	40	33	39	578
Q	580	141	147	93	99	69	75	55	61	45	51	39	45	33	39	580
000	582	143	149	93	99	69	75	55	61	45	51	39	45	33	39	582
60	584	143	149	-95	101	69	75	55	61	45	51	39	45	33	39	584
000	586	143	149	95	101	71	77	55	61	45	51	39	45	33	39	586
(90)	590	145	149	95	101	71	77	00 55	61	-40	52	30	40	33	39	590
(20)	592	145	151	95	101	71	77	57	63	47	53	39	45	33	39	592
000	594	145	151	95	101	71	77	57	63	47	53	39	45	35	41	594
00	596	_145	151	97	103	71	77	57	63	_ 47	53	_39	45	35	41	596
000	600	147	153	97	103	71	77	57	63	47	53	39	45	35	41	598
	000	121	100	01	100	11	- 11	01	00	41	00	00	40	00	4	000

	MUL	TIPL	E-C	IRCU	UT, 1	RIP	LEW	VIND	ING	5, FC	R D	RUM	ARM	MAT	JRES	5.
7	TORS				FI	RONT	ANI	D BAC	CK PI	TCHI	ES					rors
TRANC	NDUCT	Do	4		6		3	1	.0	1	2	1	4	1	.6	NDÜCT
E-EN	F CO	P0.	LES	PO.	LES	PO.	LES	FU	LES	PU	LES	PO.	LES	FU	LES	PF CO
œ	No. 0	F	B	F	B	F	B	F	B	F	B	F	B	F	B	No. C
@	602	147	153	97	103	73	79	57	63	47	53	39	45	35	41	602
000	606	149	155	97	103	73	79	57	63	47	53	41	47	35	41	606
œ	608	149	155	99	105	73	79	57	63	47	53	41	47	35	41	608
@	610	149	155	99	105	73	79	57	63	47	53	41	47	35	41	610
000	614	149 151	$150 \\ 157$	99	$105 \\ 105$	73	79	59	65	49	55	41	47	35	41	614
@	616	151	157	99	105	73	79	59	65	49	55	41	47	35	41	616
000	618	151	157	99	105	75	81	59	65	49	55	41	47	35	41	618
@	620	151	157	101	107	75	81	59	65	49	55	41	47	35	41	620
000	624	153	159	101	107	75	81	59	65	49	55	41	47	35	41	624
œ	626	153	159	101	107	75	81	59	65	49	55	41	47	37	43	626
Q	628	153	159	101	107	75	81	59	65	49	55	41	47	37	43	628
000	630	155	$161 \\ 161$	101	107	75	81	<u>59</u> 61	65	49	55	41	41	37	43	630
	634	155	161	103	109	77	83	61	67	49	55	43	49	37	43	634
000	636	155	161	103	109	77	83	61	67	49	55	43	49	37	43	636
œ	638	157	163	103	109	77	83	61	67	51	57	43	49	37	43	638
@	640	157	163	103	109	77	83	61	67	51	57	43	49	37	43	640
600	642	157	163	103 105	109	77	83	61	67	<u>51</u>	57	43	49	37	43	644
Q	646	159	165	105	111	77	83	61	67	51	57	43	49	37	43	646
000	648	159	165	105	111	77	83	61	67	51	57	43	49	37	43	648
œ	650	159	165	105	111	79	85	61	67	51	57	43	49	37	43	650
(00)	654	161	165	105	111	79	85	63	69	51	57	43	49	37	43	654
QQ	656	161	167	103	111	79	85	63	69	51	57	43	49	37	43	656
Q	658	161	167	107	113	79	85	63	69	51	57	43	49	39	45	658
000	660	161	167	107	113	79	85	63	69	51	57	45	51	39	45	660
00	662	163	169	107	113	79	85	63	69	53	59	45	51	39	45	662
000	666	163	169	107 107	113	81	87	63	69	53	59	45	51	39	45	666
Q	668	163	169	109	115	81	87	63	69	53	59	45	51	39	45	668
œ	670	165	171	109	115	81	87	63	69	53	59	45	51	39	45	670
000	672	165	171	109	115	81	87	65	$\frac{71}{71}$	53	59	45	51	39	45	672
000	676	165	171	109	115	81	87	65	71	53	59	45	51	39	45	676
000	678	167	173	109	115	81	87	65	71	53	59	45	51	39	45	678
œ	680	167	173	111	117	81	87	65	71	53	59	45	_ 51	39	45	680
00	682	167	173	111	117	83	89	65	71	53	59	45	51	39	45	682
600	686	169	175	111	117	83	89	65	71	55	61	45	51	39	40	686
Q	688	169	175	111	117	83	89	65	71	55	61	47	53	39	45	688
000	690	169	175	111	117	83	89	65	71	_55	61	47	53	41	47	690
@	692	169	175	113	119	83	89	67	73	55	61	47	53	41	47	692
000	696	171	177	113	119	83	89	67	73	55	61	41	53	41	47	696
œ	698	171	177	113	119	85	91	67	73	55	61	47	53	41	47	698
œ	700	171	177	113	119	85	91	67	73	55	61	47	53	41	47	700



-

	MUL	TIPL	E-CI	IRCU	IT, 1	RIP	LEW	VIND	ING	s, fo	R D	RUM	ARI	MAT	JRE	з.
×	ORS				FF	RONT	ANI	BAC	CK PI	TCHI	ES					ORS
RANC	DUCT		4	(3		8	1	0	1	.2	1	.4	1	6	DUCT
ENT	CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	CON
E	No.01	F	В	F	В	F	B	F	B	F	B	F	B	F	В	No. OF
000	702	173	179	113	119	85	91	67	73	55	61	47	53	41	47	702
00	704	173	179	115	121	85	91	67	73	55	61	47	53	41	47	704
000	708	173	179	115	121	85	91	67	73	55	61	47	53	41	47	708
QD	710	175	181	115	121	85	91	67	73_	57	63	47	53	41	47	710
@	712	175	181	115	121	85	91	69	75	57	63	47	53	41	47	712
000	714	175	181	115	121	87	93	69	75	57	63	47	55	41	41	714
Q	718	177	183	117	123	87	93	69	75	57	63	49	55	41	47	718
000	720	177	183	117	123	87	93	69	75	57	63	49	55	41	47	720
00	722	177	183	117	123	87	93	69	75	57	63	49	55	43	49	722
000	726	179	185	117	123	87	93	69	75	57	63	49	55	43	49	726
Q	728	179	185	119	125	87	93	69 -	75	57	63	49	55	43	49	728
@	730	179	185	119	125	89	95	69	75	57	63	49	55_	43	49	730
600	734	181	187	119	125	89	95	71	77	59	65	49	55	43	49	732
Ŵ	736	181	187	119	125	89	95	71	77	59	65	49	55	43	49	736
000	738	181	187	119	125	89	95	71	77	59	65	49	55	43	49	738
<u>(</u>)	740	181	187	121	127	89	95	71	77	59	65	49	55	43	49	740
000	744	183	189	121	127	89	95	71	77	59	65	49	57	43	49	744
Q	746	183	189	121	127	91	97	71	77	59	65	51	57	43	49	746
@	748	183	189	121	$\frac{127}{197}$	91	97	71	77	59	65	51	57	43	49	748
000	752	185	191	121 123	129	91	97	73	79	59	65	51	57	40	49	752
Ŵ	754	185	191	123	129	91	97	73	79	59	65	51	57	45	51	754
000	756	185	191	123	129	91	97	73	79	59	65	51	57	45	51	756
600	758	187	193	123	129	91	97	73	79	61	67	51	57	45	51	758
000	762	187	193	123	129	93	99	73	79	61	67	51	57	45	51	762
Q	764	187	193	125	131	93	99	73	79	61	67	51	57	45	51	764
600	766	189	195	125	131	93	99	73	79	61	67	51	57	45	51	766
00	770	189	$195 \\ 195$	$\frac{125}{125}$	131	93	99	73	79	61	67	51	57	40	51	708
Ŵ	772	189	195	125	131	93	99	75	81	61	67	53	59	45	51.	772
000	774	191	197	125	131	93	99	75	81	61	67	53	59	45	51	774
6	776	191	197	127	133	93	99	75	81	61	67	53	59	45	51	776
000	780	191	197	$\frac{121}{127}$	$\frac{133}{133}$	95	101	75	81	$\frac{-61}{61}$	67	53	<u>59</u> 59	45	$\frac{51}{51}$	718
Q	782	193	199	127	133	95	101	75	81	63	69	53	59	45	51	782
@	784	193	199	127	133	95	101	75	81	63	69	53	59	45	51	784
000	788	193	199	127	133	95	101	75	81	63	69	53	59	47	53	786
Q	790	195	201	129	135	95	101	75	81	63	69	53	59	47	53	790
000	792	195	201	129	135	95	101	77	83	63	69	53	59	47	53	792
600	794	195	201	129	135	97	103	77	83	63	69	53	59	47	53	794
000	798	195	201	129	135	97	103	77	83	63	69	53	59	47	53	796
Q	800	197	203	131	137	97	103	77	83	63	69	55	61	47	53	800

	MUL	TIPI	LE-C	IRCU	JIT, ⁻	TRIP	LE V	VINE	DING	S, F(DR D	RUN	AR	MAT	URE	s.
X	TORS				F	RONT	r ani	D BA	CK PI	TCH	ES					ORS
TRANC	NDUCT	-	4		6		8	1	.0	1	2	1	4	1	6	I DUCT
SE-EN	DF CO	PO	LES	PO	LES	PO	LES	PO	LES	PO.	LES	PO.	LES	PO	LES	PF CON
	Š	F	B	F	B	F	B	F	B	F	B	F	B	F	B	No.
000	802	197	203	131	137	97	$103 \\ 103$	77	83	63	69	55	61	$\frac{47}{47}$	53	802
@	806	199	205	131	137	97	103	77	83	65	71	55	61	47	53	806
000	810	199	205	131	137	97	103	77	83	65	71	55	61	47	53	808
@	812	199	205	133	139	99	105	79	85	65	71	55	61	47	53	812
æ	814	201	_207_	_133	139	99_	105	79	85	65	71	55	61	47	53	814
000	816	201	207	133	139	99	105	79	85	65	71	55	61	47	53	816
(00)	820	201	$\frac{207}{207}$	133	139 139	99	105	79	85	65	71	55	61	49	55	818
000	822	203	209	133	139	99	105	79	85	65	71	_ 55	61	49	55	822
0	824	203	209	135	141	99	105	79	85	65	71	55	61	49	55	824
(00)	826	203	209	135	141	101	107	79	85	65	71	55	61	49	55	826
00	830	205	209	$\frac{135}{135}$	141	101	107	79	85	67	73	57	63	49	55	828
Q	832	205	211	135	141	101	107	81	87	67	73	57	63	49	55	832
000	834	205	211	135	141	101	107	81	87	67	73	57	63	_49	55	834
(00)	836	205	211	137 127	143	101	107	81	87	67	73	57	63	49	55	836
000	840	207	213	137	143	101	107	81	87	67	10	57	63	49	55	838
œ	842	207	213	137	143	103	109	81	87	67	73	57	63	49	55	842
Q	844	207	213	137	143	103	109	81	87	67	73	57	63	49	55	844
000	846	209	$\frac{215}{915}$	137	$143 \\ 145$	103	109	81	87	67	73	57	63	49	55	846
œ	850	209	215	139	$145 \\ 145$	103	109	81	87	67	73	57	63	49	57	840
000	852	209	215	139	145	103	109	83	89	67	73	57	63	51	57	852
@	854	211	217	139	145	103	109	83	89	69	75	57	63	51	57	854
000	858	211	$\frac{217}{217}$	139	145	103	109	83	89	69	75	59	65	51	57	856
Q	860	211	217	141	147	105	111	83	89	69	75	59	65	51	57	860
QD	862	213	219	141	147	105	111	83	89	69	75	59	65	51	57	862
000	864	213	219	141	147	105	111	83	89	69	75	59	65	51	57	864
6	868	$\frac{213}{213}$	$\frac{219}{219}$	$141 \\ 141$	$\frac{147}{147}$	$105 \\ 105$	111	83	89	<u>69</u> 69	75	59	65 65	51	57	866
000	870	215	221	141	147	105	111	83	89	69	75	59	65	51	57	870
Q	872	215	221	143	149	105	111	85	91	69	75	_59	65	51	57	872
00	874	215	$\frac{221}{991}$	143	149	107	113	85	91	69	75	_59	65	51	57	874
00	878	$\frac{215}{217}$	223	143 143	149	107	113	85	91	71	75	59	65 65	51	57	876
œ.	880	217	223	143	149	107	113	85	91	71	77	59	65	51	57	880
000	882	217	223	143	149	107	113	85	91	71	77	59	65	53	59_	882
00	886	217	223	145	151	107	113	85	91	71	77	61	67	53	59	884
000	888	219	225	145	151	107	113	85	91	71	77	61	67	<u>- 53</u>	59	886
Q	890	219	225	145	151	109	115	85	91	71	77	61	67	53	59	890
Q	892	219	225	145	151	109	115	87	93	71	77	61	67	53	59	892
000	894	221	227	145	151	109	115	87	93	71	77	61	67	53	59	894
Q	898	221	227	147	$\frac{153}{153}$	109	115	87	93	71	77	61	67	53	59	896
000	900	221	227	147	153	109	115	87	93	71	77	61	67	53	59	900

	MUL	TIPL	E-C	IRCU	IT, 1	RIP	LE W	/IND	INGS	5, FC	R D	RUM	ARM	MATU	JRE	5.
*	ORS				FF	RONT	AND	BAC	K PI	ТСНЕ	CS					rors
RANC	DUCT	-	4	6	3	8	3	1	0	1	2	1	4	1	6	DUC
-ENT	CON	POI	LES	PO	LES	Pol	LES	PO	LES	PO	LES	PO	LES	POI	LES	CON
R	No. OF	F	В	F	В	F	В	F	B	F	В	F	В	F	В	No.01
Q	902	223	229	147	153	109	115	87	93	73	79	61	67	53	59	902
Q	904	223	229	147	153	109	115	87	93	73	79	61	67	53	59	904
000	908	223	229	147	$\frac{155}{155}$	111	117	87	93	73	79	61	67	53	59	.908
Q	910	225	231	149	155	111	117	87	93	73	79	61	67	53	59	910
000	912	225	231	149	155	111	117	89	95	73	79	63	69	53	59	912
00	914	225	231	149	155	111	117	89	95 95	73	79	63	69	55	61	914
000	918	227	233	149	155	111	117	89	95	73	79	63	69	55	61	918
@	920	227	233	151	157	111	117	89	95	73	79	63	<u>69</u>	55	61	920
000	922	227	233	151	157	113	119	89	95	73	79	63	69	55	61	922
Q	926	229	235	151	157	113	119	89	95	75	81	63	69	55	61	926
Q	928	229	235	151	157	113	119	89	95	75	81	63	69	55	61	928
000	930	229	235	151	157	113	119	89	95	75	81	63	69	55	61	930
6	934	231	237	153	159	113	119	91	97	75	81	63	69	55	61	934
000	936	231	237	153	159	113	119	91	97	75	81	63	69	55	61	_936
Q	938	231	237	153	159	115	121	91	97	75	81	63	69	55	61	938.
(00)	940	231	237	153	159	115	121	91	97	75	81	65	71	55	61	940
00	944	233	239	155	161	115	121	91	97	75	81	65	71	55	61	944
Q	946	233	239	155	161	115	121	91	97	75	81	65	71	57	63	946
000	948	233	239	155	161	115	121	91	97	75	81	65	$\frac{71}{71}$	57	63	948
6	950	235	241	155	161	115	121	93	99	77	83	65	71	57	63	952
000	954	235	241	155	161	117	123	93	99	77	83	65	71	57	63	954
Q	956	235	241	157	163	117	123	93	99	77	83	65	71	57	63	956
QQ	958	237	243	157	163	117	123	93	99	77	83	65	71	57	63	958
000	962	237	243	157	163	117	123	93	99	77	83	65	71	57	63	962
Q	964	237	243	157	163	117	123	93	99	77	83	65	71	57	63	964
000	966	239	245	157	163	117	123	93	99	77	83	65	71	57	63	966
600	908	239	245	159	165	119	125	93	99	77	83	67	73	57	63	970
000	972	239	245	159	165	119	125	95	101	77	83	67	73	57	63	972
œ	974	241	247	159	165	119	125	95	101	79	85	67	73	57	63	974
œ	976	241	247	159	165	119	125	95	101	79	85	67	73	57	63	976
000	918	241	247	$159 \\ 161$	165	119	$\frac{125}{125}$	$\frac{95}{95}$	101	79	85	67	73	59	65	980
Q	982	243	249	161	167	119	125	95	101	79	85	67	73	59	65	982
000	984	243	249	161	167	119	125	95	101	79	85	67	73	59	65	984
(00)	986	243	249	161	167	121	127	95	101	79	85	67	73	59	65	986
000	990	245	215	161	167	121	127	95	101	79	85	67	73	59	65	990
Q	992	245	251	163	169	121	127	97	103	79	85	67	73	59	65	992
Q	994	245	251	163	169	121	127	97	103	79	85	67	73	59	65	994
000	996	245	251	163	169	121	127	97	$\frac{103}{103}$	81	85	69	75	59	65	996
Q	1000	247	253	163	169	121	127	97	103	81	87	69	75	59	65	1000

	MUL	TIPL	E-CI	RCU	IT, 1	RIP	LEW	/IND	INGS	5, FO	R D	RUM	ARM	ΛΑΤΙ	JRES	5.
7	ORS				F	RONT	ANI	D BAC	CK PI	TCHI	ES			3.5		rors
RANC	DUCT	1	4	(3	8	3	1	0	1	2	1	4.	1	6	DUC
ENT	CON	PO	LES	PO	LES	POI	LES	POI	LES	PO	LES	PO	LES	POI	LES	FCON
E E	No.01	F	В	F	B	F	В	F	В	F	В	F	В	F	В	No. O
000	1002	247	253	163	169	123	129	97	103	81	87	<u>69</u>	75	59 59	65	1002
@	1004 1006	$\frac{247}{249}$	$\frac{255}{255}$	$105 \\ 165$	171	123	129	97	103	81	87	69	75	59	65	1000
000	1008	249	255	165	171	123	129	97	103	81	87	69	75	59	65	1008
(00)	1010 1012	249	$\frac{255}{255}$	165	171	123 123	129	97	103 105	81	87	69	75	61	67	1010
000	1014	251	$\frac{250}{257}$	165	171	123	129	99	105	81	87	69	75	61	67	1014
QD	1016	251	257	167	173	123	129	99	105	81	87	69	75	61	67	1016
(00)	1018 1020	$\frac{251}{951}$	$\frac{257}{957}$	$167 \\ 167$	173 173	125 195	131	99	$105 \\ 105$	81	87	69	75	61	67	1018 1020
Q	1020	253	259	167	173	125	131	99	105	83	89	69	75	61	67	1022
œ	1024	253	259	167	173	125	131	99	105	83	89	71	77	61	67	1024
000	1026 1028	253	259	167	173	125	131	99	105	83	89	71	77	61	67	1020
Q	1028	255	261	169	175	125	131	99	105	83	89	71	77	61	67	1030
000	1032	255	261	169	175	125	131	101	107	83	89	71	77	61	67	1032
@	1034	255	261	169	175	127	133	101	107	83	89	71	77	61	67	1034
000	1036	$\frac{299}{257}$	$\frac{261}{263}$	$169 \\ 169$	$175 \\ 175$	127	$\frac{133}{133}$	101	107	83	89	71	77	61	67	1038
œ	1040	257	263	171	177	127	133	`101	107	83	89	71	77	61	67	1040
Q	1042	257	263	171	177	127	133	101	107	83	89	71	77	63	69	1042
000	1044	257	$\frac{263}{265}$	$\frac{171}{171}$	177	$\frac{127}{197}$	133	101	107	85	91	71	77	63	69	1044
Q	1048	259	265	171	177	127	133	101	107	85	91	71	77	63	69	1048
000	1050	259	265	171	177	129	135	101	107	85	91	71	77	63	69	1050
@	1052	259	265	173	179	129	135	103	109	85	91	73	79	63	69	1052 1054
000	1054 1056	261	267	$\frac{173}{173}$	179	$\frac{129}{129}$	135	103	109	85	91	73	79	63	69	1056
æ	1058	261	267	173	179	129	135	103	109	85	91	73	79	63	69	1058
œ	1060	261	267	173	179	129	135	103	109	85	91	73	79	63	<u>69</u>	1060
000	1062	263	269	173	179	129	130	103	109	85	91	73	79	63	69	1064
Q	1064	263	269	175	181	131	137	103	109	85	91	73	79	63	69	1066
000	1068	263	269	175	181	131	137	103	109	85	91	73	79	63	69	1068
@	1070	265	271	175	181	131	137	103	$\frac{109}{111}$	87	93	73	79	63	69	1070
000	1072 1074	$\frac{265}{265}$	271	175	181	131	137	105	111	87	93	73	79	65	71	1074
@	1076	265	271	177	183	131	137	105	111	87	93	73	79	65	71	1076
QQ	1078	267	273	177	183	131	137	105	111	87	93	73	79	65	71	1078
000	1080	267	273	177	183	$131 \\ 133$	137	105	111	87	93	75	81	65	71	1080
Q	1084	267	273	177	183	133	139	105	111	87	93	75	81	65	71	1084
000	1086	269	275	177	183	133	139	105	111	87	93	75	81	65	71	1086
(20)	1088	269	275	-179 179	185	133	139	105	111	87	93	75	81	65	71	1088
000	1092	269	275	179	185	133	139	107	113	87	93	75	81	65	71	1092
œ	1094	271	277	179	185	133	139	107	113	89	95	75	81	65	71	1094
Q	1096	271	277	179	185	133	139	107	113	89	95	75	81	65	71	1096
600	11098	271	277	179	185	$\frac{135}{135}$	$141 \\ 141$	107	113	89	95	- 75	81	65	71	1100

	MUL	TIPI	_E-C	IRCL	ЛΤ, Έ	TRIP	LE V	VINE	DING	S, F	OR D	RUN	AR	MAT	URE	S.
×	rors				F	RONT	r ani	D BA	CK P	ITCH	ES					ORS
RANC	and		4.		6		8	1	10	1	12	1	4		16	DUCT
E-ENT	F COM	PO	LES	PO	LES	PC	DLES	PO	LES	PO	LES	PC	LES	PC	LES	CON
<u>م</u>	No. O	F	B	F	B	F	B	F	B	F	B	F	B	F	B	N 0. 0
@	1102	273	279	181	187	135	141	107	113	89	95	75	81	65	71	1102
000	1104	210	279	181	187	130	141	107	113	89	95	75	81	65	71	1104
00	1108	273	279	181	187	135	141	107	113	80	95	77	81	67	70	1100
000	1110	275	281	181	187	135	141	107	113	89	95	77	83	67	73	1110
æ	1112	275	281	183	189	135	141	109	115	89	95	77	83	67	73	1112
œ	11114	275	281	183	189	137	143	109	115	89	95	77	83	67	73	1114
000	1116	275	281	183	189	137	143	109	115	89	95	77	83	_67	73	1116
	1120	277	283	183	189	137	143	109	115	91	97	77	83	67	73	1118
000	1122	277	283	183	189	137	143	109	115	91	97	77	83	67	73	1120 1122
œ	1124	277	283	185	191	137	143	109	115	91	97	77	83	67	73	1124
QD	1126	279	285	185	191	137	143	109	115	91	97	77	83	67	73	1126
000	1128	279	285	185	191	137	143	109	115	91	97	77	83	67	73	1128
6	1132	279	285	185	191	139	140	109	110	91	97	77	83	67	73	1130
000	1134	281	287	185	191	139	145	111	117	91	97	77	83	67	73	1132
Q	1136	281	287	187	193	139	145	111	117	91	97	79	85	67	73	1134
Q	1138	281	287	187	193	139	145	111	117	91	97	79	85	69	75	1138
000	1140	281	287	187	193	139	145	111	117	91	97	79	85	69	75	1140
60	1142	283	289	187	193	139	145	111	117	93	99	79	_ 85	69	75	1142
000	1146	283	289	187	193	139	140	111	117	93	99	79	85	69	75	1144
Q	1148	283	289	189	195	141	147	111	117	93	99	79	85	69	75	1148
æ	1150	285	291	189	195	141	147	111	117	93	99	79	85	69	75	1150
000	1152	285	291	189	195	141	147	113	119	93	99	_ 79	85_	69	75	1152
6	1154 1156	285	291	189	195	$141 \\ 141$	147	113	119	93	99	79	85	<u>69</u>	75	1154
000	1158	287	293	189	195	141	147	113	119	93	99	79	85	<u>69</u> <u>69</u>	75	1150
@	1160	287	293	191	197	141	147	113	119	93	99	79	85	69	75	1160
@	1162	287	293	191	197	143	149	113	119	93	99	79	85	69	75	1162
000	1164	287	293	191	197	143	149	113	119	93	99	81	87	69	75	1164
00	1100 1168	289	295	191	197	143	149	113 112	119	95	101	81	87	69	75	1166
000	1170	289	295	191	197	143	149	110	119	90	101	81 91	87	69	75	1168
Q	1172	289	295	193	199	143	149	115	121	95	101	81	87	71	77	1170
@	1174	291	297	193	199	143	149	115	121	95	101	81	87	71	77	1174
000	1176	291	297	193	199	143	149	115	121	95	101	81	87	71	77	1176
<u></u>	11/8	291	297	193	199	145	151	115	121	95	101	81	87	71	77	1178
000	1182	293	299	193	199	145	151	115	121	95	101	81	87	71	77	1180
Q	1184	293	299	195	201	145	151	115	121	95	101	81	87	71	77	1182
æ	1186	293	299	195	201	145	151	115	121	95.	101	81	87	71	77	1186
000	1188	293	299	195	201	145	151	115	121	95	101	81	87	71	77	1188
00	1190	295	301	195	201	145	151	115	121	97	103	81	87	71	77	1190
000	1192	295	301	195	201	-145 147	151	117	123	_97	103	83	89	71	77	1192
0	1196	295	301	197	203	147	153	117	123	97	103	83	89	71	77	1194
@	1198	297	303	197	203	147	153	117	123	97	103	83	89	71	77	1190
000	1200	297	303	197	203	147	153	117	123	97	103	83	89	71	77	1200

	MUL	TIPL	E-CI	RCU	ΙТ, Τ	RIP	LE W	IND	ING	5, FC	RD	RUM	ARM	MATU	JRES	3.
7	ORS				FI	RONT	ANI	D BAG	CK PI	TCHI	ES					ORS
ANC	DUCT		4	(3		8	1	0	1	2	1	4,	1	6	DUCT
ENTF	CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	CONI
RE	40.0F	F	В	F	B	F	В	F	В	F	В	F	В	F	В	No. OF
œ	1202	297	303	197	203	147	153	117	123	97	103_	83	89	73	79	1202
QD	1204	297	303	197	203	147	153	117_	123	97	103	83	89	73	79	1204
000	1206	299	305	197	203	147	153	117	123	97	103	83	89_	73	79	1206
6	1210	299	305	199	205	149	155	117	123	97	103	83	89	73	79	1210
000	1212	299	305	199	205	149	155	119	125	97	103	83	89	73	79	1212
Q	1214	301	307	199	205	149	155	119	125	99	105_	83	89	73	79	1214
œ	1216	301	307	199	205	149	155	119	125	99	105	83	89	73	79	1216
000	1218	301	307	201	205	149	155	119	125	99	105	85	91	73	79	1218
(QQ)	1222	303	309	201	207	149	155	119	125	99	105	85	91	73	79	1222
000	1224	303	309	201	207	149_	155	119	125	99	105	85	91	73	79	1224
œ	1226	303	309	201_	207	151	157	119_	125	99	105	85	91	73_		1226
œ	1228	303	309	201	207	151	157	119	125	99	105	85	91	73	79	1228
000	1230 1932	305	311	201	207	151	$\frac{157}{157}$	19	125	99	105	85	91	73	79	1230 1939
0	1234	305	311	203	209	151	157	121	127	99	105	85	91	75	81	1234
000	1236	305	311	203	209	151	157	121	127	99	105	85	91	75	81	1236
œ	1238	307	313	203	209	151	157_	121	127	101_	107	85	91	75	81	1238
(00)	1240	307	313	203	209	151	157	121	127	101	107	85		75	81	1240
000	$\frac{1242}{1244}$	$\frac{307}{307}$	$\frac{313}{313}$	$\frac{203}{205}$	$\frac{209}{211}$	153	159 159	121	$\frac{127}{197}$	101	107	85	91	75	81	1242 1944
6	1246	309	315	205	211	153	159	121	127	101	107	85	91	75	81	1246
000	1248	309_	315	205	211	153	159	121	127	101	107_	_ 87_	_93_	75	81	1248
œ_	1250	309	315	205	211	153	159	121	127	101	107	87	93	75	81	1250
QQ	1252	309	$\frac{315}{217}$	205	211	153	159	123	129	101	107	87	93	75	81	1252
000	1204 1256	311	$\frac{517}{317}$	205	211 213	153	159	120	129	101	107	81	93	75	81	1204
Q	1258	311	317	207	213	155	161	123	129	101	107	87	93	75	81	1258
000	1260	311	317	207	213	155	161	123	129	101	107	87	93	75	81	1260
œ	1262	313	_319	207	213	155	161	123	129	103	109	87	93	75	81	1262
(20)	1264	313	319	207	213	155	161	123	129	103	109	87	93	75	81	1264
000	1200 1268	$\frac{313}{313}$	319	201	$\frac{215}{215}$	155	161	123	129 129	103	109	87	95	77	83	1200 1268
Ŵ	1270	315	321	209	215	155	161	123	129	103	109	87	93	77	83	1270
000	1272	_315_	321	209	215	155	161	125	131	_103_	109	87	93	77	83	1272
æ	1274	315	321	209	215	157	163	125	131	103	109	87	93	77	_83_	1274
(00)	1276	315	321	209	215	157	163	125	131	103	109	89	95	77	83	1276
600	1218	$\frac{-517}{317}$	$\frac{-340}{323}$	211	$\frac{213}{217}$	157	163	$125 \\ 125$	131	103	109	89	<u>95</u> 95	77	83	1218
Q	1282	317	_323	211	217	157	163	125	131	103	109	89	95	77	83	1282
000	1284	_317	323	211	217	157	163_	125	131	103	109	89	95	77	83	1284
œ	1286	319	325	211	217	157	163	125	131	105	111	89	95	77	83	1286
(00)	1288	319	325	211_	217	157	163	125	131	105	111	- 89	95	77	83	1288
000	1292	319	325	213	219	159	165	120	133	105	111	89	95	77	83	1290
·@	1294	321	327	213	219	159	165	127	133	105	111	89	95	77	83	1294
000	1296	321	327	213	219	159	165	127	133	105	111	89	_95	.77	83	1296
00	1298	321	327	213_		159	165	127	133_	105	_ 111_	89	95	79	85	1298
all all	1900	021	021	210	219	109	100	127	100	105	111	09	90	19	80	1300

	MUL	TIPL	E-C	IRCU	ЛΤ, Ί	RIP	LE V	VIND	ING	S, FC	DR D	RUM	ARM	MATU	JRES	5.
~	ORS				FF	RONT	ANI	BAC	CK PI	TCHI	ES					rors
ANC	DUCT	4	4	(6		8	1	0	1	2	1	4	1	6	DUCI
ENTE	CON	PO	LES	PO	LES	POI	LES	PO	LES	PO	LES	PO	LES	PO	LES	CON
RE	No. 0F	F	В	F	B	F	В	F	В	F	B	F	B	F	В	No. OF
000	1302	323	329	213	219_	159	165	127	133	105	111	89	95	79	85	1302
@	1304	323	329	215	221	159	165	127	133	105	111	91	97	79	85	1304
000	1306	$\frac{323}{323}$	$\frac{329}{329}$	$\frac{215}{215}$	$\frac{221}{221}$	161	167	127 127	$\frac{155}{133}$	105	111	91	97	79	85	1308
(20)	1310	325	331	215	221	161	167	127	133	107	113	91	97	79	85	1310
QD	1312	325	331	215	221	161	167	129	135	107	113	91	97	79	85	1312
000	1314	325	331	215	221	161	167	129	135	107	113	91	97	79	85	1314
Q	1318	327	333	217	223	161	167	129	135	107	113	91	97	79	85	1318
000	1320	327	333	217	223	161	167	129	135	107	113	91	97	79	85	1320
@	1322	327	333	217	223	163	169	129	135	107	113 112	91	97	79	85	1322
000	1324 1326	329	335	$\frac{217}{217}$	223	163	169	129	135	107	113	91	97	79	85	1326
QQ	1328	329	335	219	225	163	169	129	135	107	113	91	97	79	85_	1328
00	1330	329	335	219	225	163	169	129	135	107	113	91	97	81	87	1330
000	1332	329	335	219	225	163	169	131	137	107	113	93	99	81	87	1332
60	1336	331	337	219	225	163	169	131	137 137	109	115	93	99	81	87	1334 1336
000	1338	331	337	219	225	165	171	131	137_	109	115_	93	99_	81	87	1338
00	1340	331	337	221	227	165	171	131	137	109	115	93	99	81	87	1340
00	1342	333	339	221	227	165	171	131	137 127	109	115	93	99	81	87	1342
000	1346	333	339	221	227	165	171	131	137	109	115	93	99	81	87	1346
Ŵ	1348	333	339	221	227	165	171	131	137	109	115.	93	99	81	87	1348
000	1350	335	341	221	· 227	165	171	131	137	109	115	93	99	81	87	1350
00	1352	335	$\frac{341}{241}$	223	229	165	171	133	139	109	115	93	99	81	87	1352
000	$\frac{1504}{1356}$	335	341	223	229	167	173	133	139	109	115	93	99	81	87	1356
Q	1358	337	343	223	229	167	173	133	139	111	117	93	99	81	87	1358
Q	1360	337	343	223	229	167	173	133	139	111	117	95	101	81	87	1360
000	1362	337	343	223	229	167	173	133	139	111	117	95	101	83	89	1362
00	1304	339	345	220	231	167	173	133	139	111	117	95	$\frac{101}{101}$	83	89	1366
000	1368	339	345	225	231	167	173	133	139	111	117	95	101	83	89	1368
Q	1370	339	345	225	231	169	175	133	139	111	117	95	101	83	89	1370
œ	1372	339	345	225	231	169	175	135	141	111	117	95	$101 \\ 101$	83	89	1372
000	1374	341	$\frac{347}{347}$	225	231	169	175	135	141	111	117	95	101	83	89	1376
60	1378	341	347	227	233	169	175	135	141	111	117	95	101	83	89	1378
000	1380	341	347	227	233	169	175	135	141	1111	117	95	101	83	89	1380
(20)	1382	343	349	227	233	169	175	135	141	113	119	95	101	83	89	1382
000	1386	343	349	227	233	109	175	135	141	113	119	95	101	83	89	1386
QD	1388	343	349	229	235	171	177	135	141	113	119	97	103	83	89	1388
QD	1390	345	351	229	235	171	177	135	141	113	119	97	103	83	89	1390
000	1392	345	351	229	235	171	177	137	143	113	119	97	103	83	89	1392
(00)	1394	345	351	229	230	171	177	137	143	113	119	97	103	85	91	1396
000	1398	347	353	229	235	171	177	137	143	113	119	97	103	85	91	1398
Q	1400	347	353	231	237	171	177	137	143	113	119	97	103	85	91	1400

· · · · ·

.

	MUL	TIPL	E-CI	IRCU	JIT, 7	RIP	LEW	/IND	ING	S, FC	R D	RUM	ARM	ΛΑΤΙ	JRE	5.
7	rors				FI	RONT	ANI	D BAC	CK PI	TCHI	ES					rors
ANC	DNC	-	4	(6	8	3	1	0	1	2	1	4	1	6	DUC
ENTR	CON	PO	LES	POI	LES	PO	LES	PO	LES	PO	LES	POI	LES	PO	LES	CON
RE	No. 0F	F	В	F	В	F	В	F	В	F	В	F	В	F	В	No. OF
Q	1402	347	353	231	237	173	179	137	143	113	119	97	103	85	91	1402
000	1404	347	353	231	237	173	179	137	143	113	119	97	103	85	91	1404
<u>(00)</u>	1408	$\frac{349}{349}$	355	231	237	$\frac{173}{173}$	$\frac{179}{179}$	$\frac{137}{137}$	$143 \\ 143$	$110 \\ 115$	121	97	$103 \\ 103$	85	$\frac{91}{91}$	1408
000	1410	349	355	231	237	173	179	137	143	115	121	97	103	85	91	1410
Q	1412	349	355	233	239	173	179	139	145	115	121	97	103	85	91	1412
Q	1414	351	357	233	239	173	179	139	145	115	121	97	103	85	91	1414
000	1416	351	357	233	239	173	179	139	145	115	121	99	105 105	85	91	1416
60	1410 1420	351	$\frac{557}{357}$	233	239	$175 \\ 175$	$\frac{101}{181}$	139 139	145	$115 \\ 115$	$\frac{121}{121}$	99	$105 \\ 105$	85	91	$1410 \\ 1420$
000	1422	353	359	233	239	175	181	139	145	115	121	99	105	85	91	1422
00	1424	353	359	235	241	175	181	139	145	115	121	99	105	85	91	1424
Q	1426	353	359	235	241	175	181	139	145	115	121	99	105	87	93	1426
000	1428	353	309	235	241	175 175	181	139	140	115	$\frac{121}{193}$	99	105	87	93	1420
	1432	355	361	235	241	175	181	141	147	117	$\frac{120}{123}$	99	105	87	93	1432
000	1434	355	361	235	241	177	183	141	147	117	123	99	105	87	93	1434
Q	1436	355	361	237	243	177	183	141	1.47	117	123	99	105	87	93	1436
Q	1438	357	363	.237	243	177	183	141	_147	117	123	99	105	87	93	1438
000	1440	357	363	237	243	177	183	1.41	147	117	123	99	105	87	93	1440
00	1442	307	363	237	243	177	183	141	147	117	123	<u>99</u> 101	$\frac{100}{107}$	87	93	1442 1444
000	1446	359	365	237	243	177	183	141	147	117	123	101	107	87	93	1446
œ	1448	359	365	239	245	177	183	141	147	117	123	101	107	87	93	1448
æ	1450	359	365	239	245	179	185	_141_	147	117	123	• 101	107	87	93	1450
000	1452	359	365	239	245	179	185	143	149	117	123	101	107	87	93	1452
000	1404	301	367	239	245	179	185	143	149	119	120	101	$\frac{107}{107}$	87	95	1454
000	1458	361	367	239	245	179	185	143	149	119	125	101	107	89	95	1458
00	1460	361	367	241	247	179	185	143	149	119	125	101	107	89	95_	1460
œ	1462	363	369	241	247	179	185	143	149	119	125	101	107	89	95	1462
000	1464	363	369	241	247_	179	185	.143	149	119	125	101	107	89	95	1464
(00)	1466	363	369	241	247	181	187	143	149	119	125	101	107	89	95	1460
000	1470	365	371	241	247	181	187	143	149	119	125	101	107	89	95	1470
œ	1472	365	371	243	249	181	187	145	151	119	125	103	109	89	95	1472
Q	1474	365	371	243	249	181	187	145	151	119	125	_103	109	89	95	1474
000	1476	365	371	243	249	181	187	145	151	119	125	103	109	89	95	1476
00	1478 1480	367	373	243	249	181	187	145	151	121	127	103	109	89	95	1478
000	1480	367	373	243	249	181	189	145	151	121	127	103	109	89	95	1480
œ	1484	367	373	245	251	183	189	145	151	121	127	103	109	89	95	1484
œ	1486	369	375	245	251	183	189	145	151	121	127	103	109	89	95	1486
000	1488	369	375	245	251	183	189	145	151	121	127	103	109	89	95	1488
00	1490	369	375	245	251	183	189	145	151	121	127	103	109	91	97	1490
000	1494	371	377	245	251	183	189	147	153	121	197	103	109	91	97	1492
@	1496	371	377	247	253	183	189	147	153	121	127	103	109	91	97	1496
00	1498	_371	377	247	253	185	191	147	153	121	127	103	109	91	97	1498
000	1 1500	371	377	9.17	053	185	101	1.47	153	191	1.97	105	111	91	07	1500

	MUL	TIPL	E-C	IRCU	лт, τ	RIP	LE V	VIND	ING	S, FC	DR D	RUM	AR	MAT	URE	S.
~	ORS		12-1		F	RONI	ANI	D BA	CK PI	TCH	ES					ORS
RANO	DUCT		4	(6		8	1	0	1	2	1	.4	1	6	DUCT
ENT	CON	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PO	LES	PC	LES	CON
RE	No. 0F	F	В	F	В	F	В	F	B	F	В	F	В	F	B	No. OF
Q	1502	373	379	247	253	185	191	147	153	123	129	105	111	91	97	1502
œ	1504	373	379	247	253	185	191	147	153	123	129	105	111	91	97	1504
000	1506	373	379	247	253	185	191	147	153	123	129	105	111	91	97	1506
6	1510	375	381	249	255	185	191	141	153	123	129	105	111	91	97	1510
000	1512	375	381	249	255	185	191	149	155	123	129	105	111	91	97	1512
Q	1514	375	381	249	255	187	193	149	155	123	129	105	111	91	97	1514
œ	1516	375	381	249	255	187	193	149	155	123	129	105	111	91	97_	_1516
000	1518	377	383	249	255	187	193	149	155	123	129	105	111	91	97	1518
	1520	377	383	251	207	187	193	149	155	123	129	105	111	91	97	1599
000	1524	377	383	251	257	187	193	149	155	123	129	105	111	93	99	1524
Q	1526	379	385	251	257	187	193	149	• 155	125	131	105	111	93	99	1526
æ	1528	379	385	251	257	187	193	149	155	125	131	107	113	93	99	1528
000	1530	379	385	251	257	189	195	149	155	125	131	107	113	93	99	1530
00	1534	379	380	253	259	189	195	151	157	125	131	107	113	93	99	1532
000	1536	381	387	253	259	189	195	151	157	120	131	107	110	93	99	1536
@	1538	381	387	253	259	189	195	151	157	125	131	107	113	93	99	1538
Q	1540	381	387	253	259	189	195	151	157	125	131	107	113	93	99	1540
000	1542	383	389	253	259	189	195	151	157	125	131	107	113	93	99	1542
00	1544	383	389	255	261	189	195	151	157	125	131	107	113	93	99	1544
000	1548	383	389	200	261	191	197	151	157	125	131	107	113	93	99	1546
@	1550	385	391	255	261	191	197	151	157	120	133	107	113	93	99	1550
Q	1552	.385	391	255	261	191	197	153	159	127	133	107	113	93	99	1552
000	1554	385	391	255	261	191	197	153	159	127	133	107	113	95	101	1554
00	1556	385	391	257	263	191	197	153	159	127	133	109	115	95	101_	1556
(22)	1560	387	393	257	263	191	197	153	159	127	133	109	115	95	101	1558
000	1562	387	393	257	205	191	197	100	159	127	133	109	110	95	101	1562
@	1564	387	393	257	263	193	199	153	159	127	133	109	115	95	101	1564
000	1566	389	395	257	263	193	199	153	159	127	133	109	115	95_	101	1566
00	1568	389	395	259	265	193	199	153	159	127	133	109	115	95	101	1568
00	1570	389	395	259	265	193	199	153	159	127	133	109	115	95	101	1570
000	1574	301	390	209	200	193	199	155	161	127	133	109	115	95	101	1574
60	1576	391	397	259	265	193	199	155	161	129	135	109	115	95	101	1576
000	1578	391	397	259	265	195	201	155	161	129	135	109	115	95	101	1578
00	1580	391	397	261	267	195	201	155	161	129	135	_109	115	95	101	1580
00	1582	393	399	261	267	195	201	155	161	129	135	109	115	95	101	1582
(00)	1586	393	399	201	207	195	201	155	161	129 .	135	111	117	95	101	1596
00	1588	393	399	261	267	195	201	155	161	129	135	111	117	97	103	1588
000	1590	395	401	261	267	195	201	155	161	129	135	111	117	97	103	1590
æ	1592	395	401	263	269	195	201	157	163	129	135	111	117	97	103	1592
QQ	1594	395	401	263	269	197	203	157	163	129	135	111	117	97	103	1594
000	1596	395	401	203	269	197	203	157	163	129	135	111	117	97	103	1596
Q	1600	397	403	263	269	197	203	157	163	131	137	111	117	97	103	1600



LIST OF WORKS

ON

ELECTRICAL SCIENCE.

PUBLISHED AND FOR SALE BY

D. VAN NOSTRAND COMPANY,

23 Murray and 27 Warren Streets, New York.

- ARNOLD, E. Armature Windings of Direct Current Dynamos. Extension and application of a general winding rule. Translated from the original German by Francis B. DeGress, M. E. (In press)
- ATKINSON, PHILIP. Elements of Static Electricity, with full description of the Holtz and Topler Machines, and their mode of operating. Illustrated. 12mo, eloth. \$1.50.
 - The Elements of Dynamic Electricity and Magnetism. Second Edition. Illustrated. 12mo, cloth. \$2.00.
 - Elements of Electric Lighting, including Electric Generation, Measurement, Storage, and Distribution. Seventh Edition. Fully revised and new matter added. Illustrated. 8vo, cloth. \$1.50.
 - The Electric Transformation of Power and its Application by the Electric Motor, including Electric Railway Construction. Illustrated. 12mo, cloth. \$2.00.
- BADT, F. B. Dynamo Tender's Handbook. 70 Illustrations. 16mo, cloth. \$1.00.
 Electric Transmission Handbook. Illustrations and Tables. 16mo, cloth. \$1.00.
 Incandescent Wiring Handbook. Fourth Edition. Illustrations and Tables. 12mo, cloth. \$1.00.
 Bell Hanger's Handbook. Illustrated. 12mo, cloth. \$1.00.
- BIGGS, C. H. W. First Principles of Electrical Engineering. Being an attempt to provide an Elementary Book for those who are intending to enter the profession of Electrical Engineering. Second Edition. Illustrated. 12mo, cloth. \$1.00.
- BLAKESLEY, T. H. Papers on Alternating Currents of Electricity. For the use of Students and Engineers. Third Edition, enlarged. 12mo, cloth. \$1.50.
- BOTTONE, S. R. Electrical Instrument-Making for Amateurs. A Practical Handbook. Fourth Edition. Enlarged by a chapter on "The Telephone." With 48 Illustrations. 12mo, cloth. 50 cents.
 - Electric Bells, and All about Them. A Practical Book for Practical Men. With over 100 Illustrations. 12mo, cloth. 50 cents.
 - The Dynamo: How Made and How Used. A Book for Amateurs. Sixth Edition. 100 Illustrations. 12mo, cloth. \$1,00.
 - Electro-Motors: How Made and How Used. A Handbook for Amateurs and Practical Men. Illustrated. 12mo, cloth. 50 cents.

ABBOTT, A. V. The Electrical Transmission of Energy. A Manual for the Design of Electrical Circuits. 8vo, cloth. (In press.)

- CLARK, D. K. Tramways: Their Construction and Working. Embracing a Comprehensive History of the System, with Accounts of the Various Modes of Traction, a Description of the Varietics of Rolling Stock, and Ample Details of Cost and Working Expenses; with Special Reference to the Tramways of the United Kingdom. Second Edition. Revised and rewritten. With over 400 Illustrations. Thick 8vo, eloth. \$9.00.
- CROCKER, F. B., and WHEELER, S. S. The Practical Management of Dyamos and Motors. Third Edition. Illustrated. 12mo, eloth. \$1.00.
- CROCKER, F. B. Electric Lighting. (In press.)
- CUMMING, LINNÆUS, M.A. Electricity Treated Experimentally. For the Use of Schools and Students. Third Edition. 12mo, cloth. \$1.50.
- **DESMOND, CHAS. Electricity for Engineers.** Part I.: Constant Current. Part II.: Alternate Current. Revised Edition. Illustrated. 12mo, cloth. \$2.50.
- **DU MONCEL, Count TH. Electro-Magnets: The Determination of the Elements of their Construction.** 16mo, eloth. (No. 64 Van Nostrand's Science Series.) 50 cents.
- DYNAMIC ELECTRICITY. Its Modern Use and Measurement, chiefly in its application to Electric Lighting and Telegraphy, including: 1. Some Points in Electric Lighting, by Dr. John Hopkinson.
 2. On the Treatment of Electricity for Commercial Purposes, by J. N. Schoolbred. 3. Electric-Light Arithmetic, by R. E. Day, M.E. 18mo, boards. (No. 71 Van Nostrand's Science Series.) 50 cents.
- EMMETT, WM. L. Alternating Current Wiring and Distribution. 16mo, cloth. Illustrated. \$1.00.
- EWING, J. A. Magnetic Induction in Iron and Other Metals. Second issue. Illustrated. 8vo, cloth. \$4.00.
- FISKE, Lieut. BRADLEY A., U.S.N. Electricity in Theory and Practice: or, The Elements of Electrical Engineering. Eighth Edition. 8vo, eloth. \$2.50.
- FLEMING, Prof. J. A. The Alternate-Current Transformer in Theory and Practice. Vol. I.: The Induction of Electric Currents. 500 pp. Second Edition. Illustrated. 8vo, cloth. \$3.00. Vol. II.: The Utilization of Induced Currents. 594 pp. Illustrated. 8vo, cloth. \$5.00.

Electric Lamps and Electric Lighting. 8vo, eloth. \$3.00.

- GORDON, J. E. H. School Electricity. 12mo, cloth. \$2.00.
- GORE, Dr. GEORGE. The Art of Electrolytic Separation of Metals (Theoretical and Practical). Illustrated. 8vo, eloth. \$3.50.
- GUILLEMIN, AMÉDÉE. Electricity and Magnetism. Translated, revised, and edited by Prof. Silvanus P. Thompson, 600 Illustrations and several Plates. Large 8vo, cloth. \$8.00.
- GUY, ARTHUR F. Electric Light and Power, giving the result of practical experience in Central-Station Work. 8vo, cloth. Illustrated. \$2.50.
- HASKINS, C. H. The Galvanometer and its Uses. A Manual for Electricians and Students. Fourth Edition, revised. 12mo, morocco. \$1.50.
 - Transformers: Their Theory, Construction, and Application Simplified. Illustrated. 12mo, eloth. \$1.25.

- HAWKINS, C. C., and WALLIS, F. The Dynamo: Its Theory, Design, and Manufacture. 190 Illustrations. 8vo, cloth. \$3.00.
- HOBBES, W. R. P. The Arithmetic of Electrical Measurements. With numerous examples, fully worked. New Edition. 12mo, cloth. 50 cents.
- HOSPITALIER, E. Polyphased Alternating Currents. Illustrated. 8vo, cloth. \$1.40.
- HOUSTON, Prof. E. J. A Dictionary of Electrical Words, Terms, and Phrases. Third Edition. Rewritten and greatly enlarged. Large 8vo, 570 illustrations, cloth. \$5.00.
- INCANDESCENT ELECTRIC LIGHTING. A Practical Description of the Edison System, by H. Latimer. To which is added, The Design and Operation of Incandescent Stations, by C. J. Field; A Description of the Edison Electrolyte Meter, by A. E. Kennelly; and a Paper on the Maximum Efficiency of Incandescent Lamps, by T. W. Howells. Illustrated. 16mo, cloth. (No. 57 Van Nostrand's Science Series.) 50 cents.
- INDUCTION COILS: How Made and How Used. Fifth Edition. 16mo, cloth. (No. 53 Van Nostrand's Science Series.) 50 cents.
- KAPP, GISBERT, C.E. Electric Transmission of Energy and its Transformation, Subdivision, and Distribution. A Practical Handbook. Fourth Edition, thoroughly revised. 12mo, cloth. \$3.50.
 - Alternate-Current Machinery. 190 pp. Illustrated. (No. 96 Van Nostrand's Science Series.) 50 cents.

Dynamos, Alternators, and Transformers. Illustrated. 8vo, cloth. \$4.00.

KEMPE, H. R. The Electrical Engineer's Pocket-Book : Modern Rules, Formulæ, Tables, and Data. 32mo, leather. \$1.75.

A Handbook of Electrical Testing. Fifth edition. 200 illustrations. 8vo, cloth. \$7.25.

- KENNELLY, A. E. Theoretical Elements of Electro-Dynamic Machinery. Vol. I. Illustrated. 8vo, cloth. \$1.50.
- KILGOUR, M. H., and SWAN, H., and BIGGS, C. H. W. Electrical Distribution: Its Theory and Practice. Illustrated. 8vo, cloth. \$4.00.
- LOCKWOOD, T. D. Electricity, Magnetism, and Electro-Telegraphy. A Practical Guide and Handbook of General Information for Electrical Students, Operators, and Inspectors. Fourth Edition. Illustrated. 8vo, cloth. \$2.50.
- LORING, A. E. A Handbook of the Electro-Magnetic Telegraph. 16mo, cloth. (No. 39 Van Nostrand's Science Series.) 50 cents.
- MARTIN, T. C., and WETZLER, J. The Electro-Motor and its Applications. Third Edition. With an Appendix on the Development of the Electric Motor since 1888, by Dr. L. Bell. 300 Illustrations. 4to, cloth. \$3.00.
- MORROW, J. T., and REID, T. Arithmetic of Magnetism and Electricity. 12mo, cloth. \$1.00.
- MUNRO, JOHN, C.E., and JAMIESON, ANDREW, C.E. A Pocket-Book of Electrical Rules and Tables. For the use of Electricians and Engineers. Tenth Edition. Revised and enlarged. With numerous diagrams. Pocket size, leather. \$2.50.
- NIPHER, FRANCIS E., A.M. Theory of Magnetic Measurements. With an Appendix on the Method of Least Squares. 12mo, cloth. \$1.00.

- NOAD, H. M. The Student's Text-Book of Electricity. A New Edition. Carefully revised by W. H. Preece. 12mo, eloth. Illustrated. \$4.00.
- OHM, Dr. G. S. The Galvanic Circuit Investigated Mathematically. Berlin, 1827. Translated by William Francis. With Preface and Notes by the Editor, Thos. D. Loekwood. 12mo, eloth. (No. 102 Van Nostrand's Science Series.) 50 cents.
- PALAZ, A. Treatise on Industrial Photometry. Specially applied to Electric Lighting. Translated from the French by G. W. Patterson, Jr., Assistant Professor of Physics in the University of Michigan, and M. R. Patterson, B.A. Fully Illustrated. 8vo, cloth. \$4.00.
- PERRY, NELSON W. Electric Railway Motors. Their Construction, Operation, and Maintenance. An Elementary Practical Handbook for those engaged in the management and operation of Electric Railway Apparatus, with Rules and Instructions for Motormen. 12mo, cloth. \$1.00.
- PLANTÉ, GASTON. The Storage of Electrical Energy, and Researches in the Effects created by Currents combining Quantity with High Tension. Translated from the French by Paul B. Elwell. 89 Illustrations. 8vo. \$4.00.
- POOLE, J. The Practical Telephone Handbook. Illustrated. 8vo, cloth. \$1.00.
- POPE, F. L. Modern Practice of the Electric Telegraph. A Handbook for Electricians and Operators. An entirely new work, revised and enlarged, and brought up to date throughout. Illustrations. 8vo, eloth. \$1.50.
- PREECE, W. H., and STUBBS, A. J. Manual of Telephony. Illustrated. 12mo, cloth. \$4.50.
- RECKENZAUN, A. Electric Traction. Illustrated. 8vo, eloth. \$4.00.
- RUSSELL, STUART A. Electric-Light Cables and the Distribution of Electricity. 107 Illustrations. 8vo, cloth. \$2.25.
- SALOMONS, Sir DAVID, M.A. Electric-Light Installations. A Practical Handbook. Seventh Edition, revised and enlarged. Vol. I.: Management of Accumulators. Illustrated. 12mo, eloth. \$1.50.
 Vol. II.: Apparatus. Illustrated. 12mo, eloth. \$2.25. Vol. III.: Application. Illustrated. 12mo, eloth. \$1.50.
- SCHELLEN, Dr. H. Magneto-Electric and Dynamo-Electric Machines. Their Construction and Practical Application to Electric Lighting and the Transmission of Power. Translated from the third German edition by N. S. Keith and Percy Neymann, Ph.D. With very large Additions and Notes relating to American Machines, by N. S. Keith. Vol. I. with 353 Illustrations. Second Edition. \$5.00.
- SLOANE, Prof. T. O'CONOR. Standard Electrical Dictionary. 300 Illustrations. 8vo, cloth. \$3.00.
- SNELL, ALBION T. Electric Motive Power. The Transmission and Distribution of Electric Power by Continuous and Alternate Currents. With a Section on the Applications of Electricity to Mining Work. Illustrated. 8vo, eloth. \$4.00.
- SWINBURNE, JAS., and WORDINGHAM, C. H. The Measurement of Electric Currents. Electrical Measuring Instruments. Meters for Electrical Energy. Edited, with Preface, by T. Commerford Martin. Folding Plate and numerous Illustrations. 16mo, cloth. 50 cents.

- THOM, C., and JONES, W. H. Telegraphic Connections, embracing recent methods in Quadruplex Telegraphy. Twenty eolored Plates. Svo, cloth. \$1.50.
- THOMPSON, EDWARD P. How to Make Inventions; or, Inventing as a Science and an Art. An Inventor's Guide. Second Edition. Revised and Enlarged. Illustrated. 8vo, paper. \$1.00.
- THOMPSON, Prof. S. P. Dynamo Electric Machinery. With an Introduction and Notes by Frank L. Pope and II. R. Butler. Fully Illustrated. (No. 66 Van Nostrand's Science Series.) 50 cents.
 - Recent Progress in Dynamo-Electric Machines. Being a Supplement to "Dynamo-Electric Machinery." Illustrated. 12mo, cloth. (No. 75 Van Nostrand's Science Series.) 50 cents.
 - The Electro-Magnet and Electro-Magnetic Mechanism. Second Edition, revised. 213 Illustrations. 8vo, eloth. \$6.00.
- TREVERT, E. Practical Directions for Armature and Field-Magnet Winding. Illustrated. 12mo, eloth. \$1.50.
 - How to Bnild Dynamo-Electric Machinery. Embracing Theory Designing and the Construction of Dynamos and Motors. With Appendices on Field-Magnet and Armature Winding. Management of Dynamos and Motors, and useful Tables of Wire Gauges. Illustrated. 8vo, cloth. \$2.50.
- TUMLIRZ, Dr. Potential, and its Application to the Explanation of Electrical Phenomena. Translated by D. Robertson, M.D. 12mo, cloth. \$1.25.
- TUNZELMANN, G. W. de. Electricity in Modern Life. Illustrated. 12mo, cloth. \$1.25.
- URQUHART, J. W. Dynamo Construction. A Practical Handbook for the Use of Engineer Constructors and Electricians in Charge. Illustrated. 12mo, cloth. \$3.00.
- WALKER, FREDERICK. Practical Dynamo-Building for Amateurs. How to Wind for any Output. Illustrated. 16mo, cloth. (No. 98 Van Nostrand's Science Series.) 50 cents.
- WALMSLEY, R. M. The Electric Correct. How Produced and How Used. With 379 Illustrations. 12mo, cloth. \$3.00.
- WEBB, II. L. A Practical Guide to the Testing of Insulated Wires and Cables. Illustrated. 12mo, cloth. \$1.00.
- WORMELL, R. Electricity in the Service of Man. A Popular and Practical Treatise on the Application of Electricity in Modern Life. From the German, and edited, with copious additions, by , 'R. Wormell, and an Introduction by Prof. J. Perry. With nearly 850 Illustrations. Royal 8vo, eloth. \$6.00.
- WEYMOUTH, F. MARTEN. Drum Armatures and Commutators. (Theory and Practice.) A complete treatise on the theory and construction of drum-winding, and of commutators for closed-coil armatures, together with a full *résumé* of some of the principal points involved in their design; and an exposition of armature reactions and sparking. Illustrated. 8vo, cloth. \$3.00.

(5)













UNIVERSITY OF CALIFORNIA LIBRARY BERKELEY

Return to desk from which borrowed. This book is DUE on the last date stamped below.



LD 21-100m-9,'48 (B399s16)476



